

R Hoadley, 22 July 2014

LV and MV Drives 101

LV and MV Drives 101

Speaker name: Rick Hoadley
Speaker title: Principle Consulting Applications Engineer
Medium Voltage Drives
Company name: ABB
Location: New Berlin, WI

Agenda

LV and MV Drives 101

What is a VFD?

- Goals
- Motors
- Method

Line Side Requirements

- Harmonics
- Power Factor
- Ground Configurations


Motor Side Challenges

- NEMA MG-1
- Topologies
- Reflected Waves


Drive Protection

- PQ Events
- Over-Voltage
- Over-Current


This is a Non-Drive System

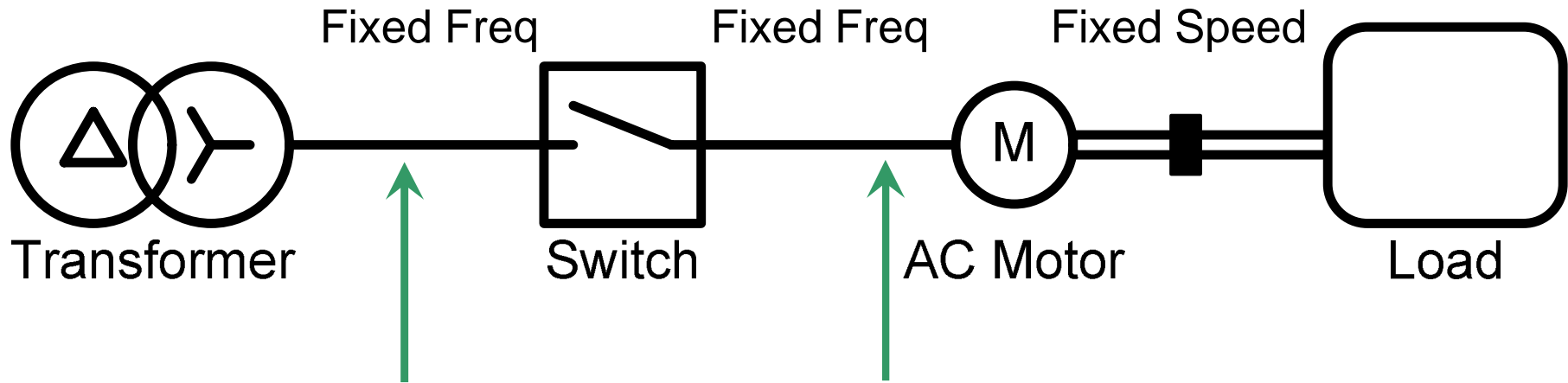

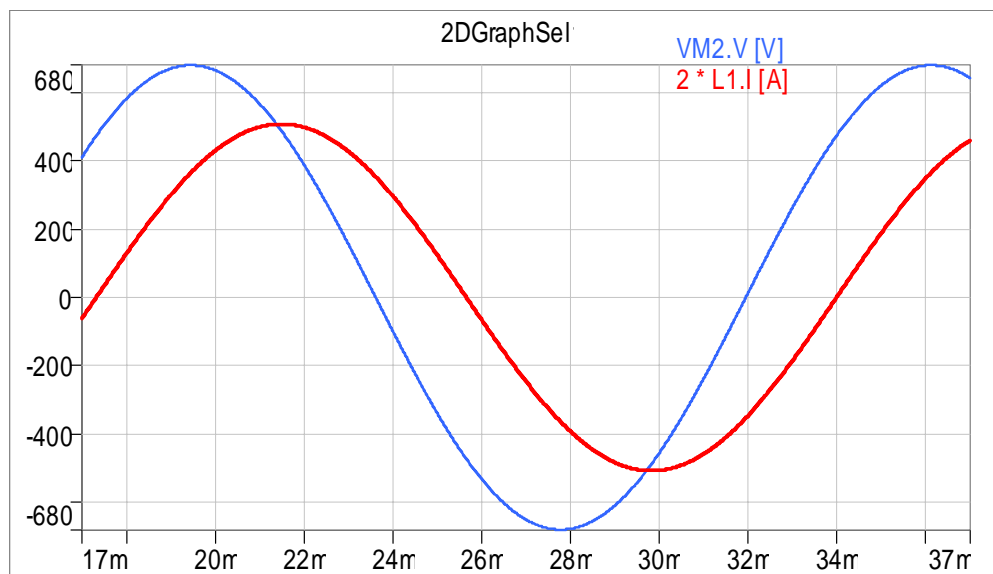Line Side: Sinusoidal Voltage Motor Side: Sinusoidal Current





This is a Drive System

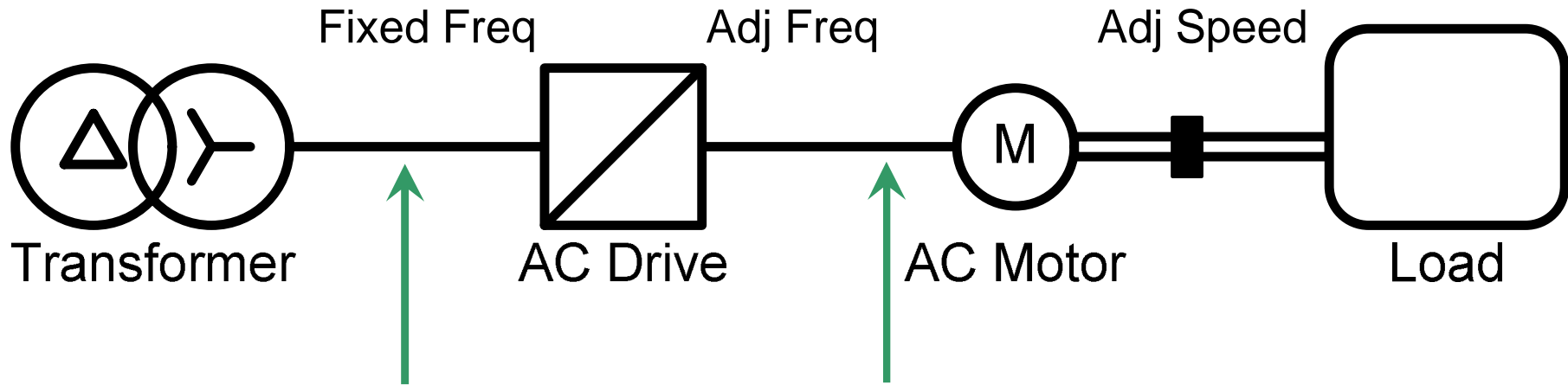

Line Side: Current Pulses


Motor Side: Voltage Pulses

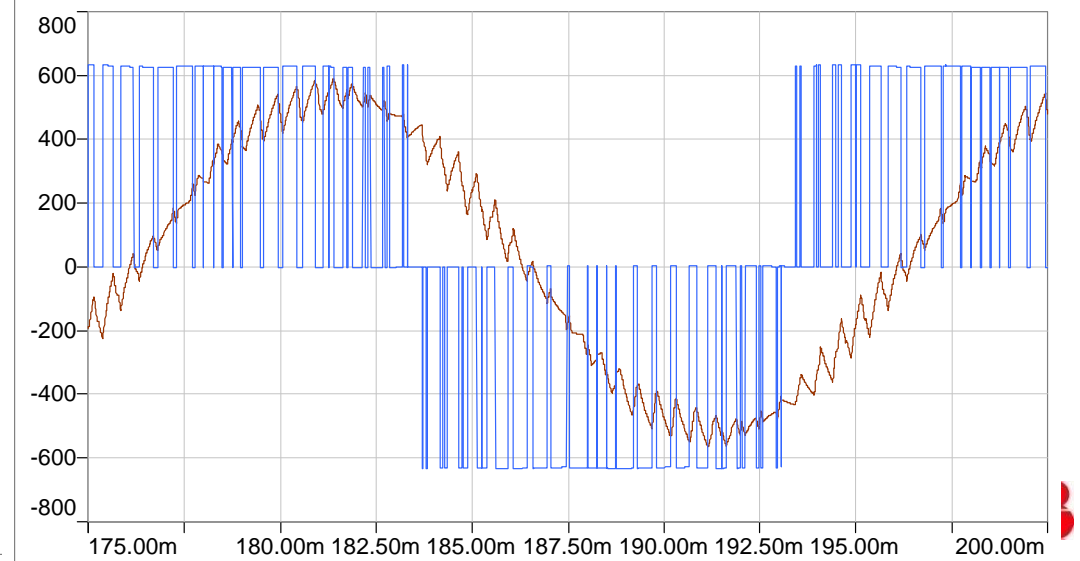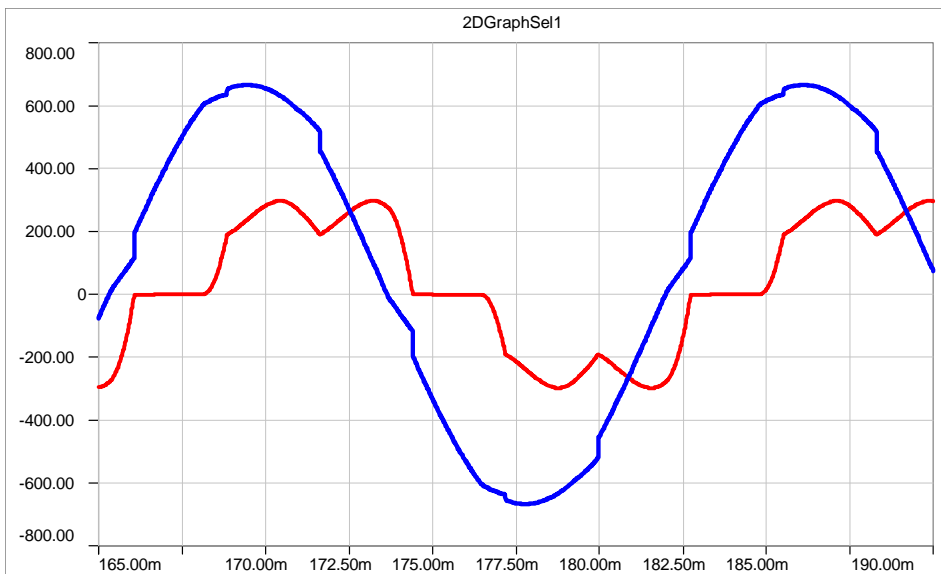

Why are AC drives used?

Why Use a VFD?


Large Operating Speed and Torque Area

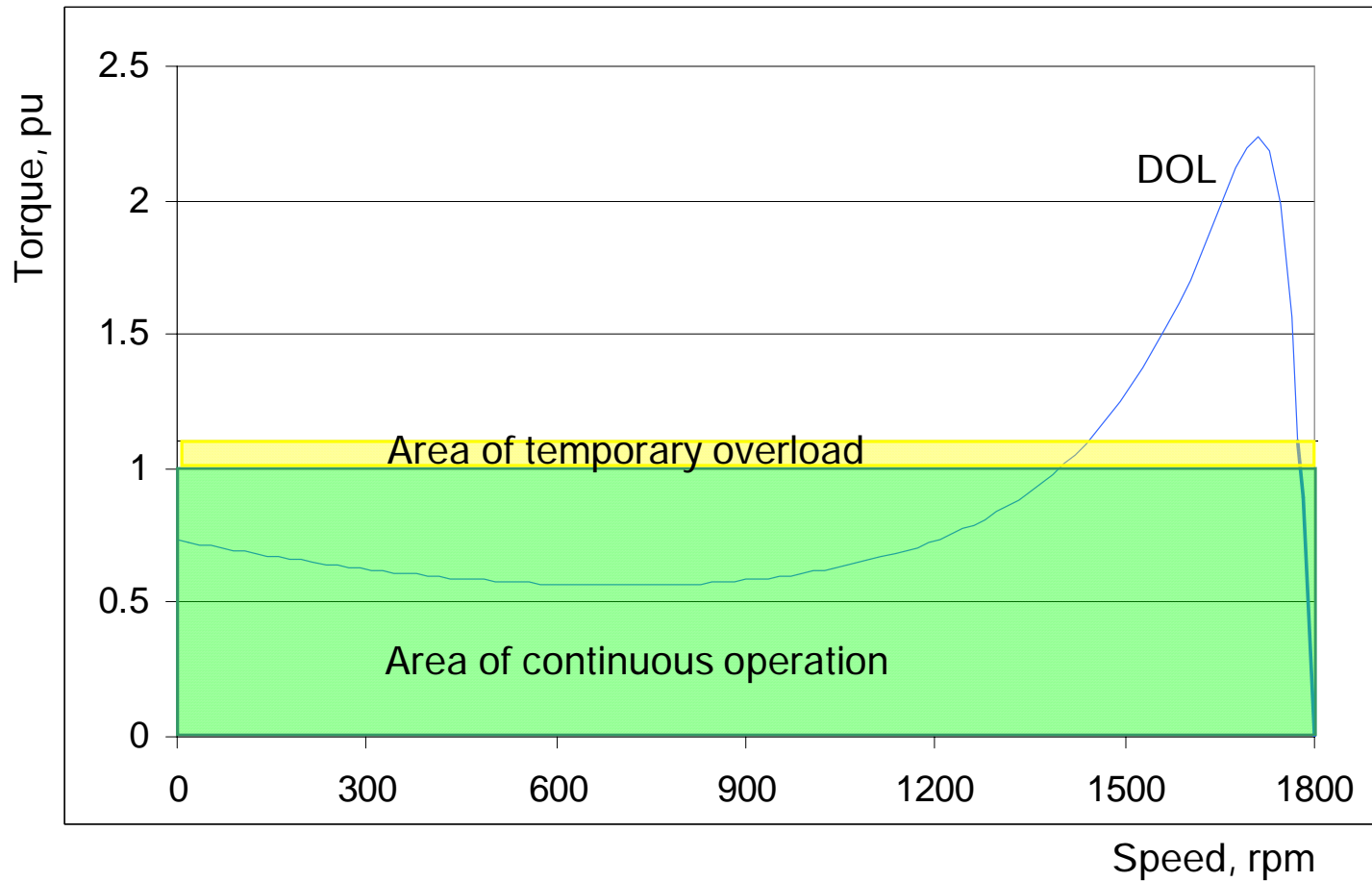

Why Use a VFD?

Power Savings = **Cost Savings** with Fans and Pumps

0.5 to 1.5 year payback !

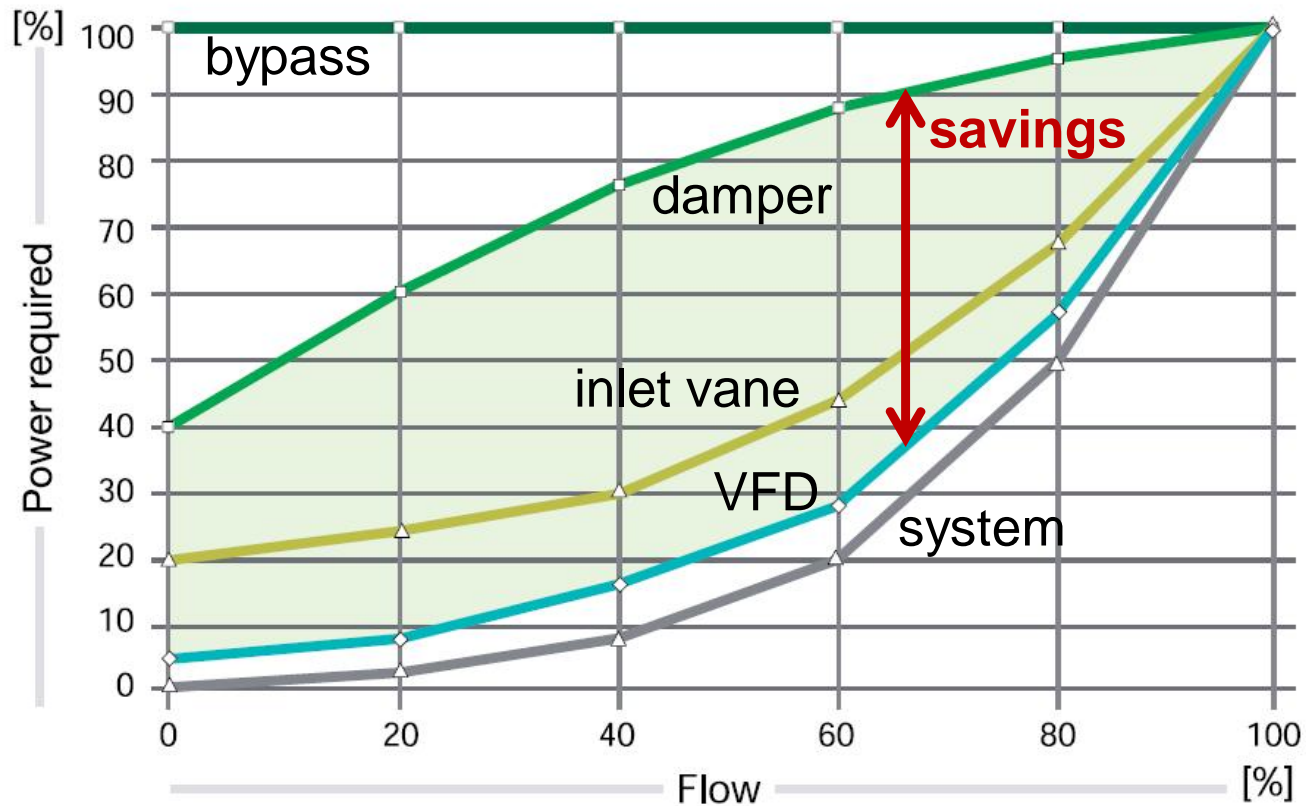

Why Use a VFD?

Adjustable speed to **Optimize Process**


Reduce production losses



Why Use a VFD?


Elimination of 6x Inrush Current for **Soft Starting**

DOL Start

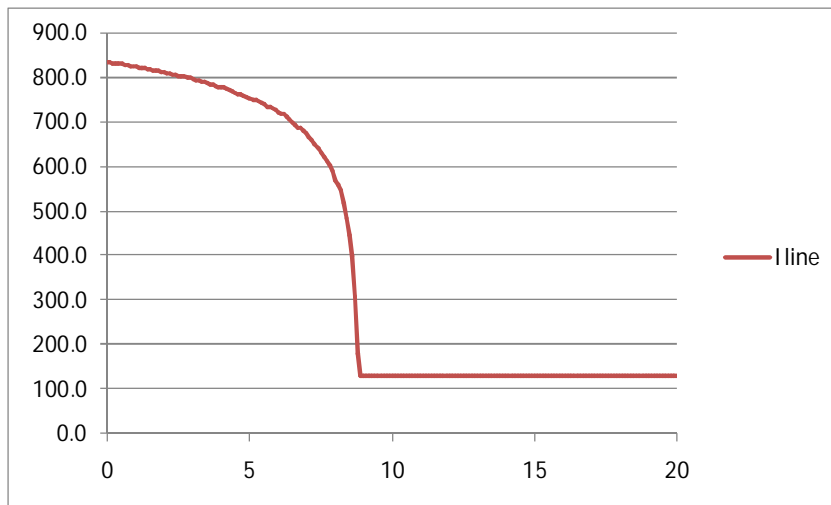

Line Current, A vs Time, s

VFD Start

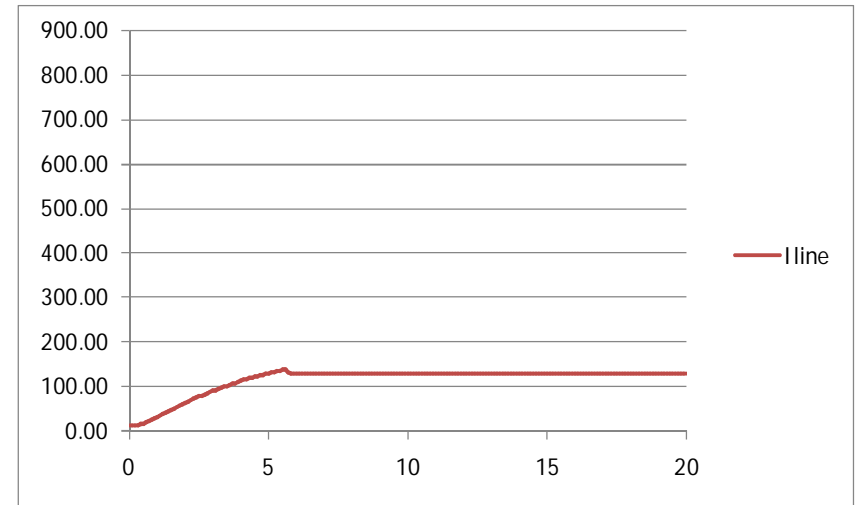


Line Current, A vs Time, s

Can have multiple starts per hour!


Why Use a VFD?

Greater **Starting Torque**

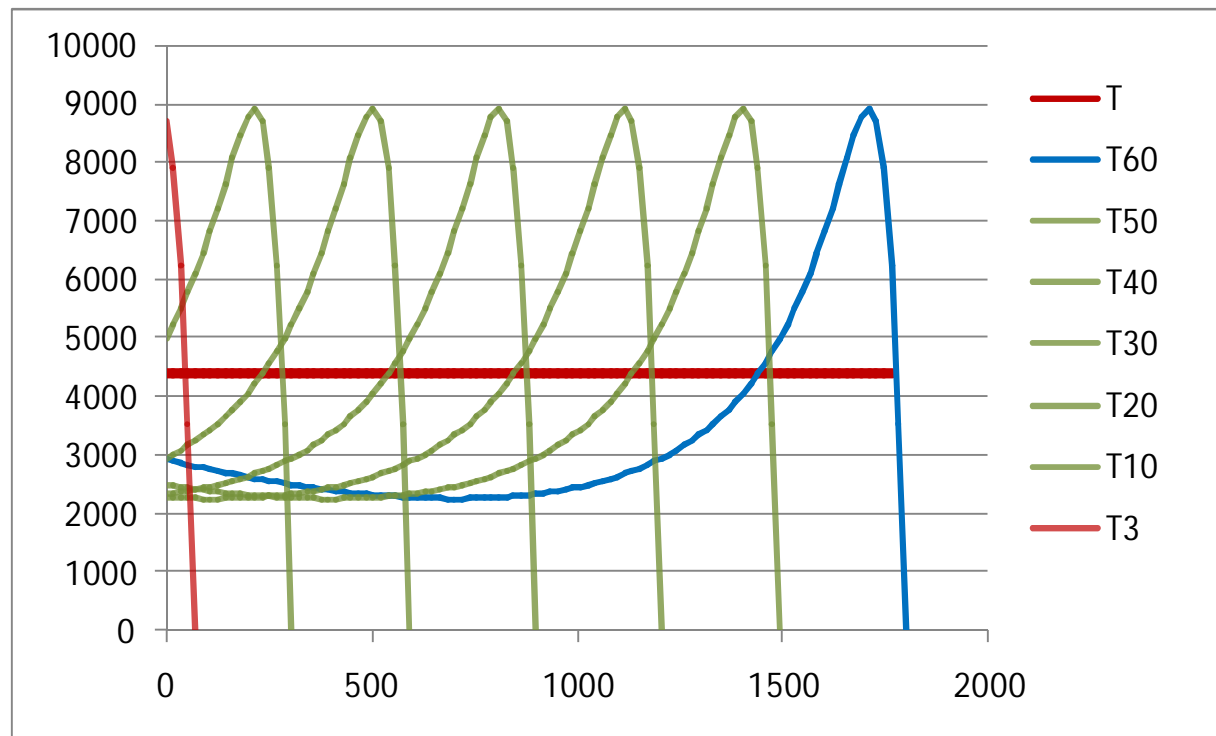

Why Use a VFD?

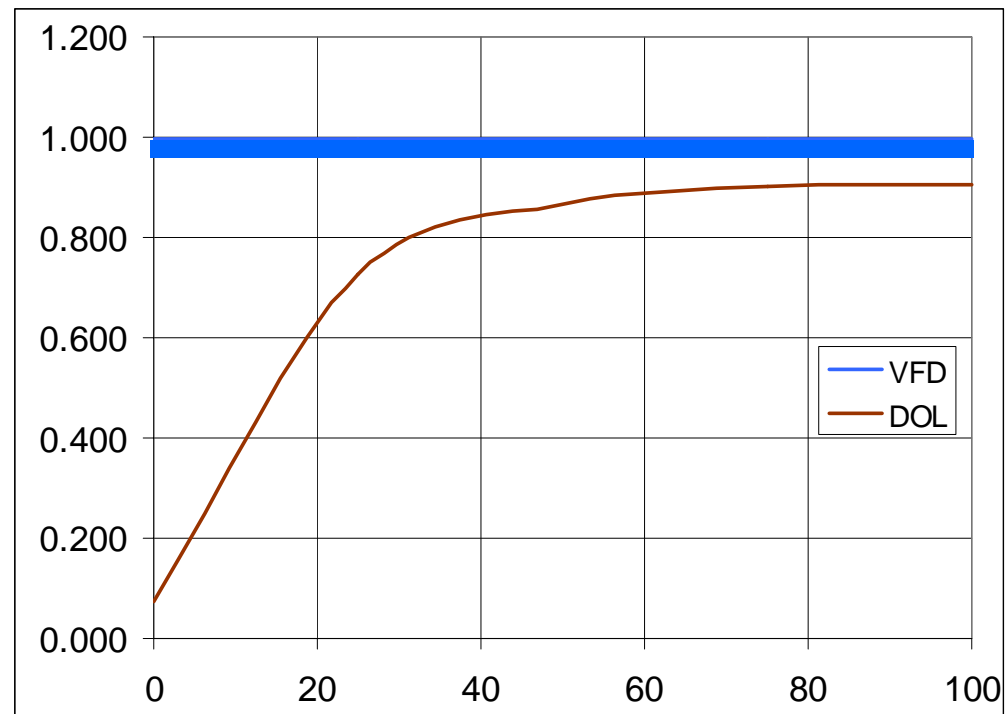Operate at or close to **Unity PF** throughout Load Range



Why Use a VFD?


Adjustable Torque Limit to prevent damage to equipment

No mechanical jerk, smooth acceleration




What is LV and MV?

What is LV and MV?

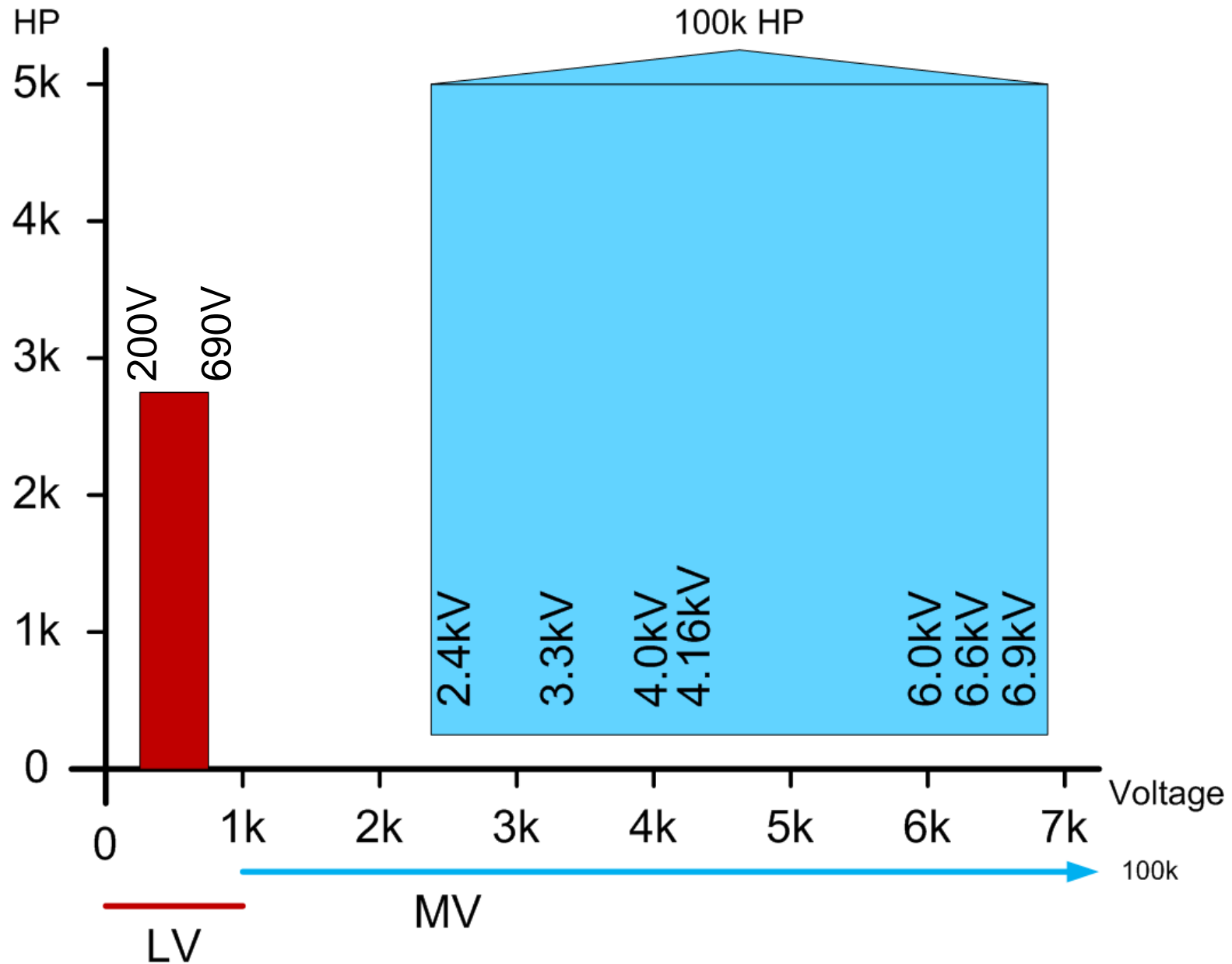




What is LV and MV?

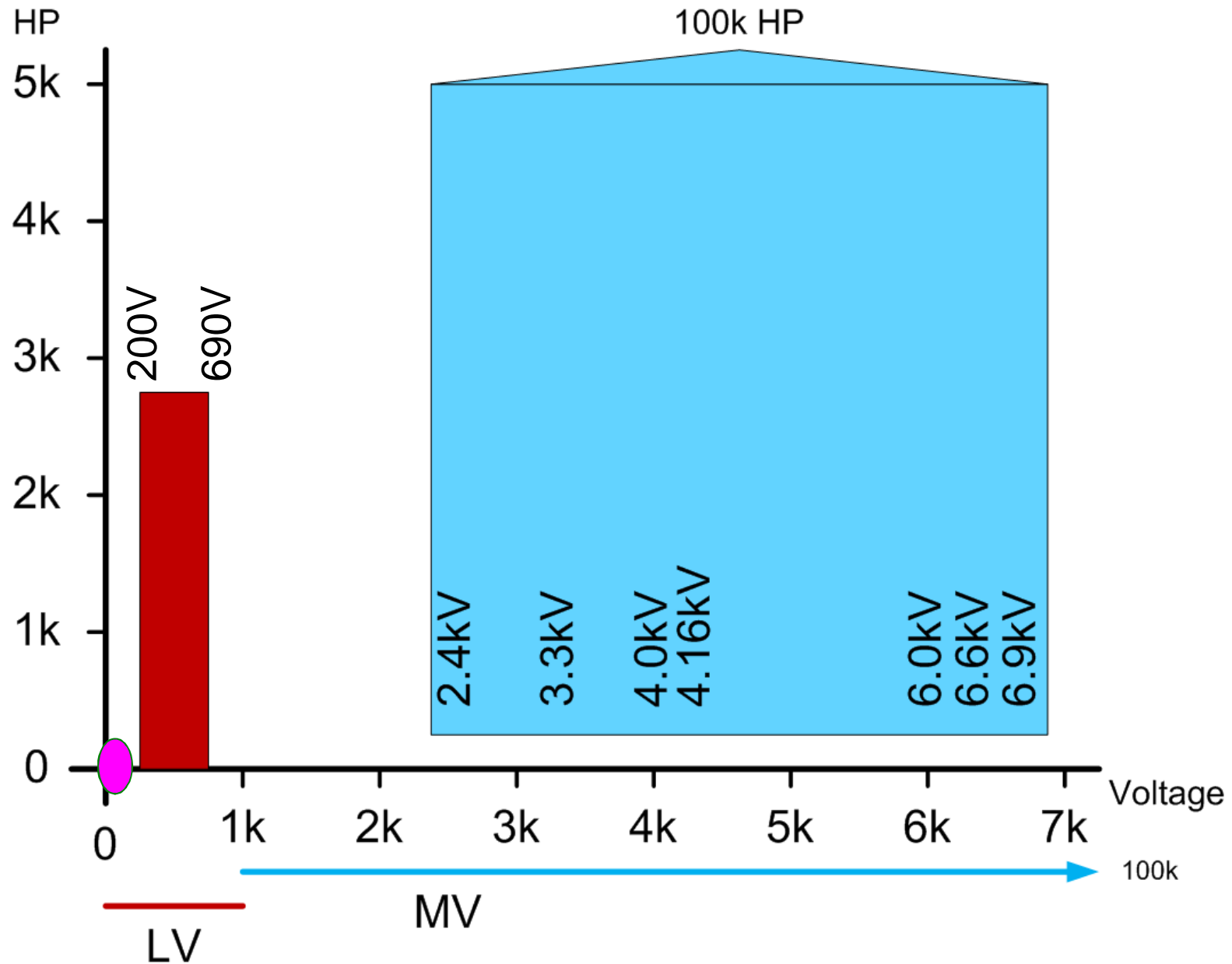

How do you change the speed of an AC motor?

How do you change motor speed?

Motor construction

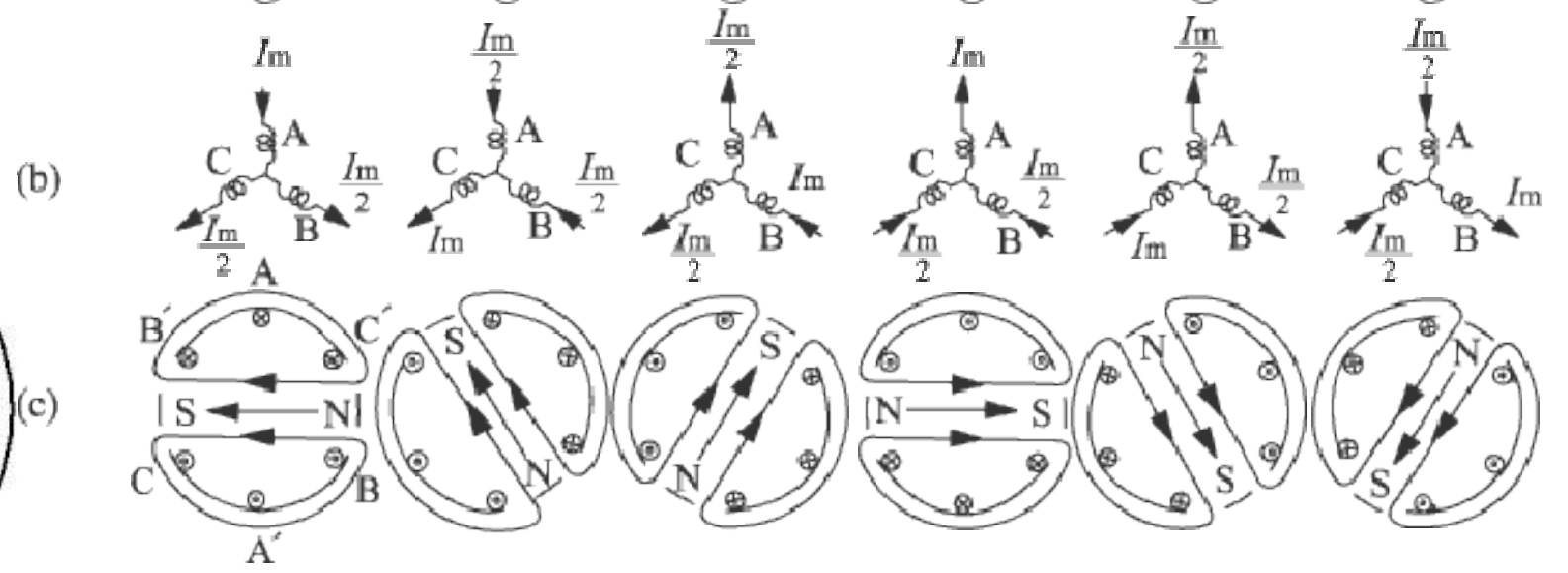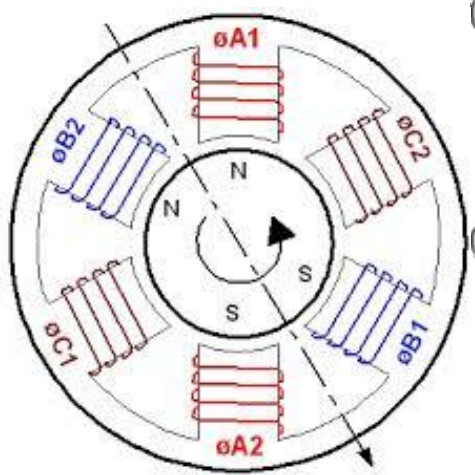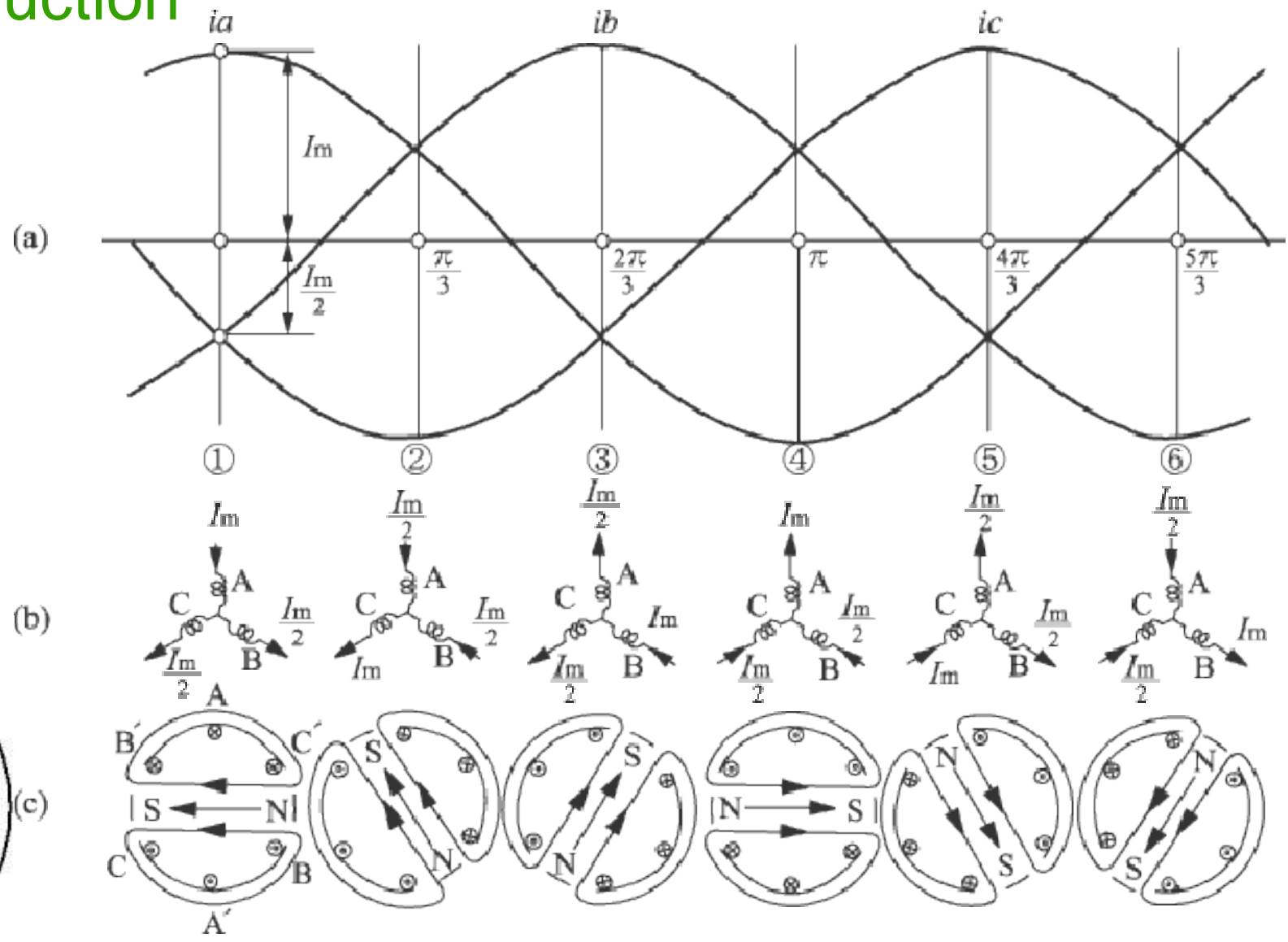

How do you change motor speed?

Motor equations

- Input

- $S_{in} = FLA \times kV \times \sqrt{3}$ [kVA]

FLA = Full load amps

- $S_{in} = P_{in} / PF_M$ [kVA]

PF_M = Motor power factor

- $P_{in} = S_{in} \times PF_M$ [kW]

- $P_{in} = P_{out} / \eta_M$ [kW]

η_M = Motor efficiency

- Losses

- $P_{loss} = P_{in} - P_{out}$

- Efficiency

- $\eta_M = P_{out} / P_{in}$

- **Speed** (synchronous)

- $n = 120 \times f / p$ [rpm]

f = Frequency, Hz


p = Number of poles (2,4,6, ...)




How do you make variable
frequency AC?

AC Drive Classifications

* used in MV drives

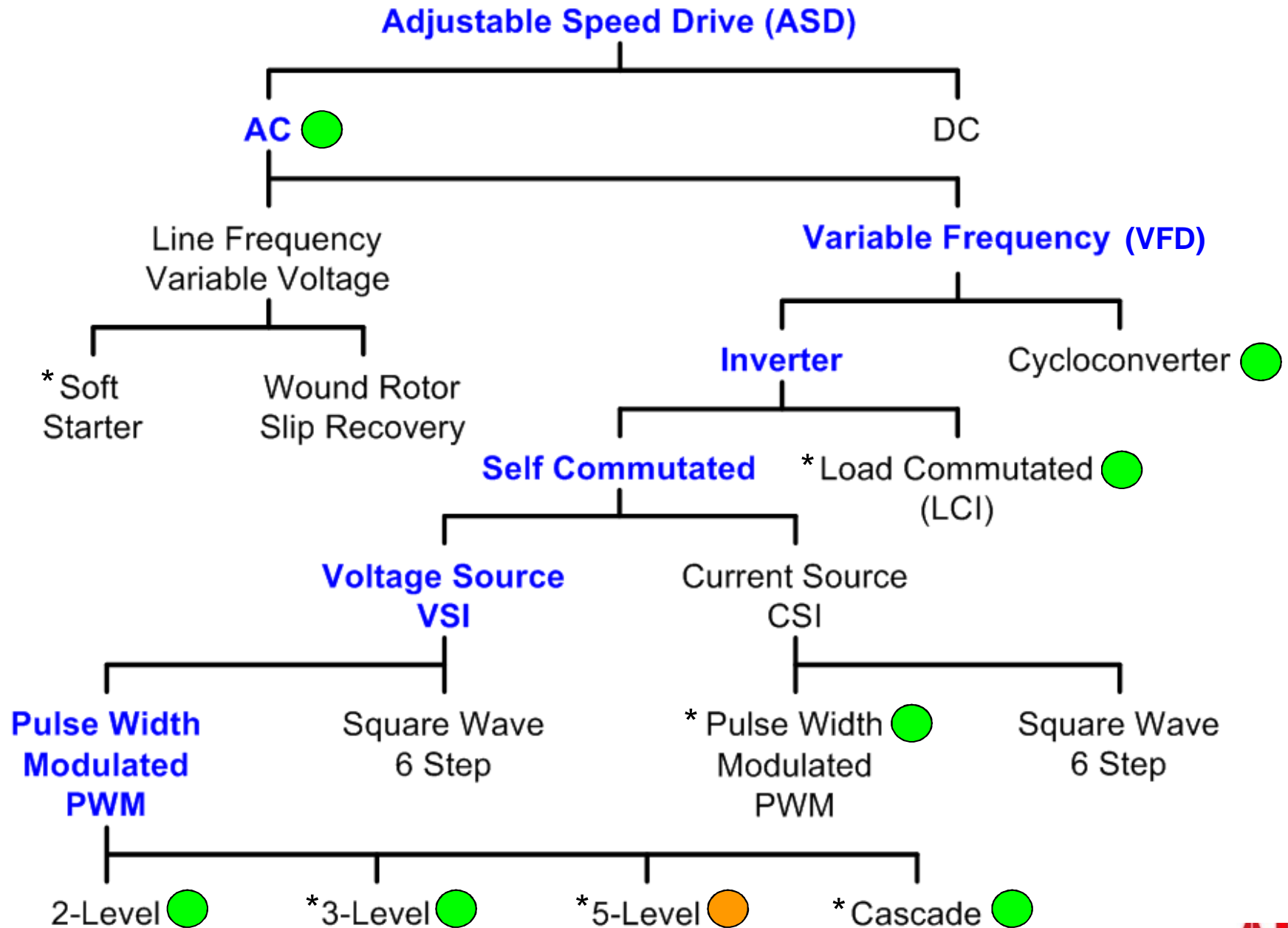


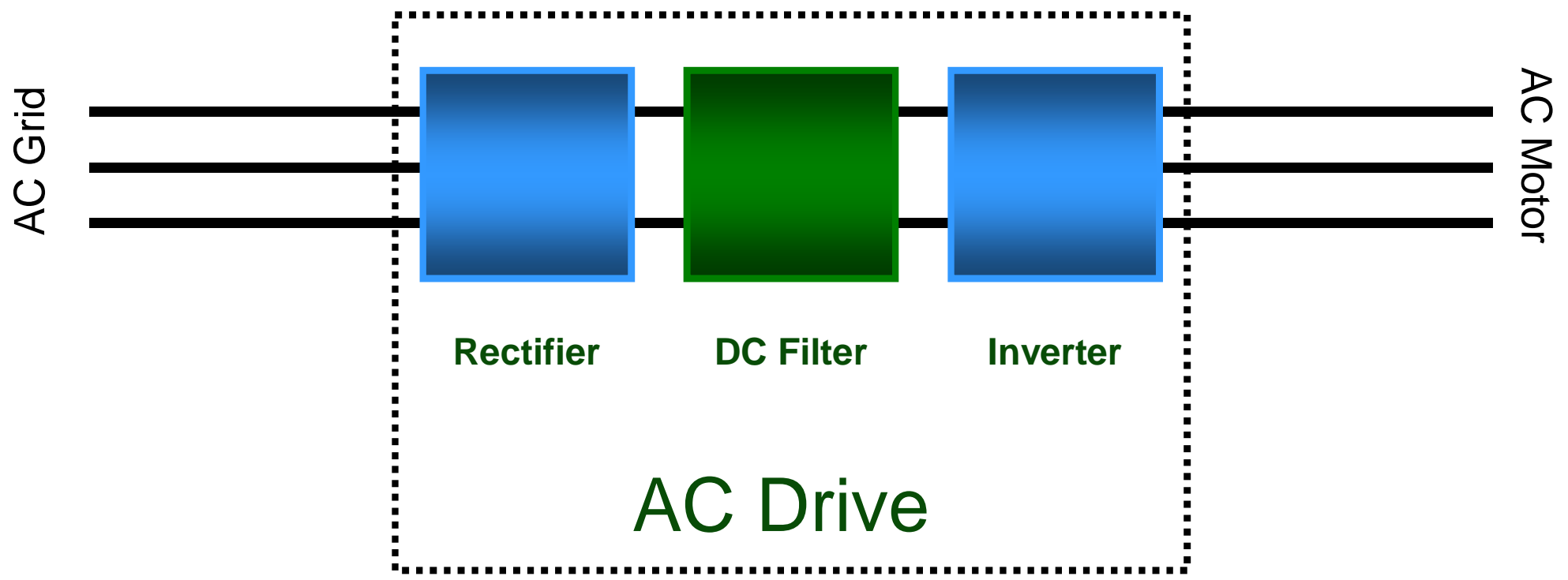General Block Diagram of a Basic AC Drive



Basic AC Drive Topology

6-Pulse

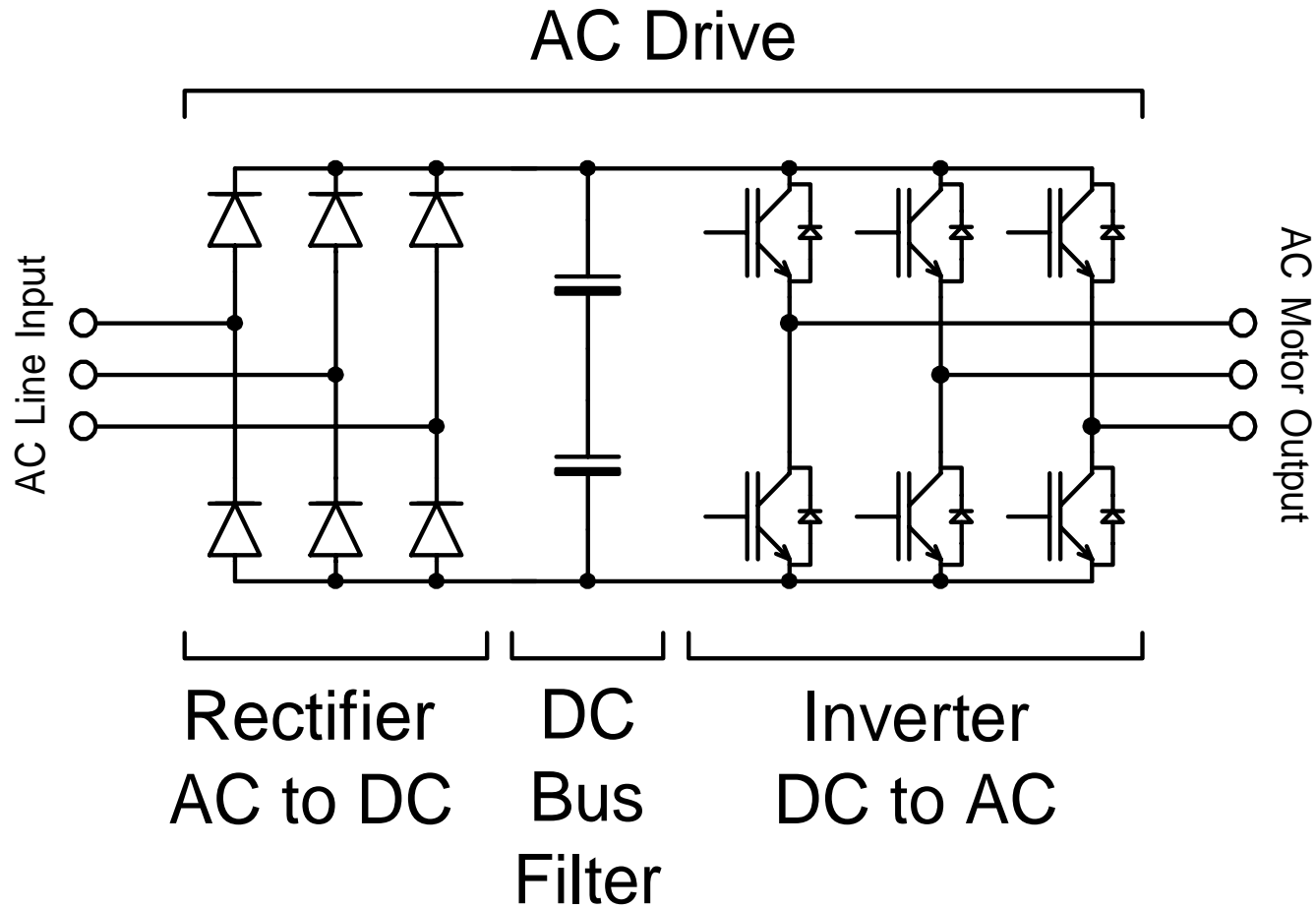


Fixed AC Voltage
Fixed AC Frequency

Fixed DC Voltage

Adjustable AC Voltage
Adjustable AC Frequency


What We'd Like to See -

480Vac / 4160Vac line-to-line

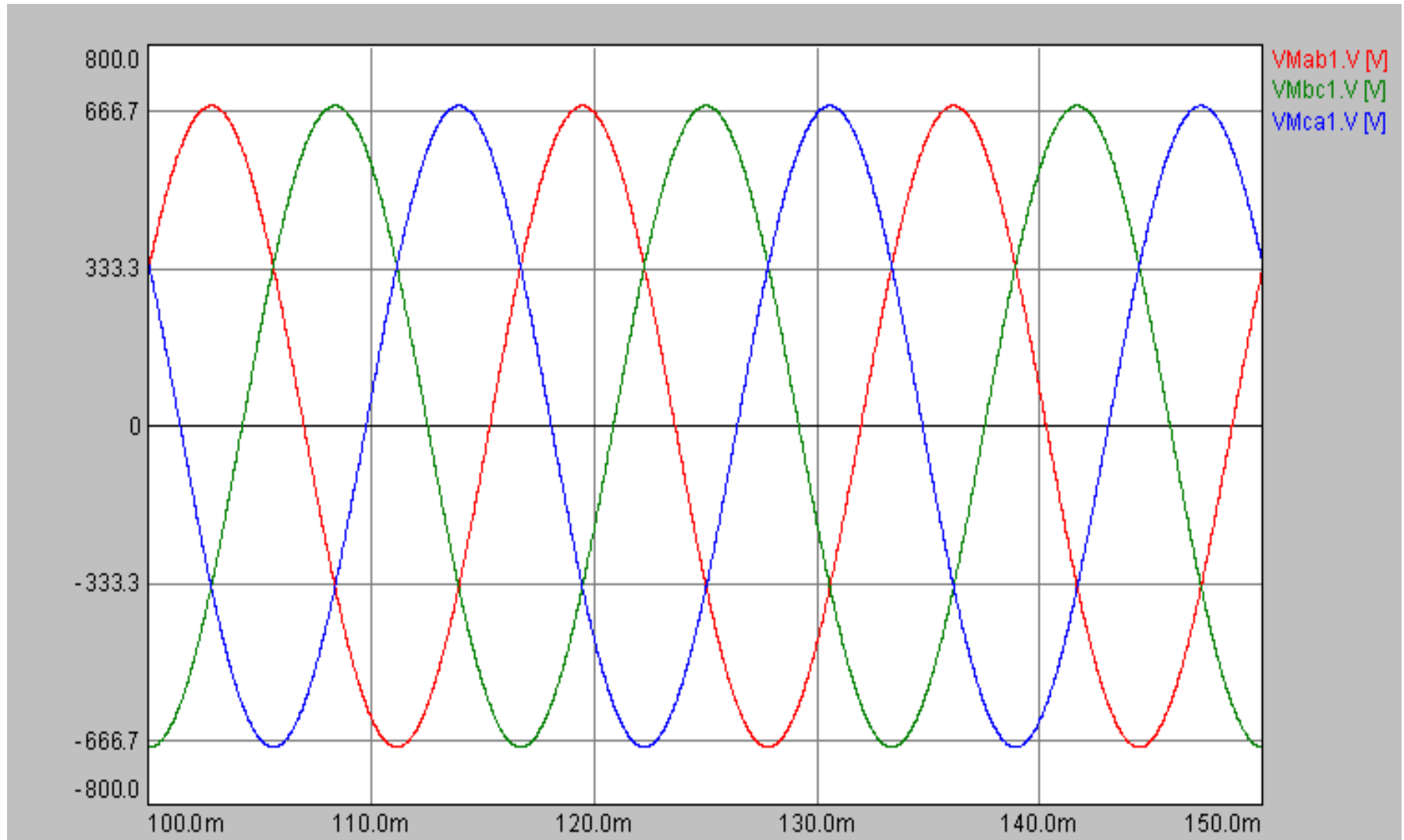

An Ideal Supply Voltage

277Vac / 2400Vac line-to-neutral

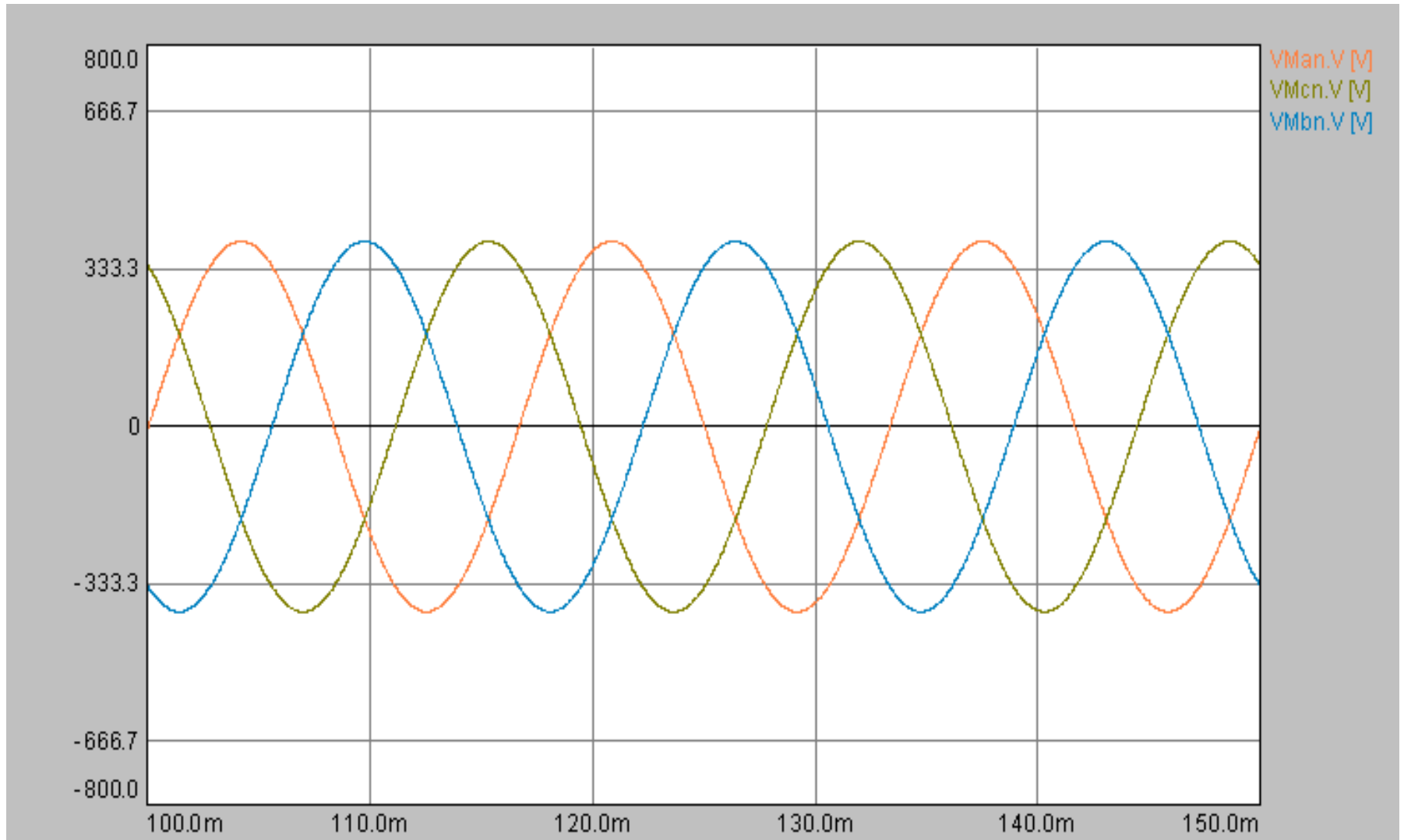

Common Power Quality Problems

- **Too High**
 - Switching in PF caps
 - DC drive transients
 - Switching off inductive loads
- **Too Low**
 - Voltage sags
 - Voltage notches
 - Voltage flat-topping
- **Nothing's There**
 - Voltage interruptions

What have we seen?

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

LAFARGE


Event Number 11

Channel ABC

Setup 14

11/03/99

09:28:13.54

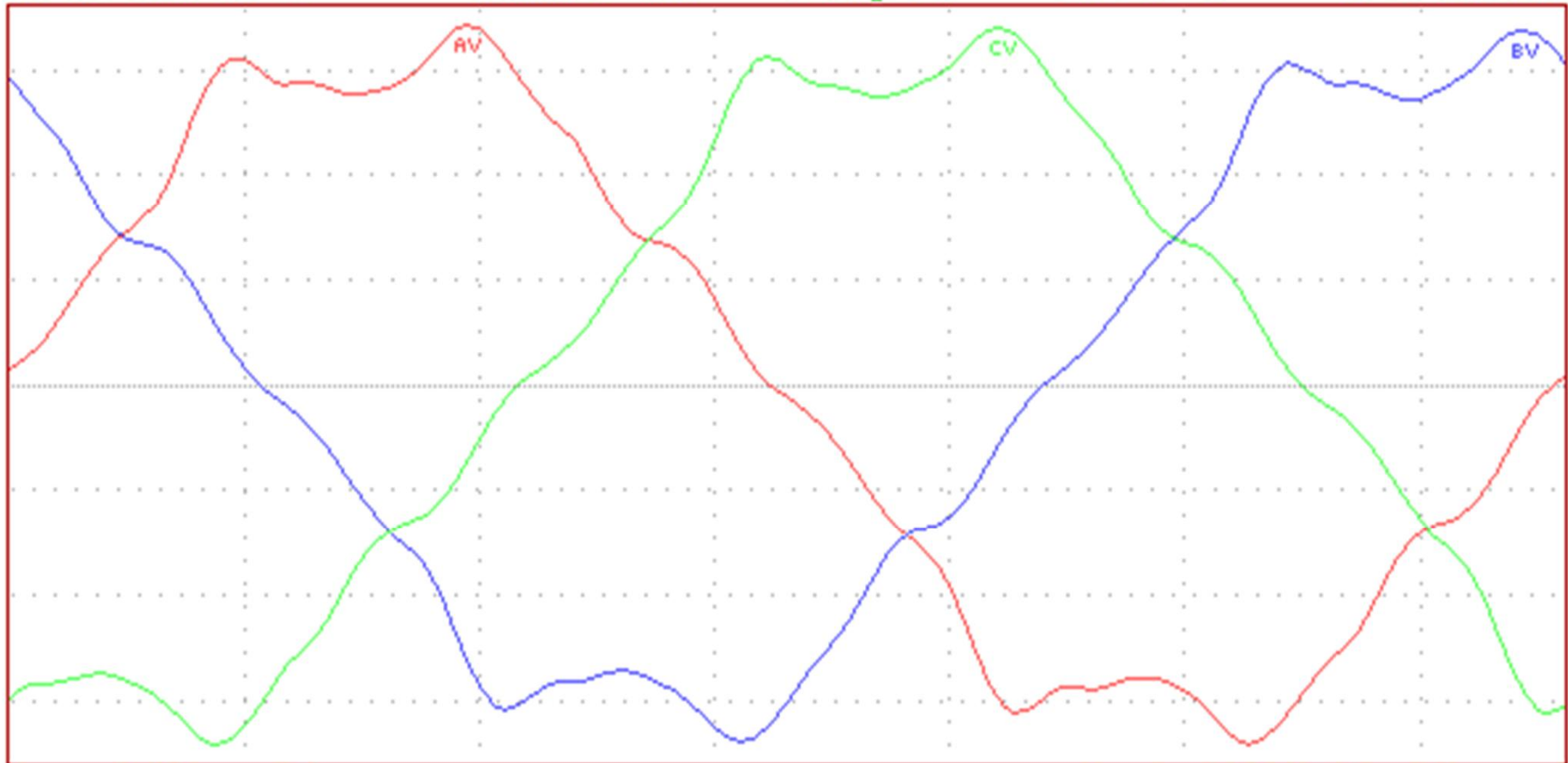

Hor. 2500 μ s/div.

Vert. 200 Volts/div.

Transfer Switch

658 GRAPHICAL & HARMONIC ANALYSIS
FIELDCREST COLUMBUS

(c)1988-1994 Dranetz Technologies, Inc.


Event Number 108

Channel A

Setup 14

11/22/98

03:54:36.98

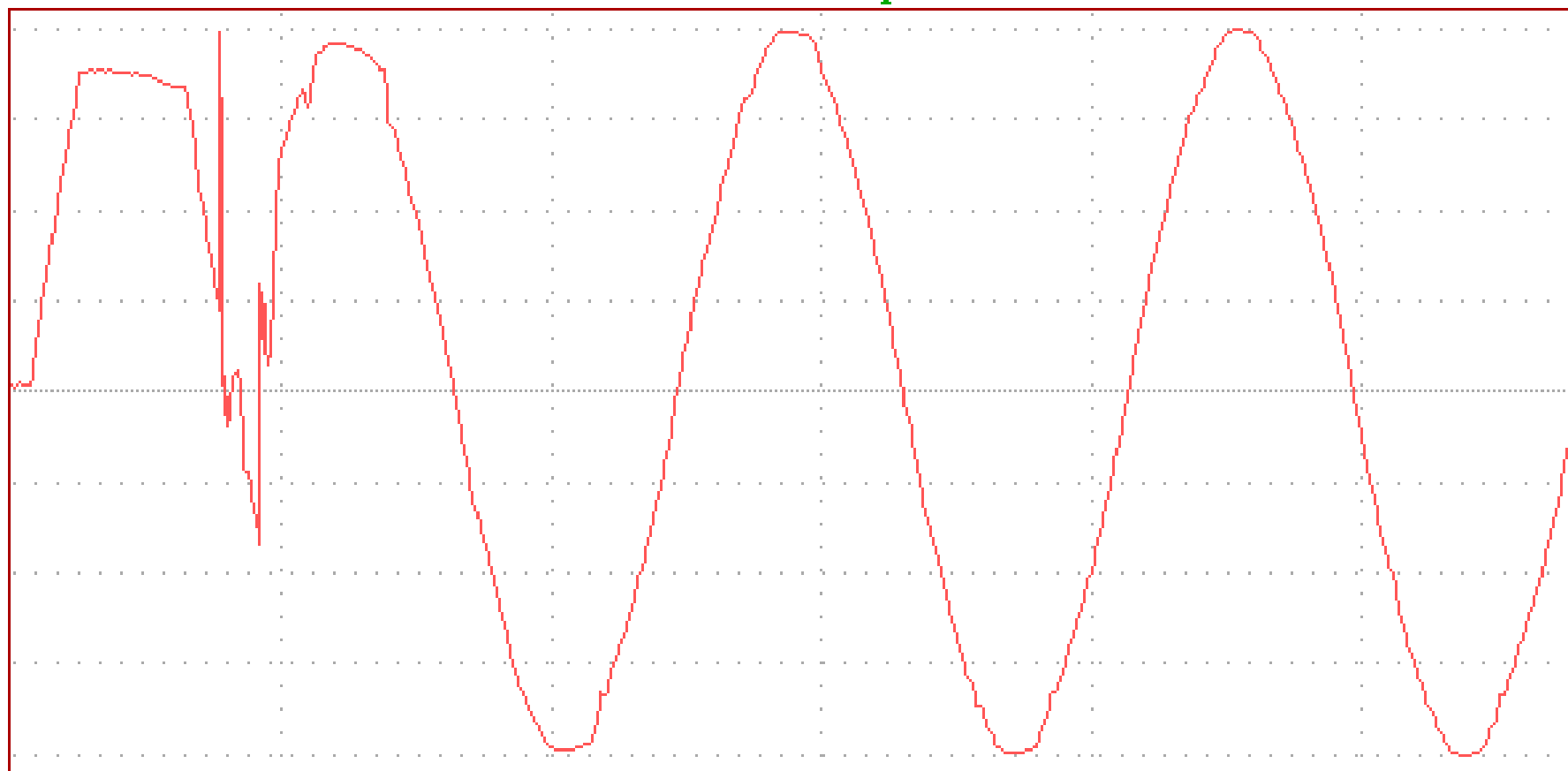

Horizontal 10 milliseconds/division

Vertical 200 Volts/division

Urms: Prev=543.2, Min=548.7, Max=570.4

- Worst Imp= 611 Vpk, 324 deg

Voltage Modulation – AFE w/ Blown Fuse

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988–1994 Dranetz Technologies, Inc.

KC


Event Number 9

Channel ABCD

Setup 1

09/27/00

16:36:53.72

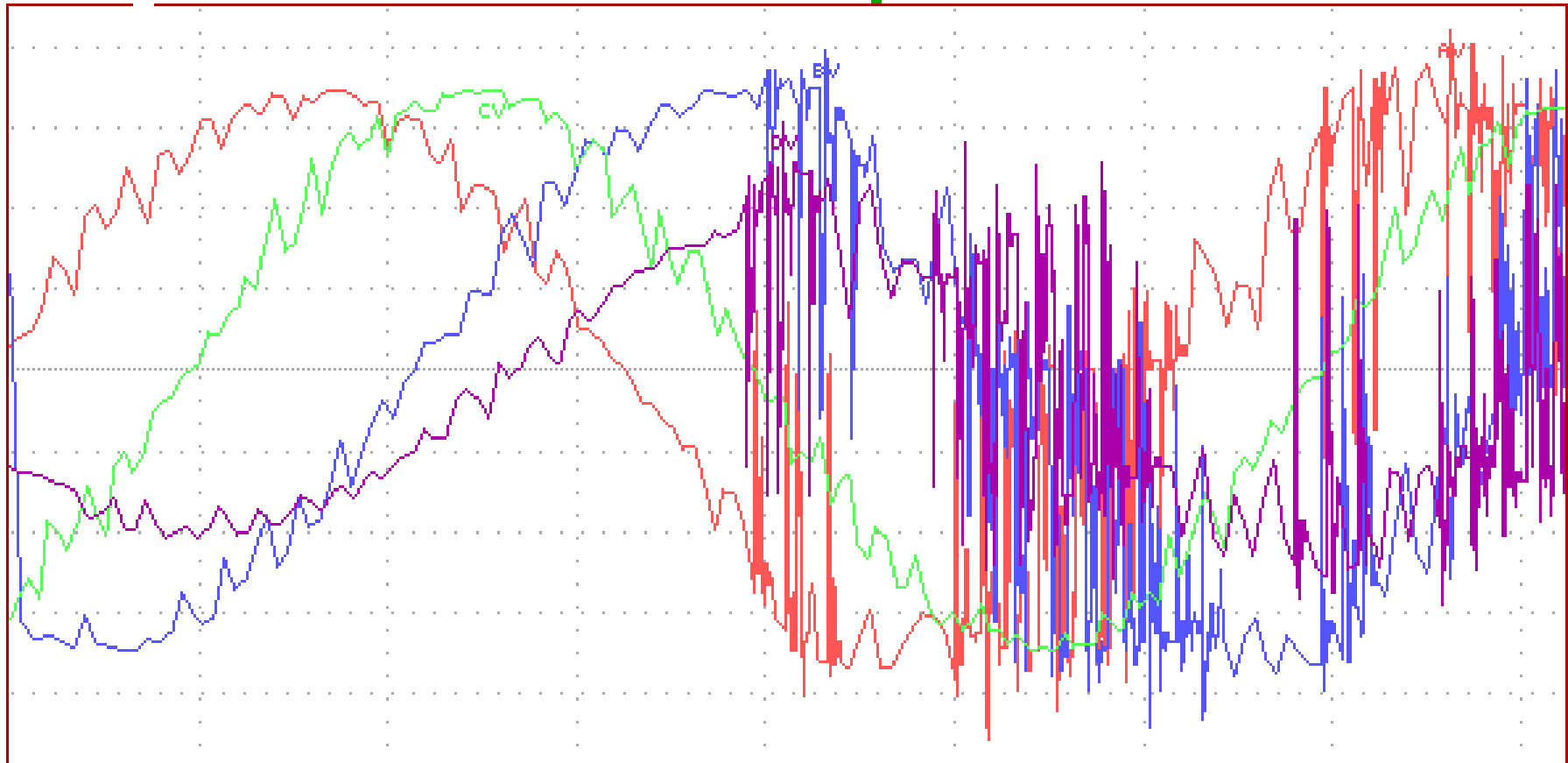

Hor. 2500 $\mu\text{s}/\text{div}$.

Vert. 200 Volts/div.

Example of Load with Ground Fault

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

SCOT


Event Number 211

Channel ABCD

Setup 14

04/12/01

10:21:22.93

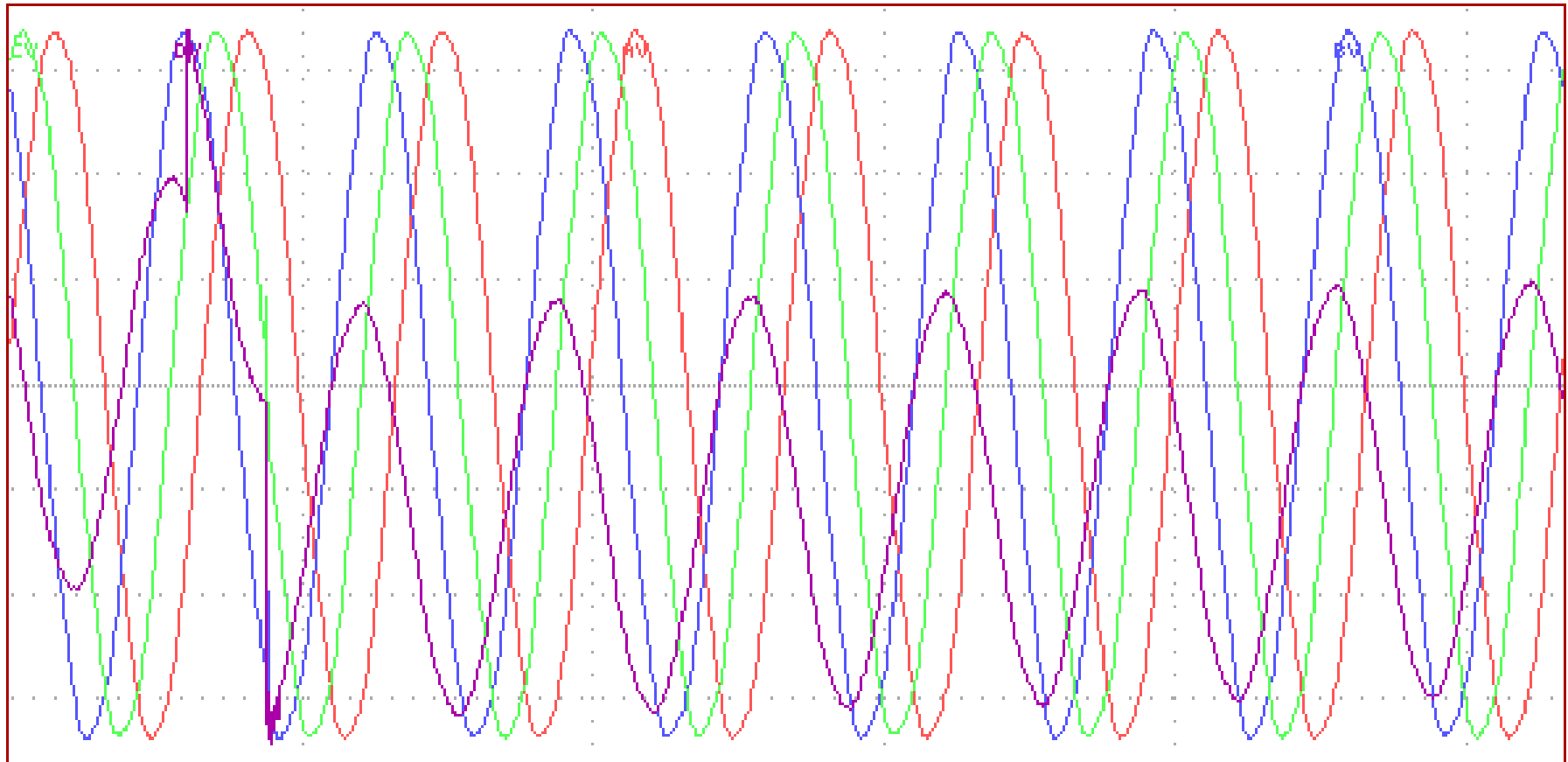

Hor. 25 ms/div.


Vert. 200 Volts/div.

Ungrounded Supply

658 GRAPHICAL & HARMONIC ANALYSIS (c)1988-1994 Dranetz Technologies, Inc.

SCOT

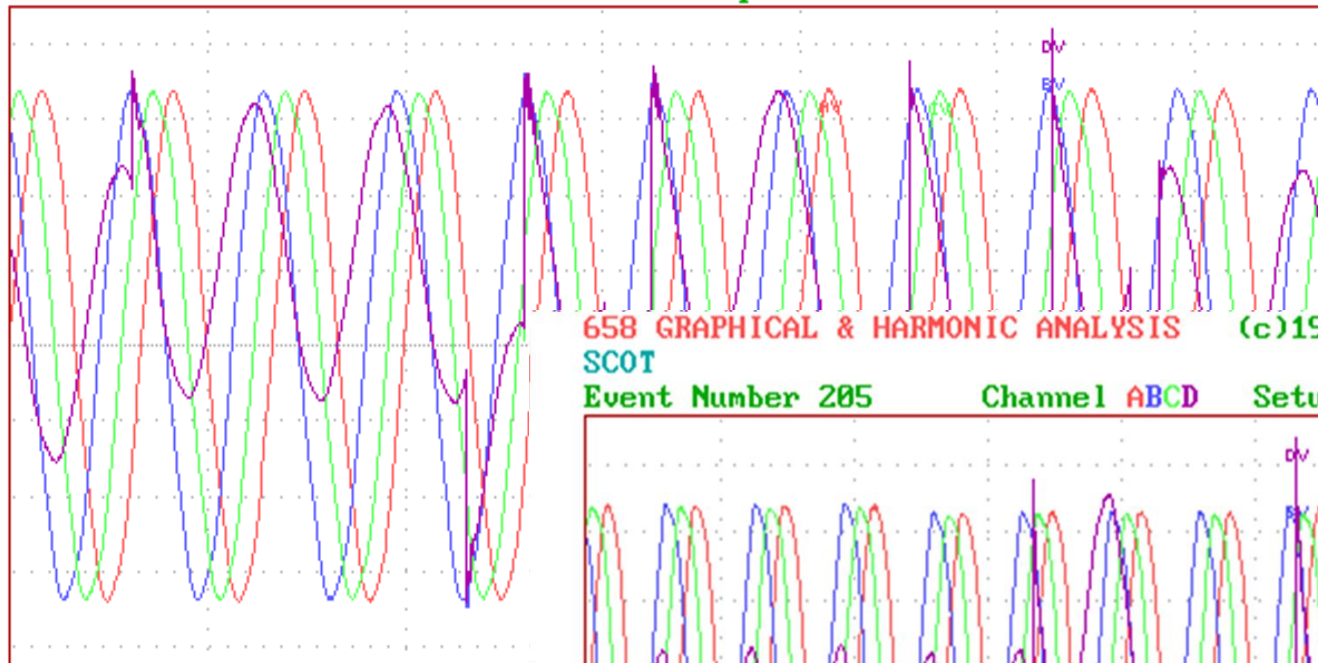Event Number 231 Channel ABCD Setup 14 04/12/01 10:21:23.70




Hor. 25 ms/div.

658 GRAPHICAL & HARMONIC ANALYSIS (c)1988-1994 Dranetz Technologies, Inc.

SCOT

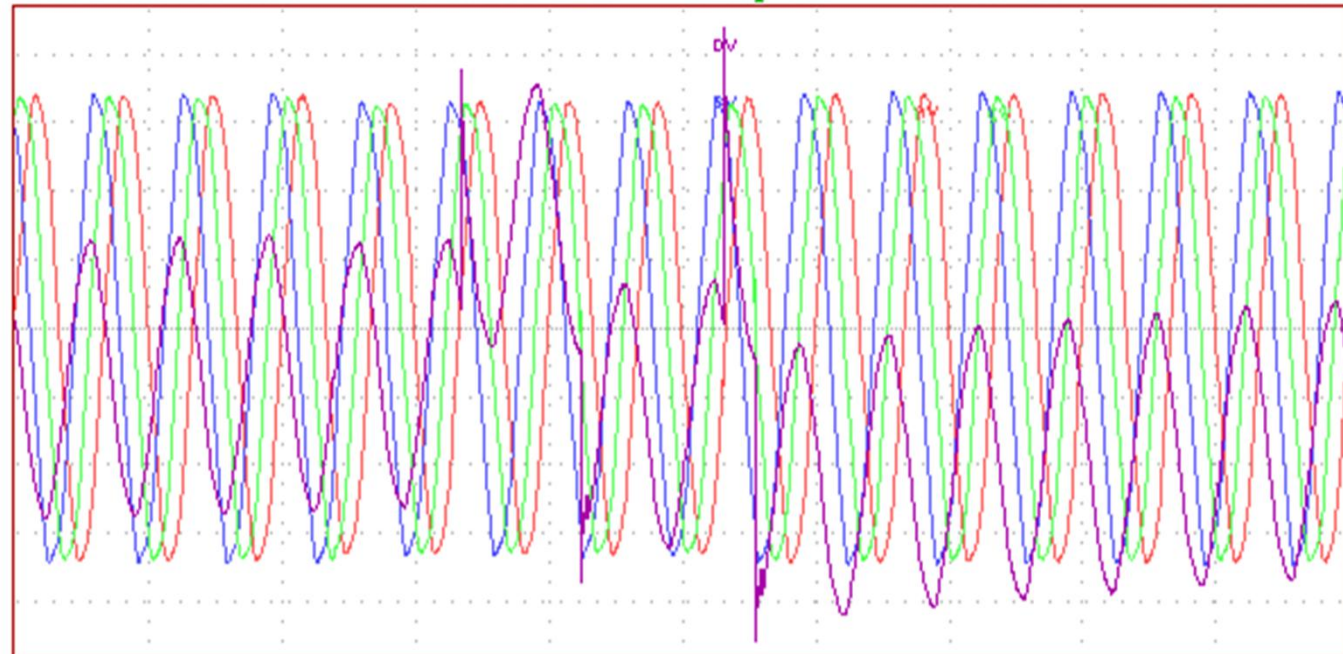Event Number 205 Channel ABCD Setup 14 04/13/01 08:22:07.96



Hor. 25 ms/div.

Vert. 200 Volts/div.

Example of Load with Ground Fault

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

CATERPILLAR AURARA


Event Number 5

Channel ABCD

Setup 16

01/26/04

18:43:50.13

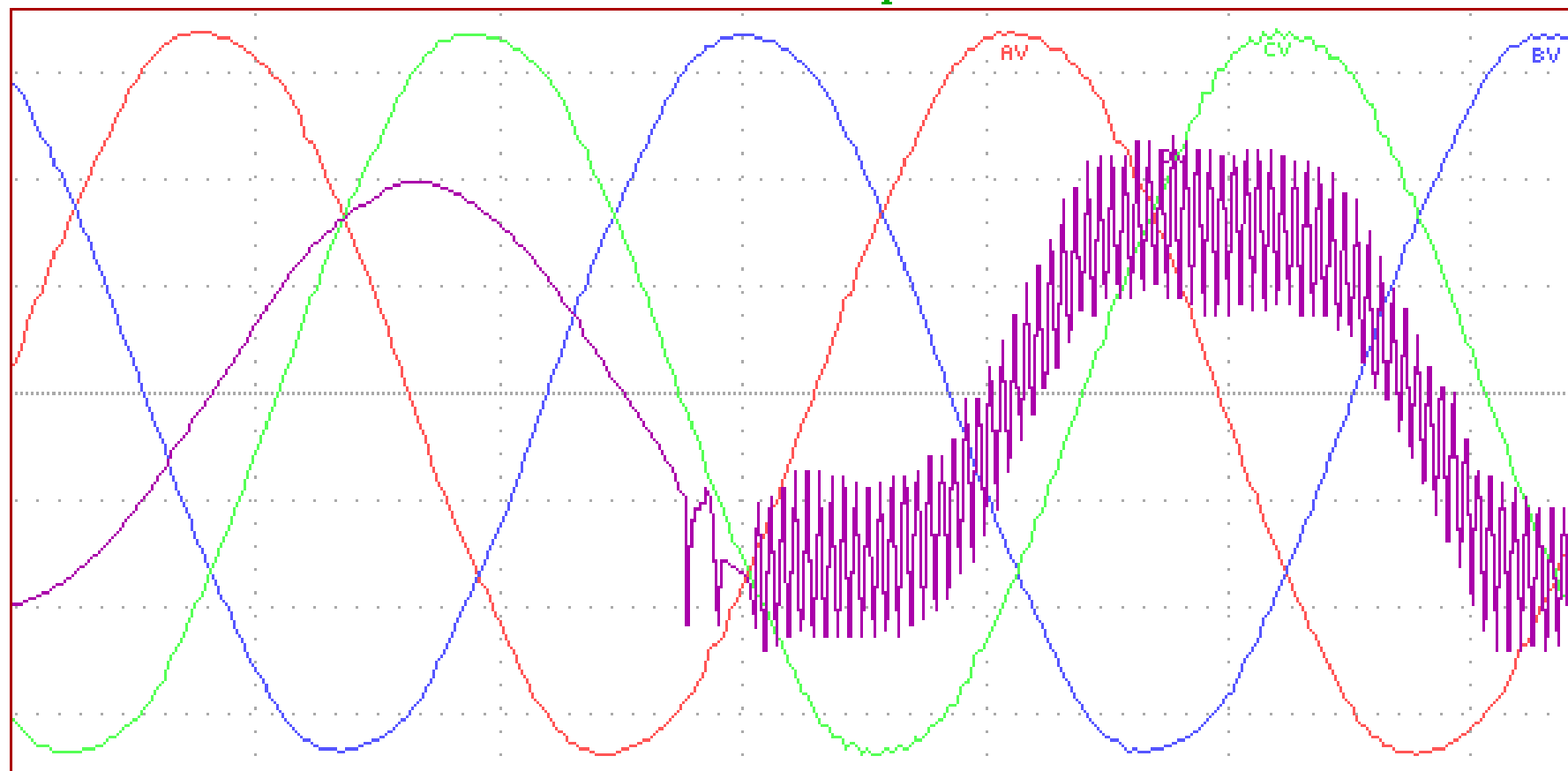

Hor. 5 ns/div.

Vert. 200 Volts/div.

PF Cap Insertion

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

IMERYS


Event Number 7

Channel ABCD

Setup 1

11/02/02

11:47:55.01

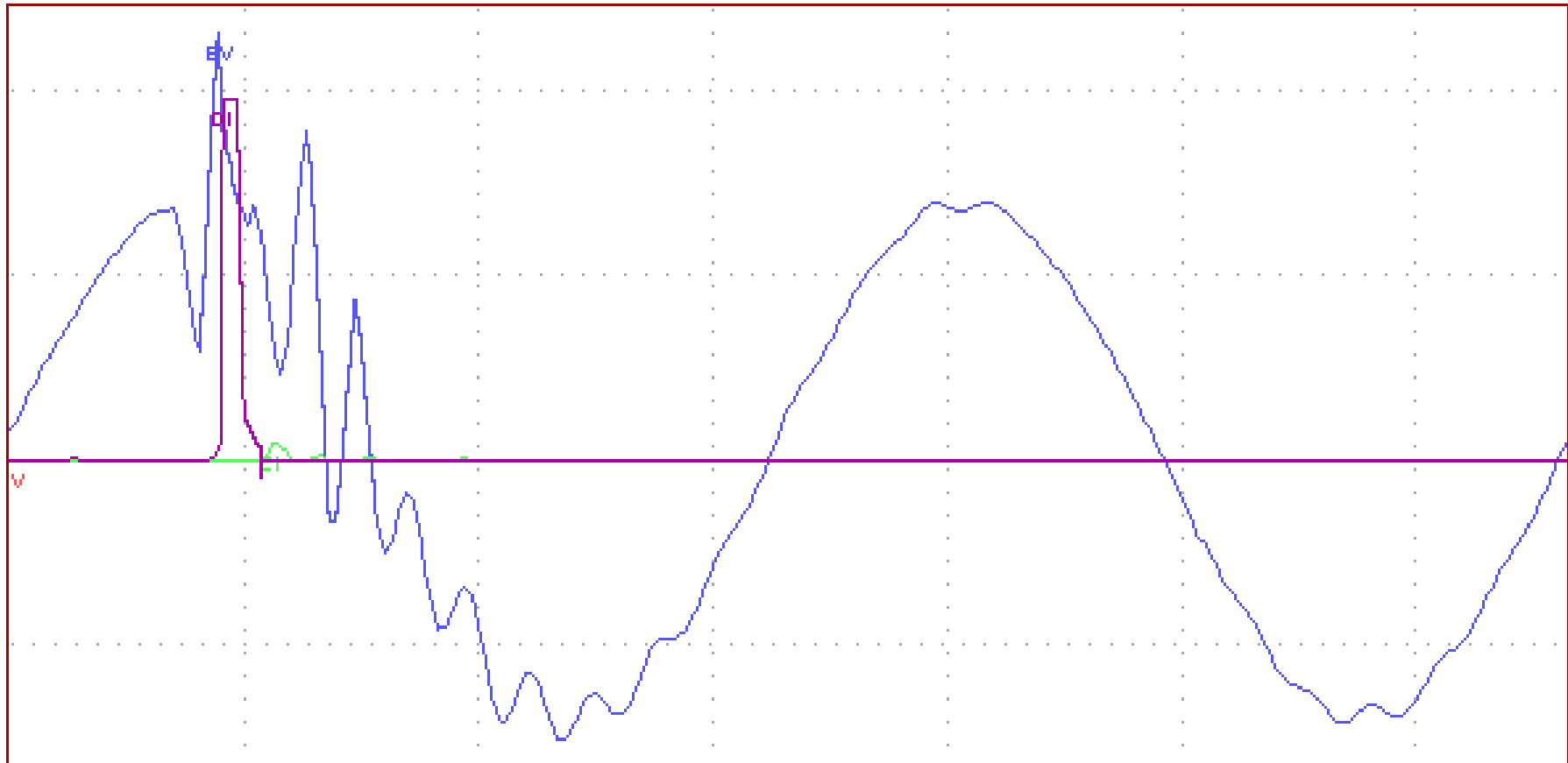

Hor. 5 ms/div.

Vert. 500 Amps/div.

Vert. 500 Volts/div.

PF Cap Insertion

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

MEQUON RTU 6

Event Number 16

Channel B

Setup 2

03/02/00

07:24:55.88



Horizontal 5 milliseconds/division

Vertical 200 Volts/division

Vrms: Prev=466.3, Min=458.0, Max=488.8

Worst Imp= -685 Vpk, 108 deg

Severe Distortion

658 GRAPHICAL & HARMONIC ANALYSIS
NOKOMIS PUMPING STATION

(c)1988-1994 Dranetz Technologies, Inc.


Event Number 29

Channel B

Setup 2

11/17/99

06:28:13.97

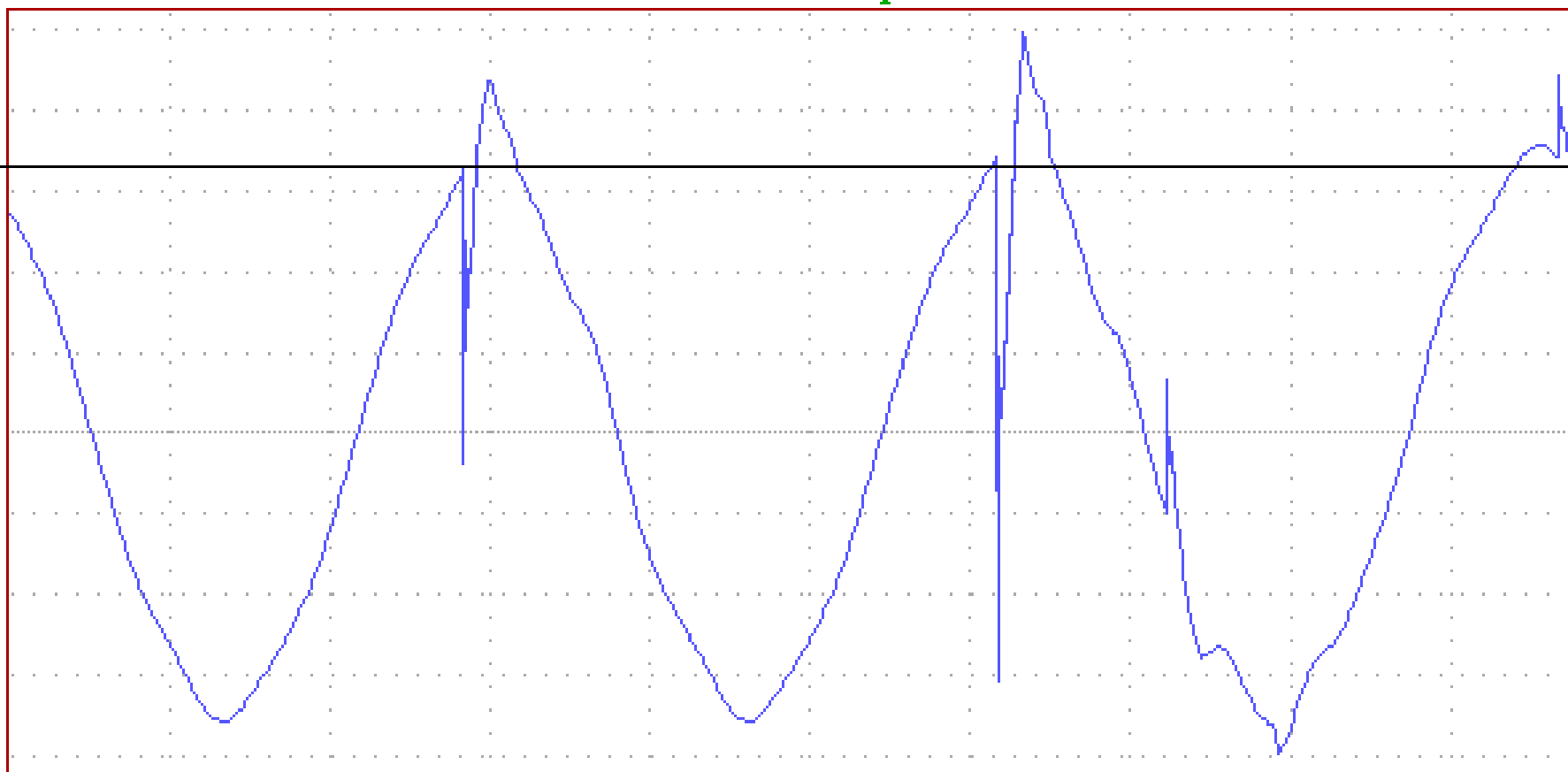

Horizontal 5 milliseconds/division

Vertical 200 Volts/division

Urms: Prev=482.3, Min=492.5, Max=499.7

- Worst Imp= -1307 Vpk, 78 deg

Line-Notching from DC Drive

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Danetz Technologies, Inc.

Event Number 9

Channel ABC

Setup 1


02/26/96

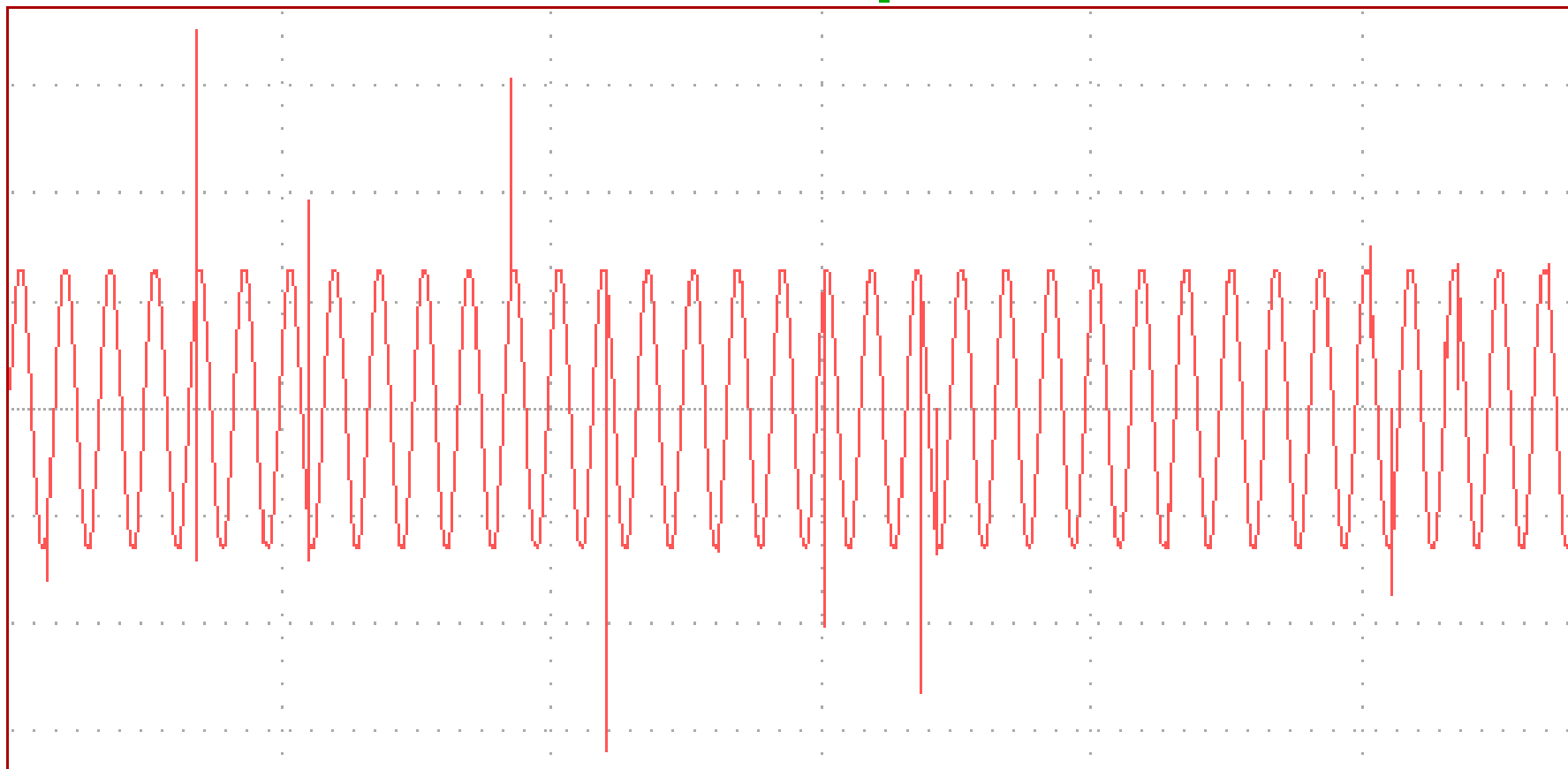14:45:33.70



Voltage Transients – Inductive Load Switching?


658 GRAPHICAL & HARMONIC ANALYSIS (c)1988–1994 Dranetz Technologies, Inc.
A.BUSH HSTN 64 FULL CAN TWO 1305 VLL
Event Number 8 Channel A Setup 14 11/02/98 12:22:30.35



Horizontal 100 milliseconds/division Vertical 500 Volts/division
Urms: Prev=463.2, Min=461.2, Max=465.1 - Worst Imp= -2213 Vpk, 111 deg

Single Notch

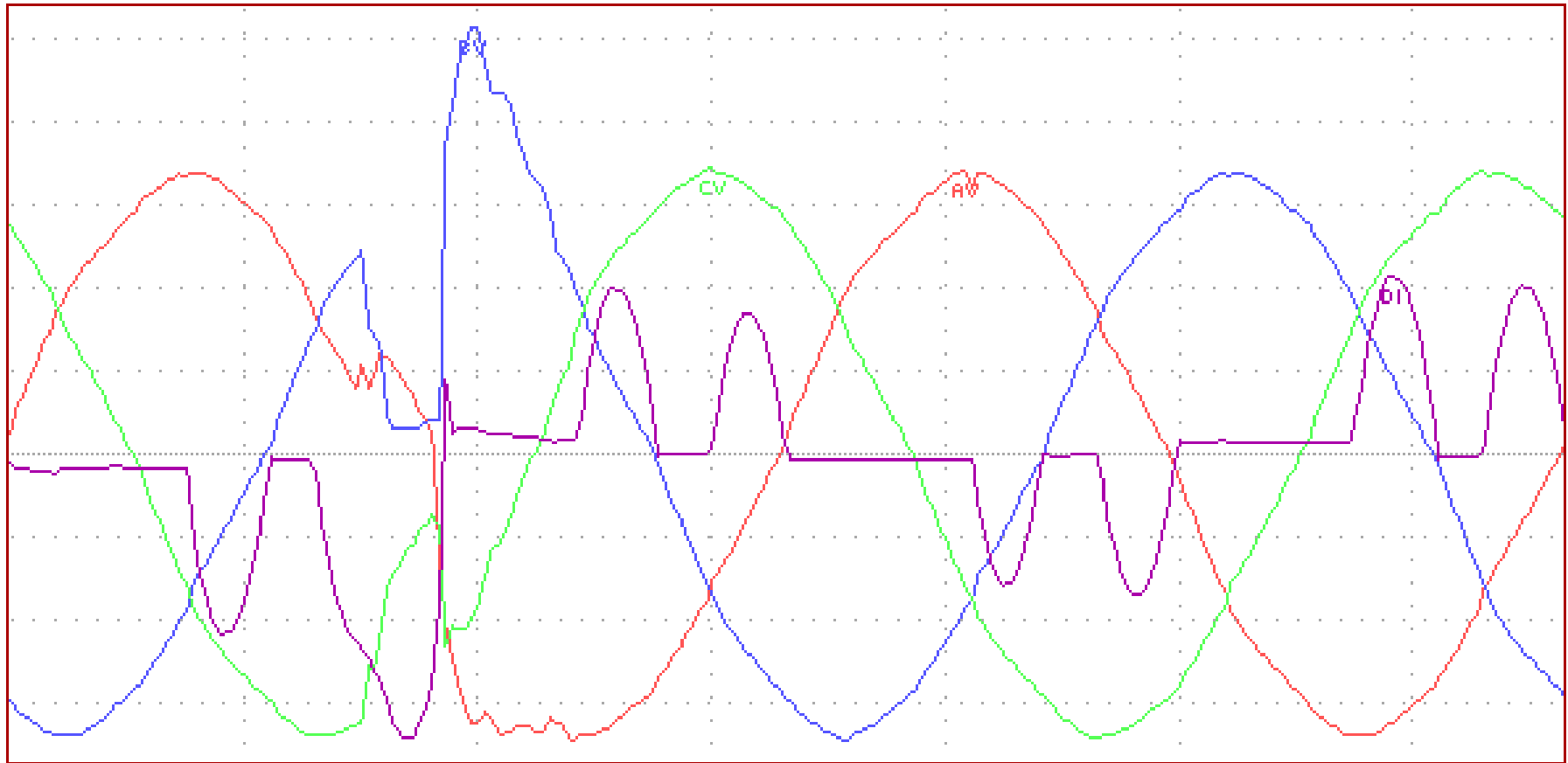658 GRAPHICAL & HARMONIC ANALYSIS (c)1988-1994 Dranetz Technologies, Inc.
DRANETZ 658 Power Quality Analyzer
Event Number 14 Channel ABCD Setup 5 01/08/01 05:12:23.28



Hor. 5 ms/div.

Vert. 20 Amps/div.

Vert. 200 Volts/div.

Voltage Sag

658 GRAPHICAL & HARMONIC ANALYSIS

(c)1988-1994 Dranetz Technologies, Inc.

TUCSON RECLAIM JOCKEY PUMP

Event Number 266

Channel A

Setup 14

02/24/98

13:27:39.32



Horizontal 25 milliseconds/division

Vertical 200 Volts/division

Urms: Prev=492.3, Min=310.6, Max=485.3

Worst Imp= 0 Vpk, 0 deg

Voltage Interruption

658 GRAPHICAL & HARMONIC ANALYSIS
FIELDCREST COLUMBUS

(c)1988-1994 Dranetz Technologies, Inc.


Event Number 22

Channel A

Setup 14

11/20/98

06:46:43.51

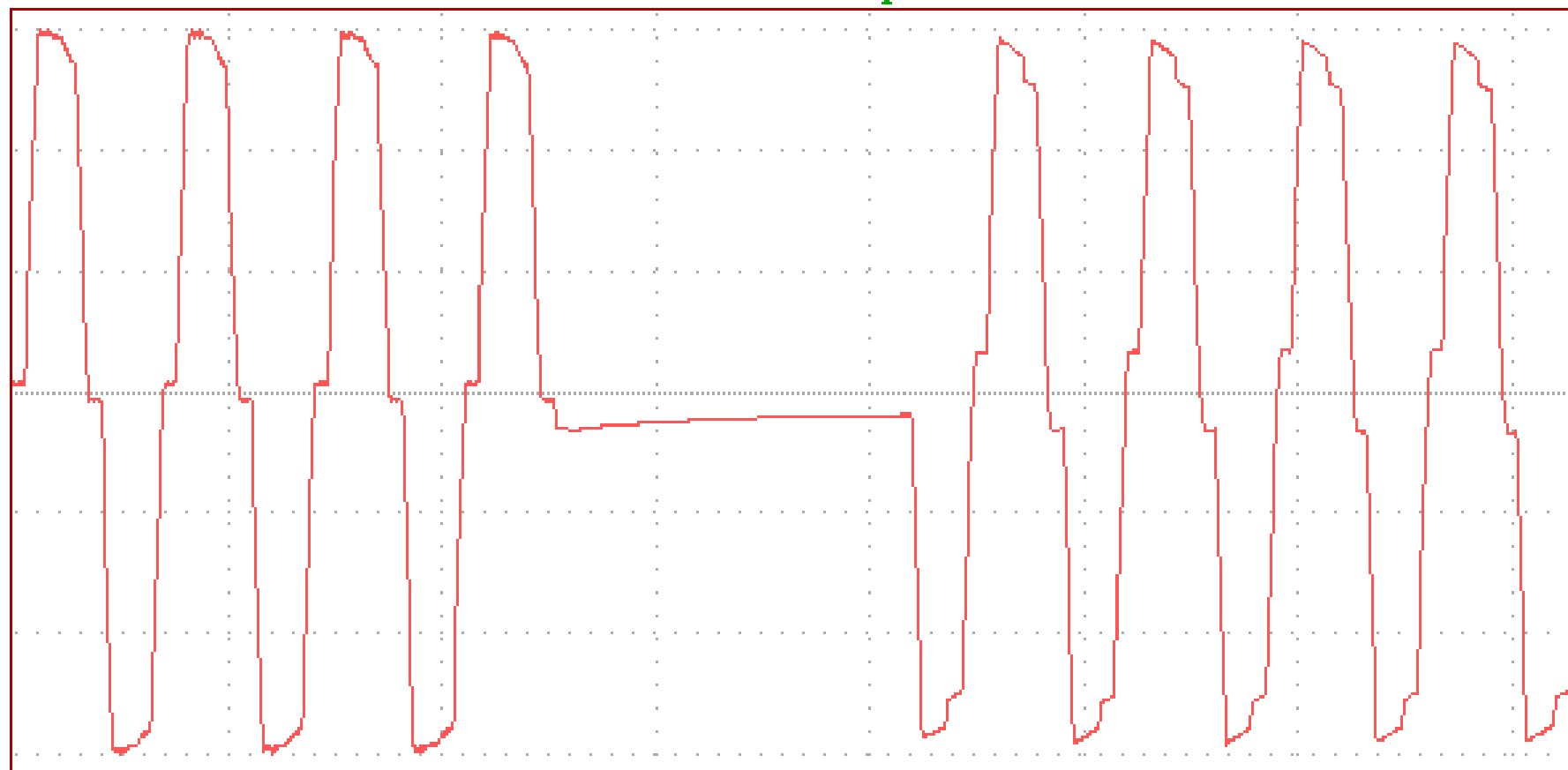

Horizontal 25 milliseconds/division

Vertical 200 Volts/division


Vrms: Prev=452.2, Min=431.7, Max=453.8

- Worst Imp= 0 Vpk, 0 deg

Analysis Rules-of-Thumb

- **Rule #1 = measurements and plots**
 - Don't rely on meter measurements alone
 - Obtain waveform plots in addition to measurements
- **Rule #2 = each phase to everything else**
 - Take Voltage measurements and plots each line-to-line
 - Take Voltage measurements and plots each line-to-neutral
 - Take Voltage measurements and plots neutral-to-ground
 - Take Current measurements and plots in each line and neutral
 - Not just line-to-ground and not just line-to-line: BOTH

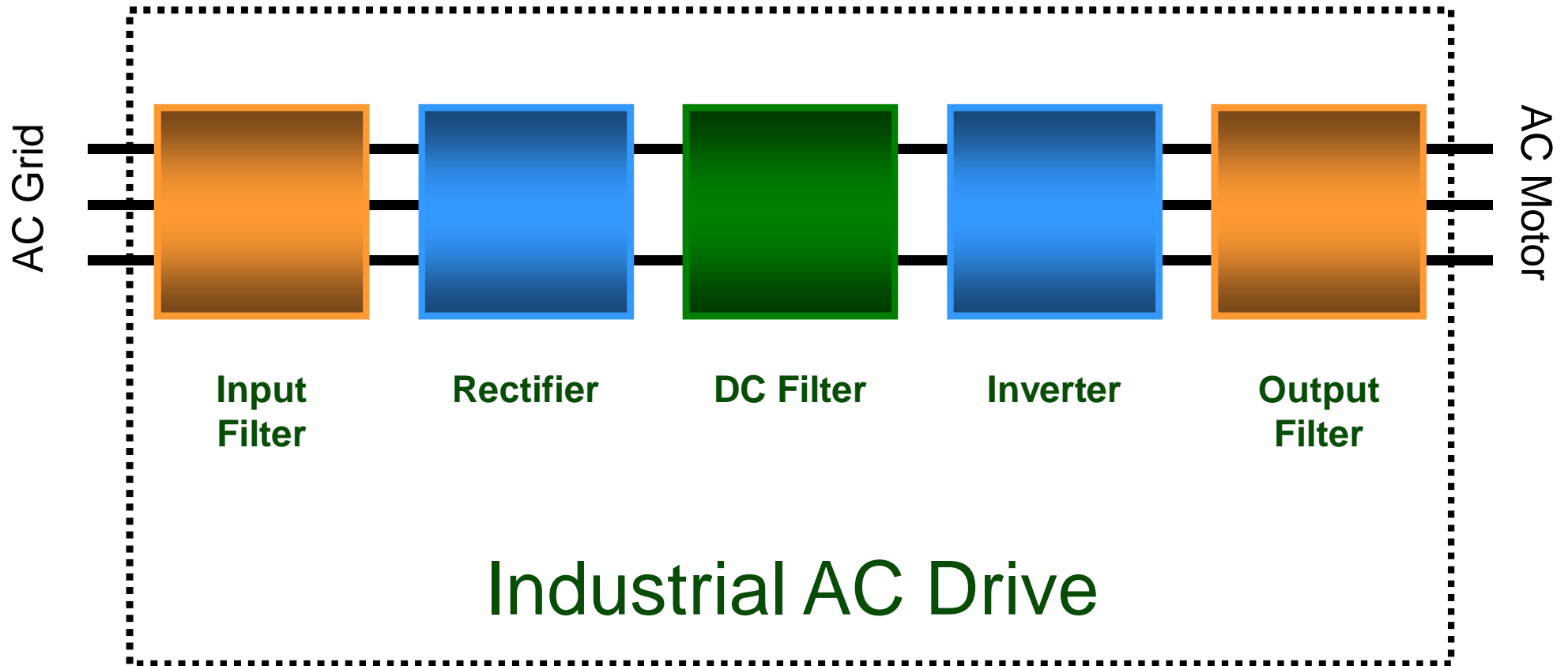General Block Diagram of an Industrial AC Drive




What's Unique to High Power Drives?

- Higher Power
 - Usually major part of operation at a plant
 - Reliability is critical
 - More internal monitoring
 - Greater protective features
- Line side
 - Transformer is expensive
 - Protection is critical
 - Line harmonics can be significant
- Motor side
 - Motor is expensive
 - Protection is critical
 - Reflected Waves


Line Side Requirements

- Harmonics
- Power Factor
- Grounding Configuration


What are Harmonics?

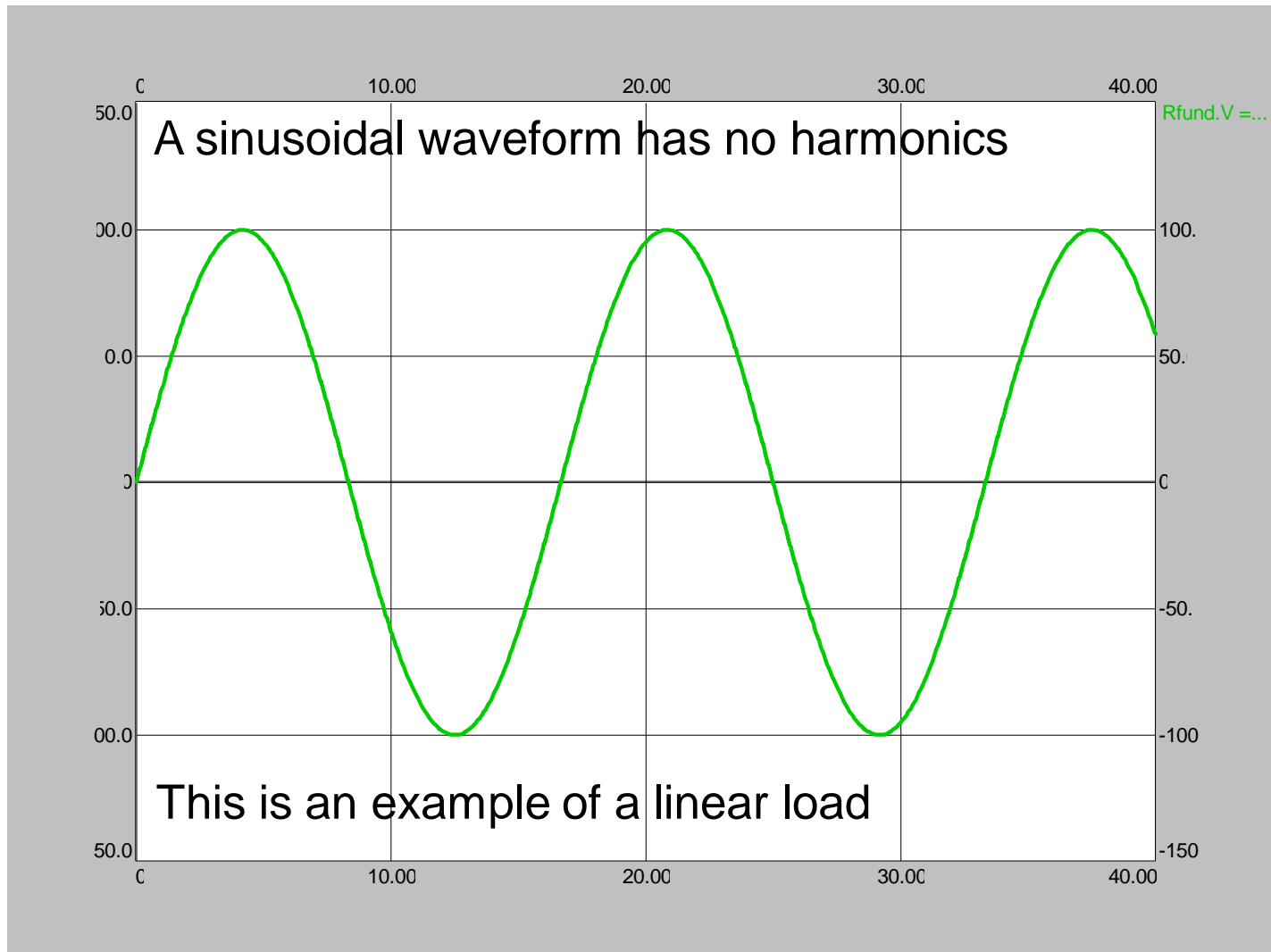

What are Harmonics?

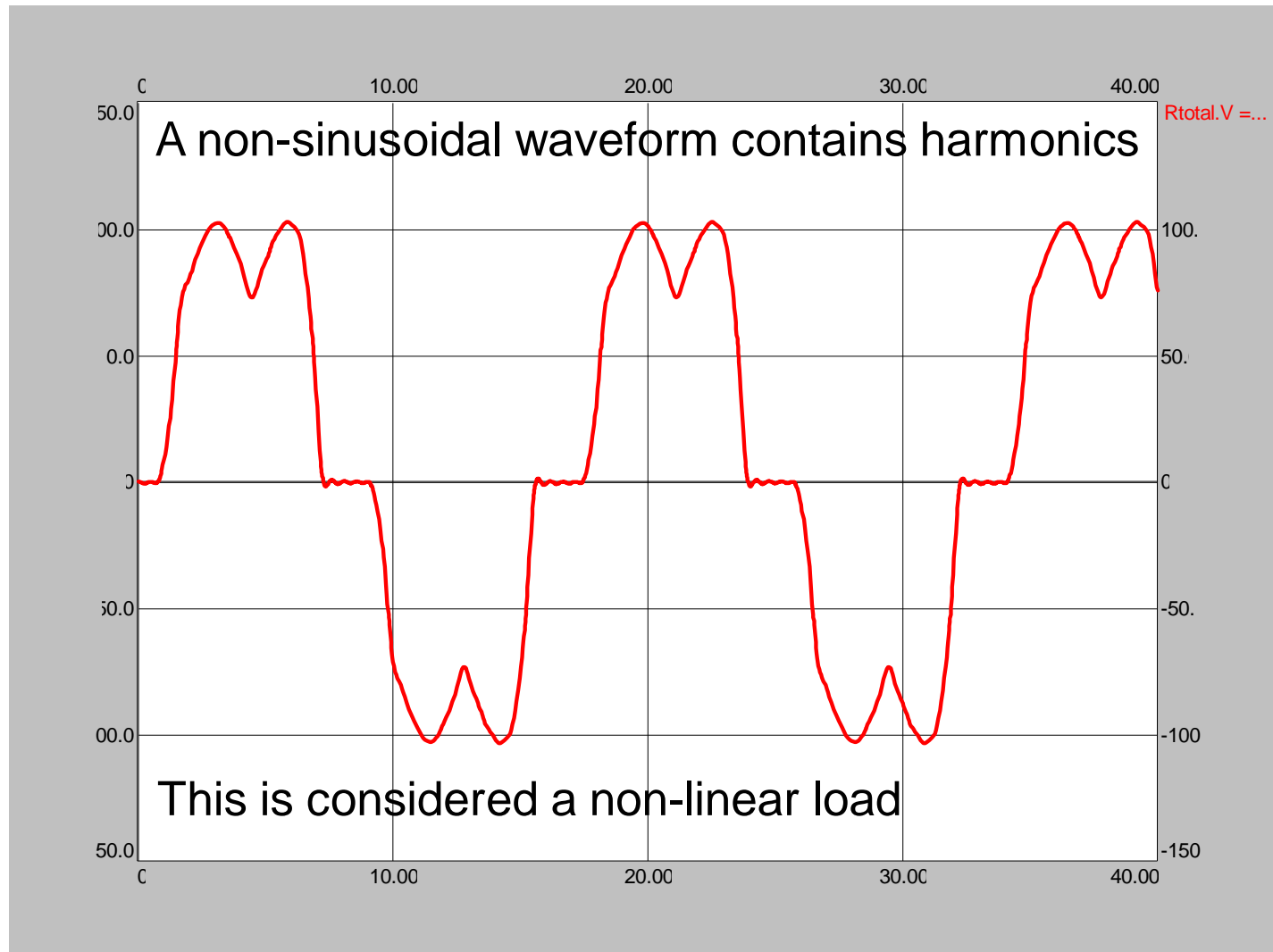

Total, Fundamental, Harmonic Current

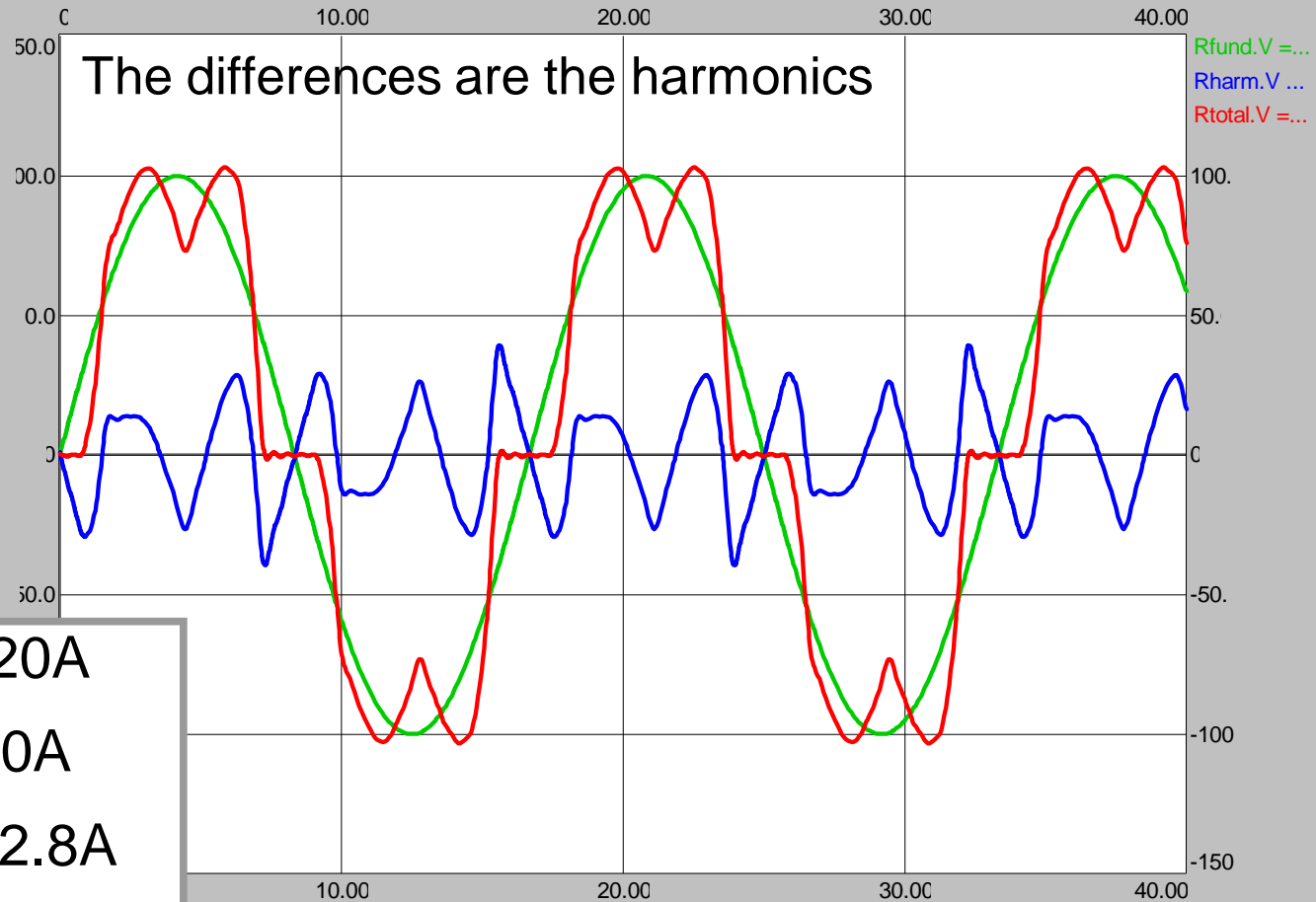

$I_{\text{harm}} = 20\text{A}$

$I_{\text{fund}} = 70\text{A}$

$I_{\text{total}} = 72.8\text{A}$

$I(\text{THD}) = 28\%$

Root Cause of Problems with Other Equipment


Current Harmonics

create

Voltage Distortion

Flat-Topping the Voltage

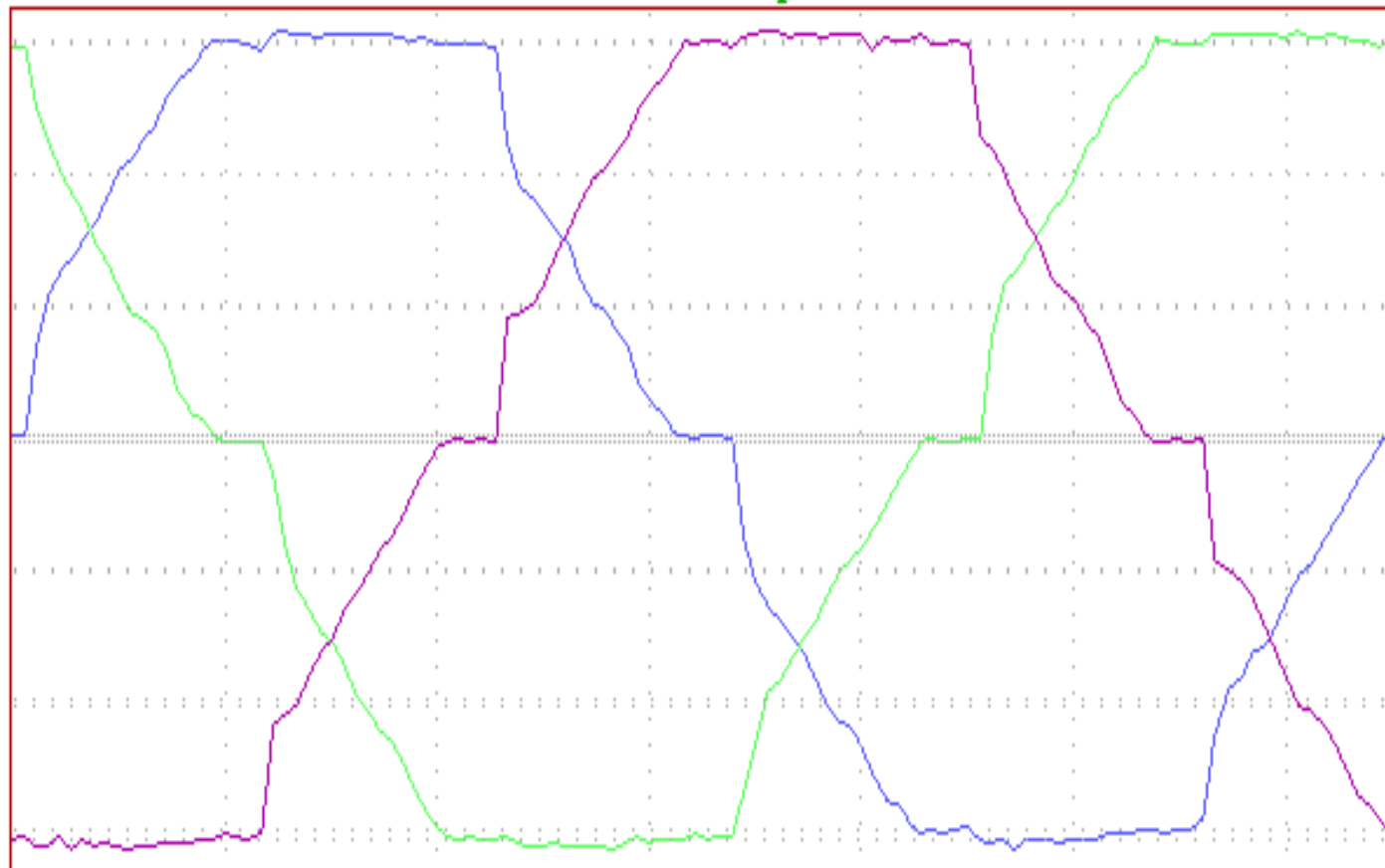658 GRAPHICAL & HARMONIC ANALYSIS (c)1988-1994 Dranetz Technologies, Inc.
DRANETZ 658 Power Quality Analyzer
Event Number 1 Channel BCD Setup 14 06/11/98 11:18:15.06



Horizontal 2500 microseconds/division Vertical 200 Volts/division
Urms: Prev=0.000, Min=458.0, Max=458.0 - Worst Imp= 0 Vpk, 0 deg

What are the IEEE 519-1992 standards?

Harmonic Voltage Limits		Table 10.2
Low-Voltage Systems		
Application	Maximum THD (%)	
Special Applications - hospitals and airports	3.0%	
General System	5.0%	
Dedicated System - exclusively converter load	10.0%	

Current distortion Limits for General Distribution Systems (120V through 69,000V)						
Maximum Harmonic Current Distortion in Percent of Iload						
Isc/Iload	<11	11<=h<17	17<=h<23	23<=h<35	35<=h	TDD (%)
<20	4.0	2.0	1.5	0.6	0.3	5.0
20<50	7.0	3.5	2.5	1.0	0.5	8.0
50<100	10.0	4.5	4.0	1.5	0.7	12.0
100<1000	12.0	5.5	5.0	2.0	1.0	15.0
>1000	15.0	7.0	6.0	2.5	1.4	20.0
Even harmonics are limited to 25% of the odd harmonic limits above						
						Table 10.3
Isc=maximum short circuit current at PCC						
Iload=maximum demand load current (fundamental frequency component) at PCC						

What are the IEEE 519-1992 standards?

Harmonic Voltage Limits		Table 11.1
Medium-Voltage Systems ($\leq 69\text{kV}$)		
Voltage Distortion	Maximum THD (%)	
Individual Harmonic Distortion	3.0%	
Total Harmonic Distortion	5.0%	

Current distortion Limits for General Distribution Systems (120V through 69,000V)						
Maximum Harmonic Current Distortion in Percent of Iload						
Isc/Iload	<11	11\leqh<17	17\leqh<23	23\leqh<35	35\leqh	TDD (%)
<20	4.0	2.0	1.5	0.6	0.3	5.0
20<50	7.0	3.5	2.5	1.0	0.5	8.0
50<100	10.0	4.5	4.0	1.5	0.7	12.0
100<1000	12.0	5.5	5.0	2.0	1.0	15.0
>1000	15.0	7.0	6.0	2.5	1.4	20.0
Even harmonics are limited to 25% of the odd harmonic limits above						
						Table 10.3
Isc =maximum short circuit current at PCC						
Iload =maximum demand load current (fundamental frequency component) at PCC						


Where is the PCC?

For an Harmonic Study:

Need to calculate and measure the voltage and current magnitudes and distortion at each of the 6 locations (PCCs) noted.


Need to know types of loads, max loads and impedances.

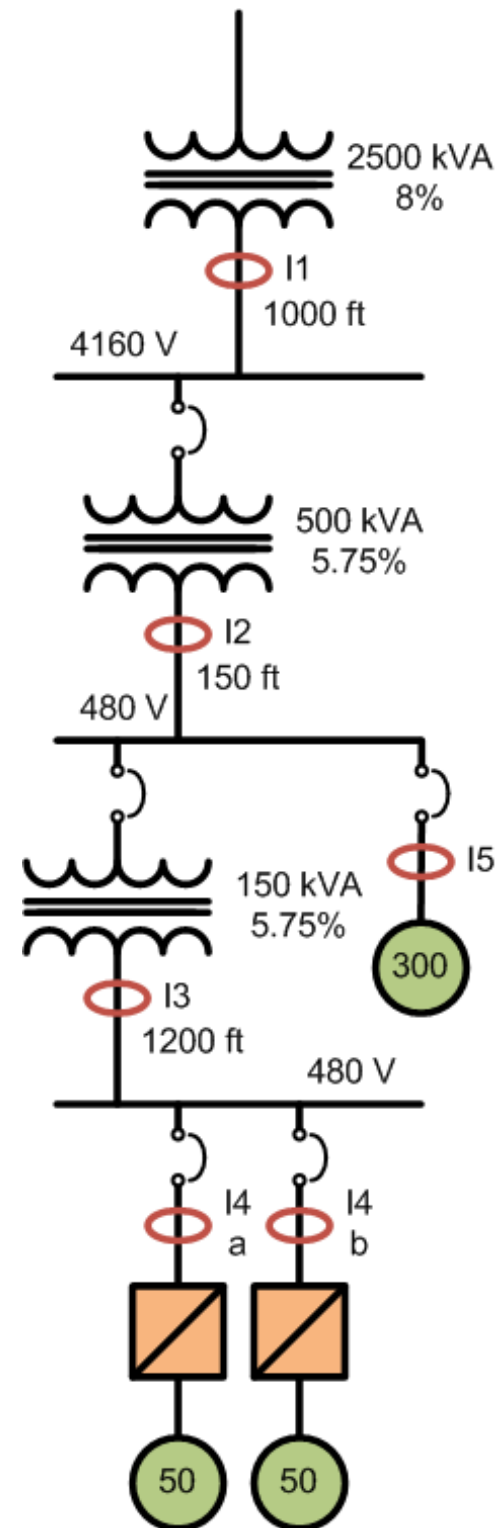Need to know if there are back-up generators, too.




Basic AC Drive Topology

6-Pulse Rectifier

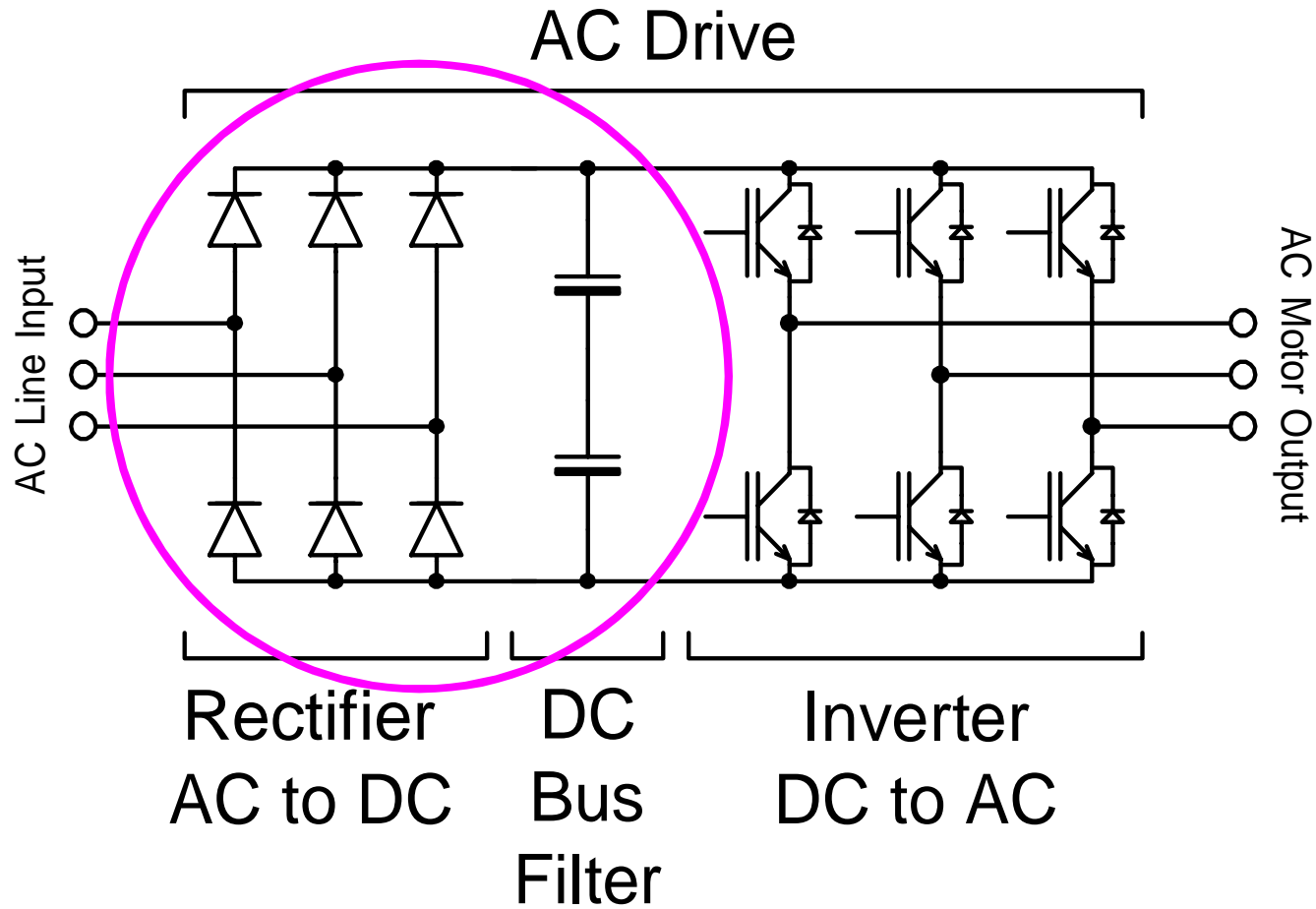


Line Current Harmonic Mitigation Methods


6-Pulse ($120^\circ/2 = 60^\circ$)

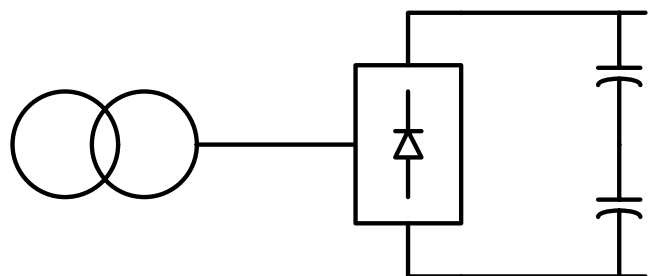


Basic Converter

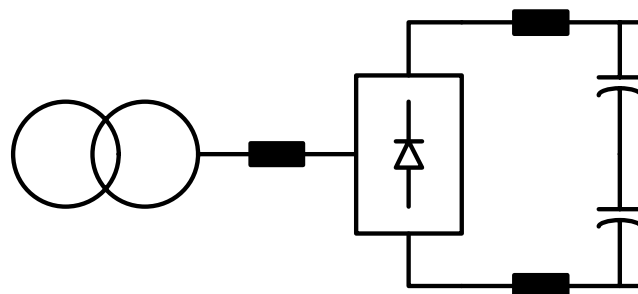


Link Choke and Reactor

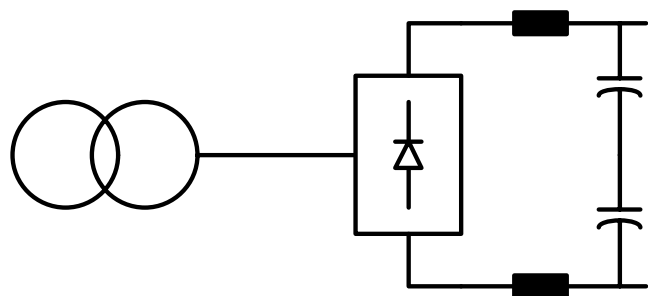


DC Link Chokes

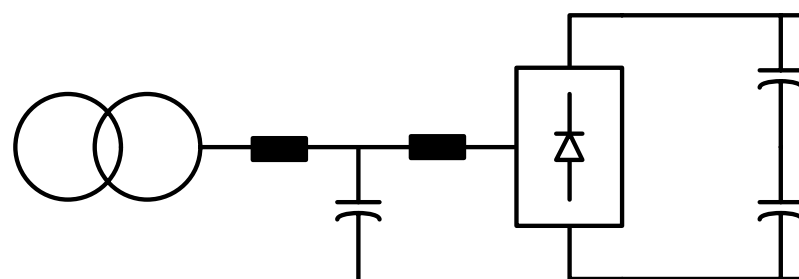

Passive Harmonic Filter

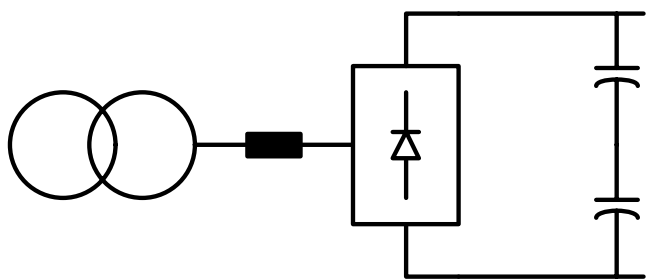


AC Line Reactor

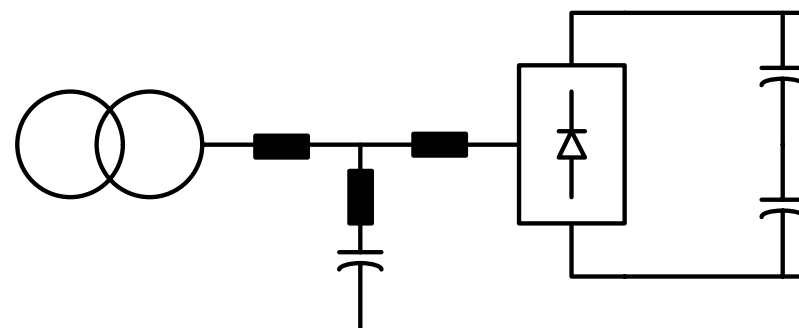

Passive Notch Filter

Line Current Harmonic Mitigation Methods

6-Pulse

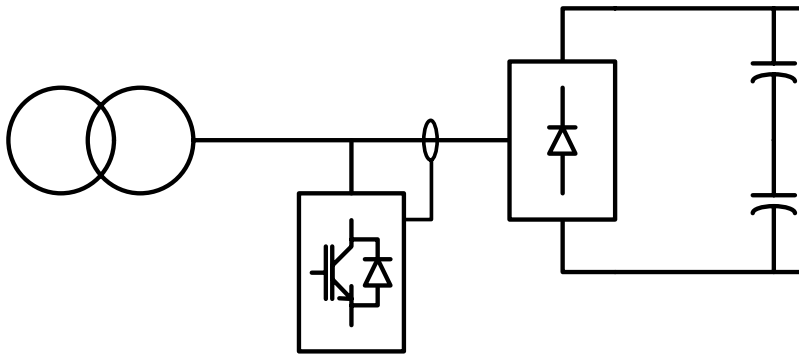


Active Harmonic Filter


Line Current Harmonic Mitigation Methods

12-Pulse (30°)


* Used in MV drives

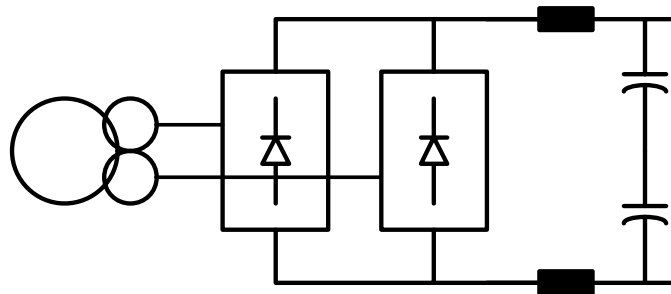


Parallel Bridges

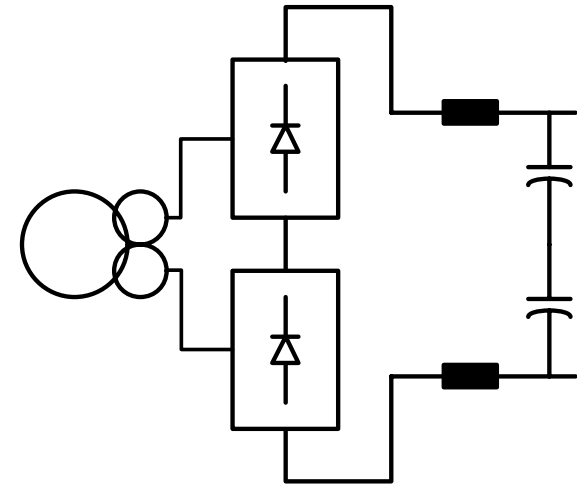

*Series Bridges

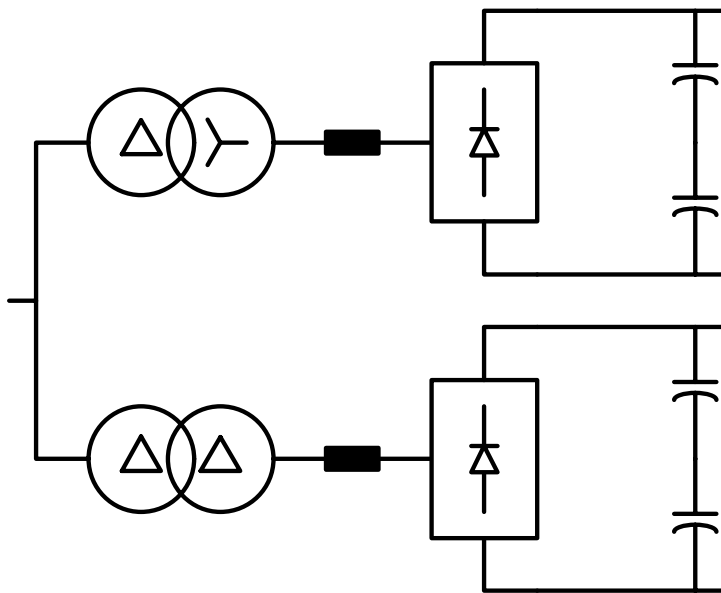

Pseudo 12-Pulse

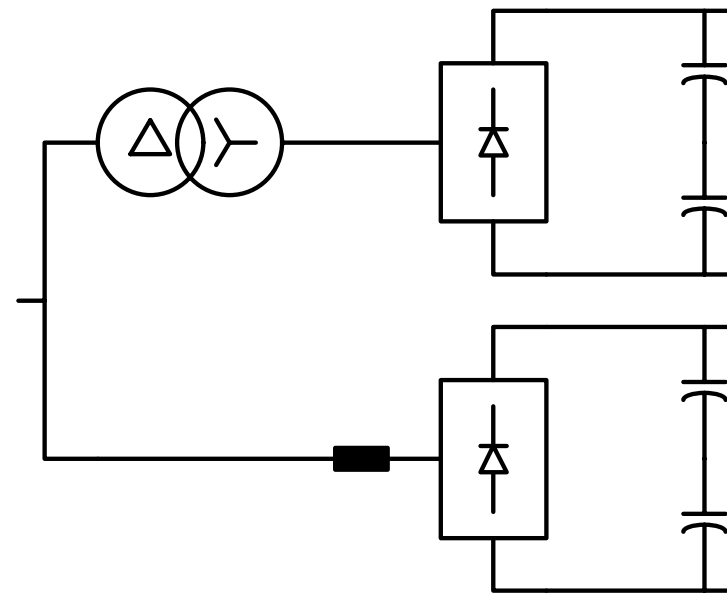


Poor-Man's 12-Pulse


Line Current Harmonic Mitigation Methods

18-Pulse (20°)


* Used in MV drives

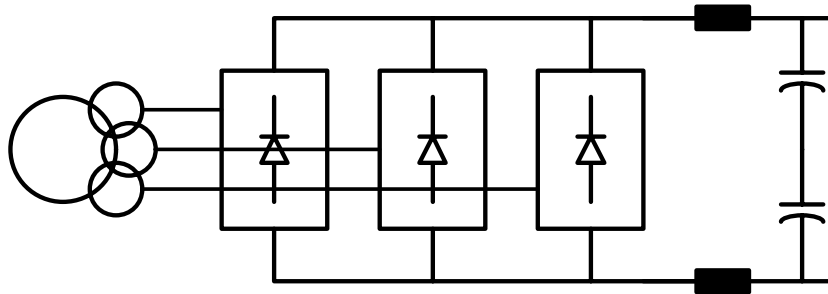

Parallel Bridges

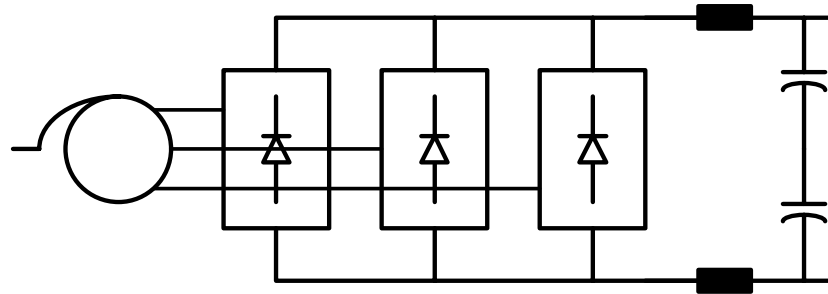

Auto-Transformer with Parallel Bridges

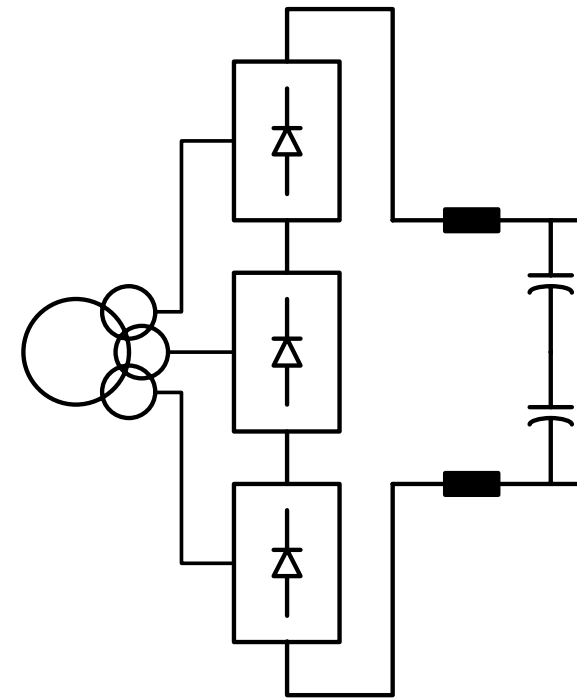


*Series Bridges


Line Current Harmonic Mitigation Methods

24-Pulse (15°), 36-Pulse (10°)

* Used in MV drives

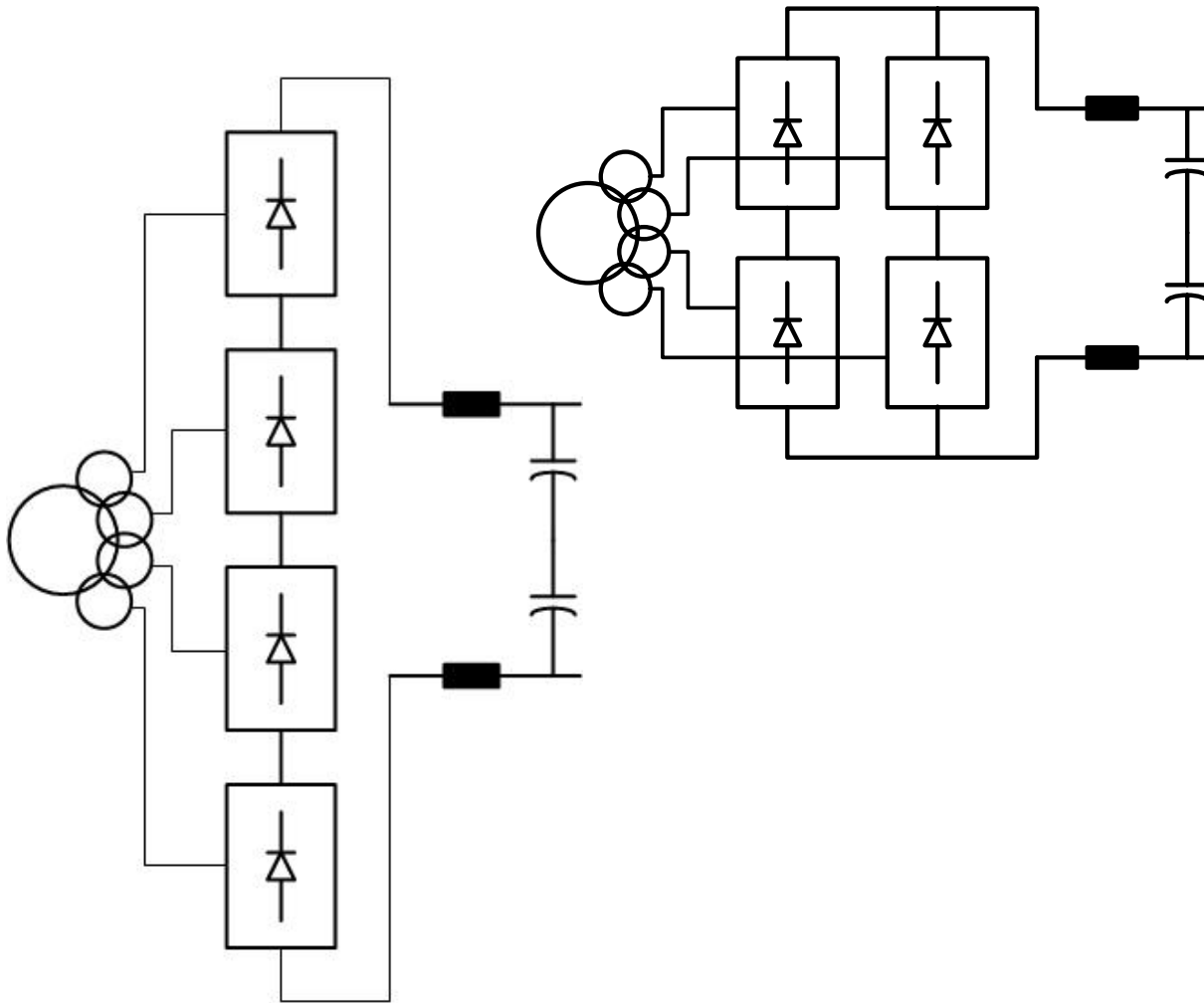

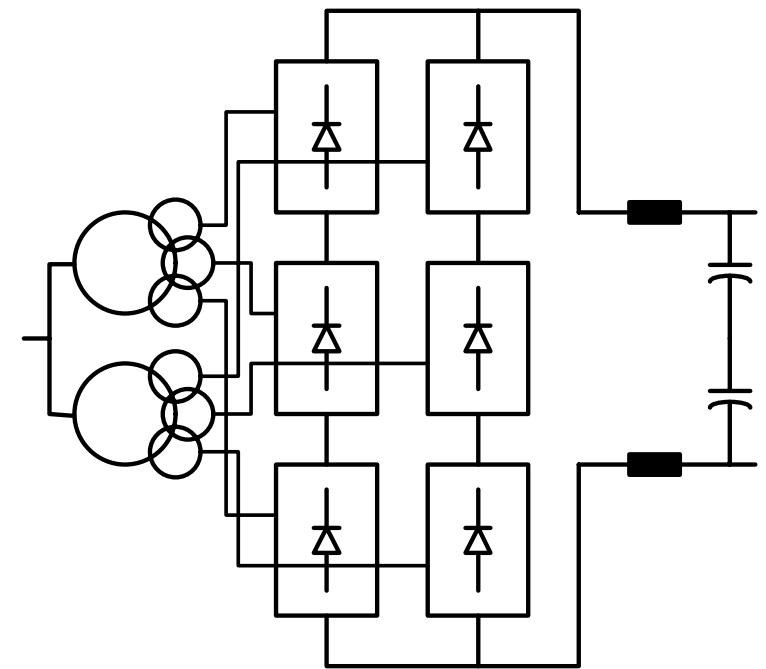
*Series or Series / Parallel Bridges, 24P



*Series / Parallel Bridges, 36P

Line Current Harmonic Mitigation Methods


Active Front End (AFE)

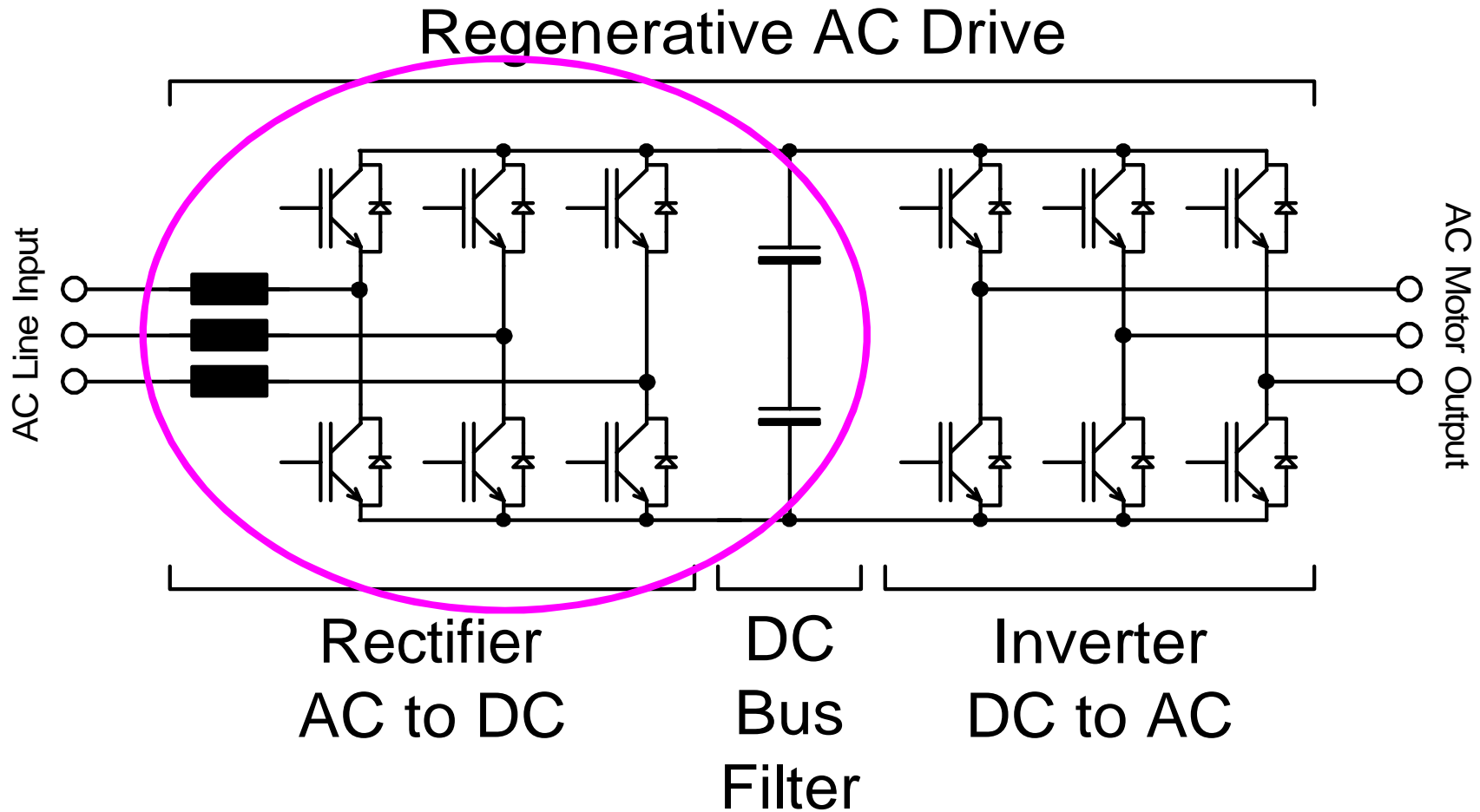


Line Current Harmonic Mitigation Methods

Active Front End (AFE)

* Used in MV drives

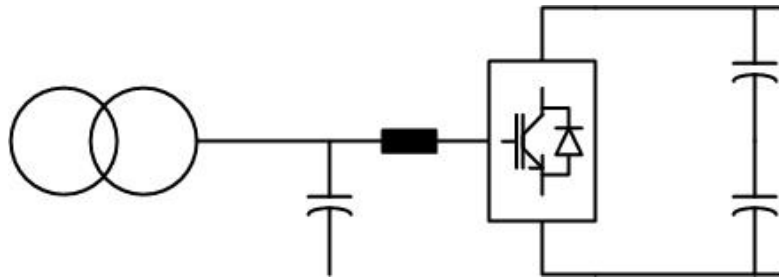

AFE with Isolation Transformer

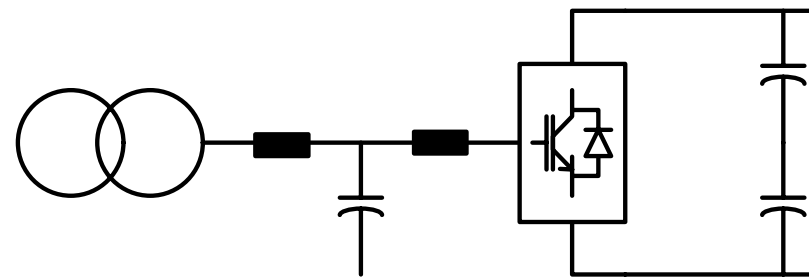


*AFE with LCL Filter


NOTE: The AFE can be 2-Level, 3-Level, 5-Level
(more on this later)

The Goal of Harmonic Mitigation


6-Pulse: 32% I_{thd}

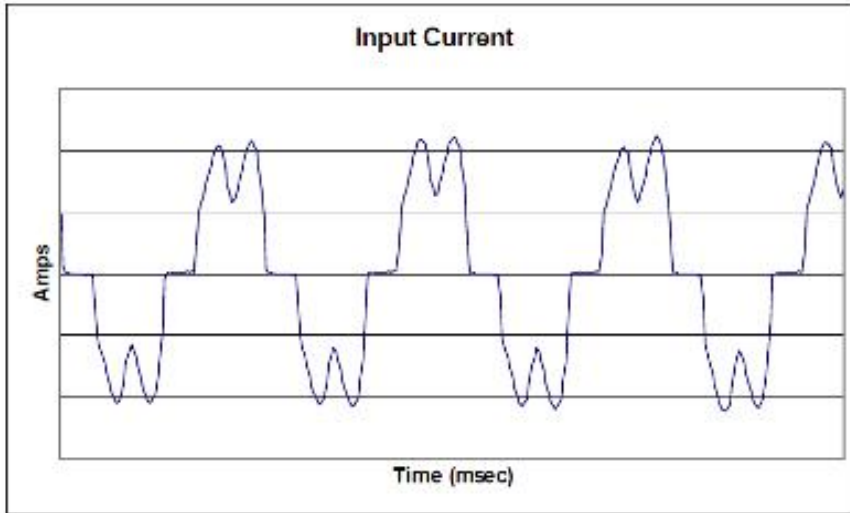

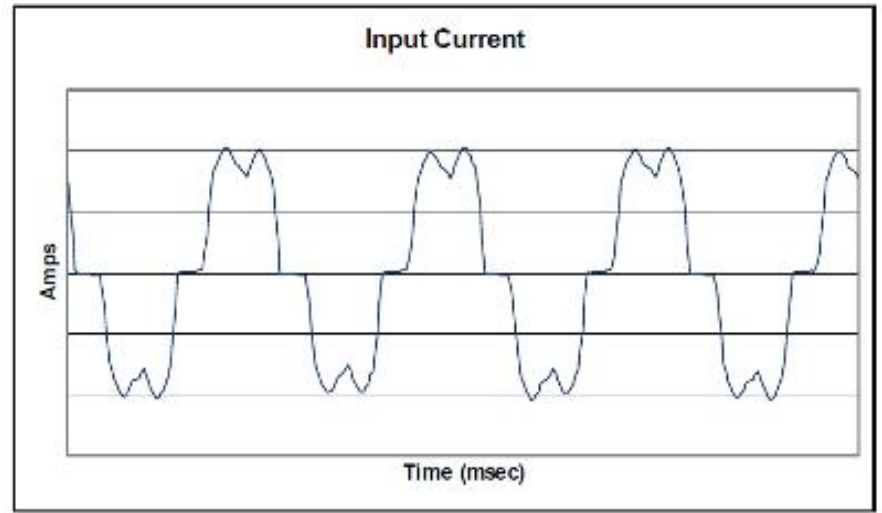
6-Pulse with 5% Line Reactor: 25% I_{thd}



12-Pulse: 10% I_{thd}

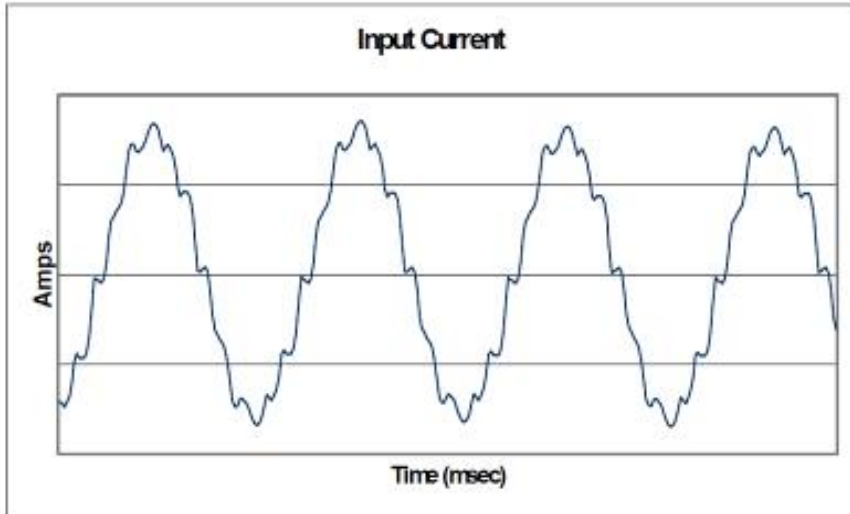

18-Pulse, AFE, AHF: 5% I_{thd}

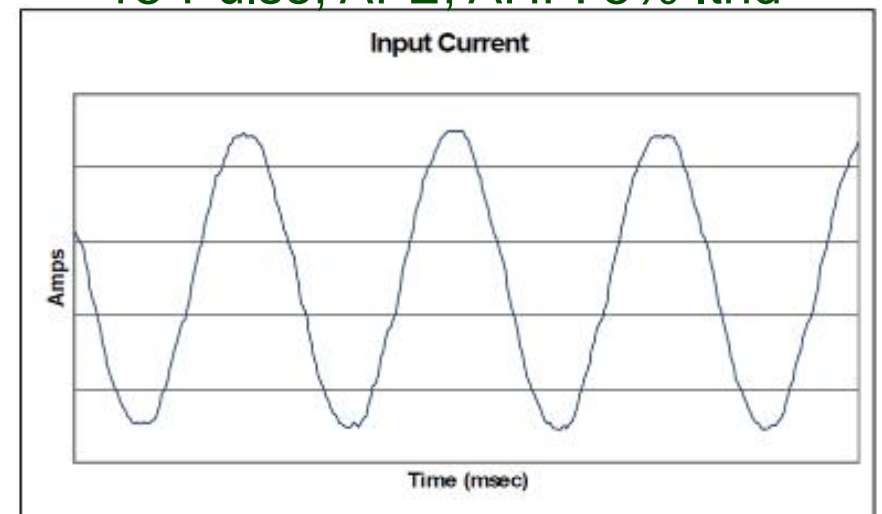

Line Current Harmonic Mitigation Methods

Harmonic Content

Multi-Pulse

	XFMR	lthd	PF
▪ 6 Pulse	std xfmr	30-120%	0.90
▪ 12 Pulse	6 phase shift xfmr	10-15%	0.92
▪ 18 Pulse	9 phase shift xfmr	5-6%	0.95
▪ 24 Pulse	12 phase shift xfmr	4-5%	0.96
▪ 36 Pulse	18 phase shift xfmr	3-4%	0.96


Active Front End (AFE)

▪ AFE	std xfmr	4-5%	1.0
-------	----------	------	-----

Current Source PWM


▪ CSI, LCI	std xfmr	5-6%	0 – 1.0 lead
------------	----------	------	--------------

Power Cube

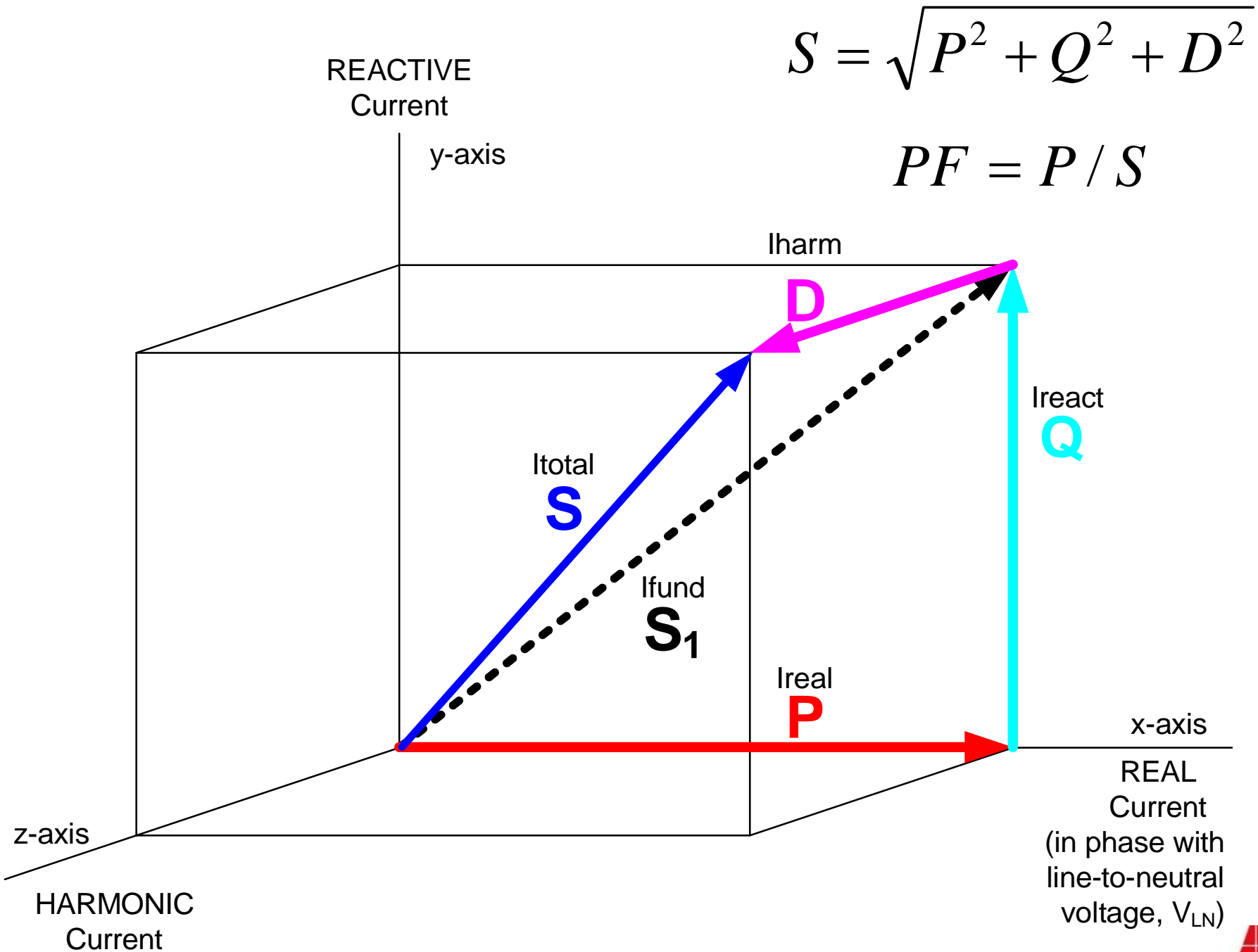


Grounding Configurations

- **Floating** secondary

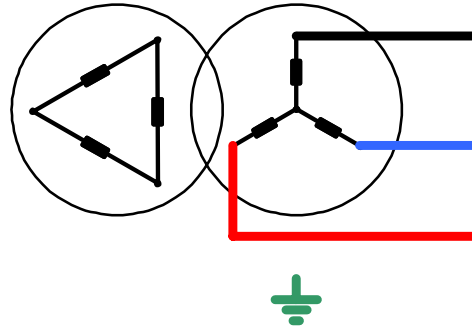


- **Solidly grounded** secondary

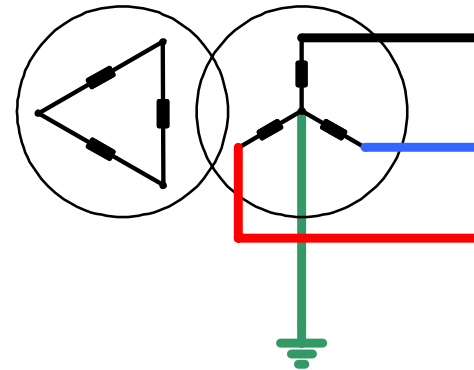

- **Low resistance grounded** secondary

- LV – 10, 50, 100A
- MV – 200, 400A

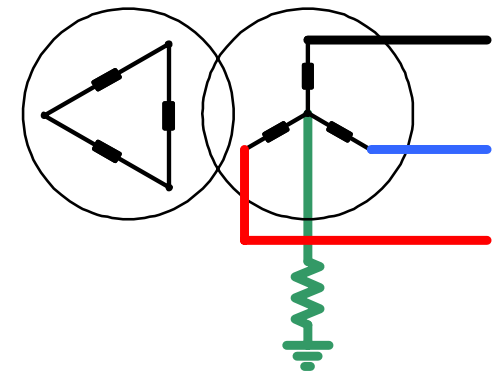

Motor Side Challenges

- NEMA MG-1
- Topologies
- Reflected Wave

MG 1-2006, Rev 1, Part 30

Section IV
APPLICATION CONSIDERATIONS

MG 1-2006
Part 30, Page 1

Section IV PERFORMANCE STANDARDS APPLYING TO ALL MACHINES Part 30

APPLICATION CONSIDERATIONS FOR CONSTANT SPEED MOTORS USED ON A SINUSOIDAL BUS WITH HARMONIC CONTENT AND GENERAL PURPOSE MOTORS USED WITH ADJUSTABLE-VOLTAGE OR ADJUSTABLE-FREQUENCY CONTROLS OR BOTH

30.0 SCOPE

The information in this Section applies to 60 Hz NEMA Designs A and B squirrel-cage motors covered by Part 12 and to motors covered by Part 20 rated 5000 horsepower or less at 7200 volts or less, when used on a sinusoidal bus with harmonic content, or when used with adjustable-voltage or adjustable-frequency controls, or both.

NEMA Designs C and D motors and motors larger than 5000 horsepower and voltages greater than 7200 volts are excluded from this section and the manufacturer should be consulted regarding their application.


For motors intended for use in hazardous (classified) locations refer to 30.2.2.10.

Topologies

- Reflected Wave Reduction
 - 2-Level
 - 3-Level
 - 5-Level
 - Cascaded H-Bridge
- CSI, LCI
- CCV
- Matrix

Basic AC Drive Topology



2-Level Inverter Topology

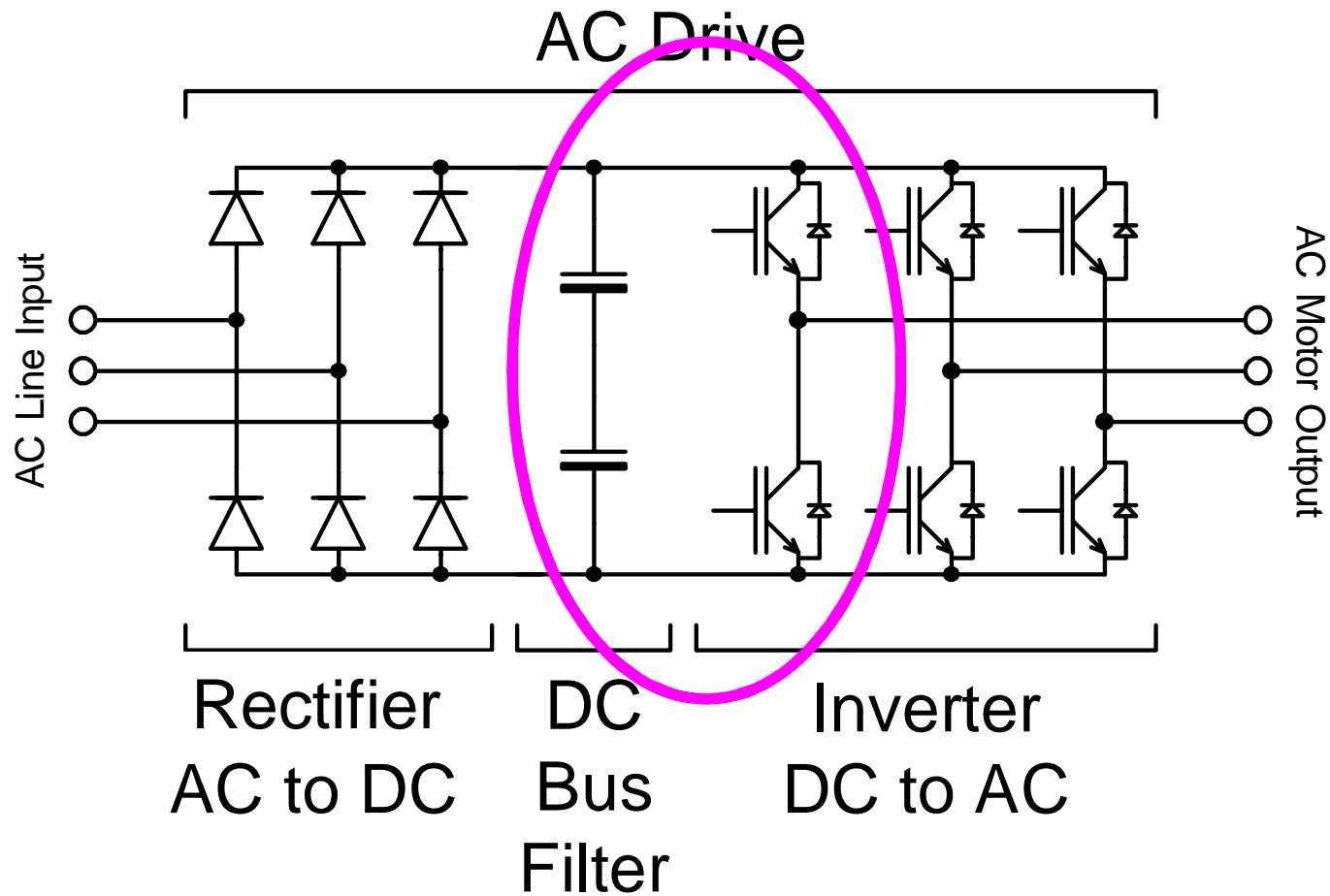

The n-level VSI topology

2-Level



- 2-Level VSI
- Phase output voltages

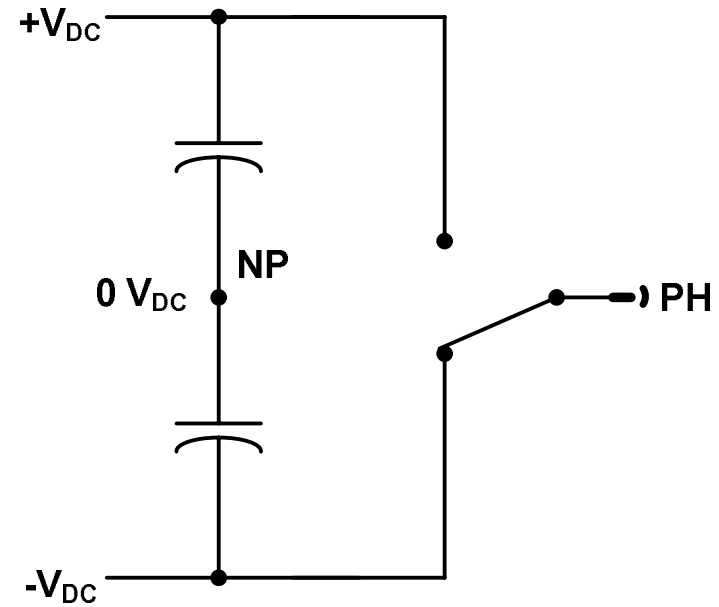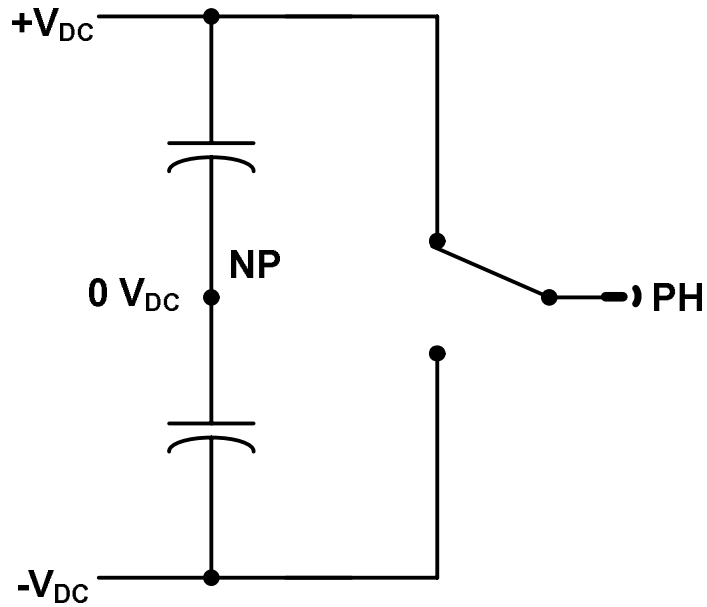

The n-level VSI topology

2-Level



- 2-Level VSI
- Phase output voltages

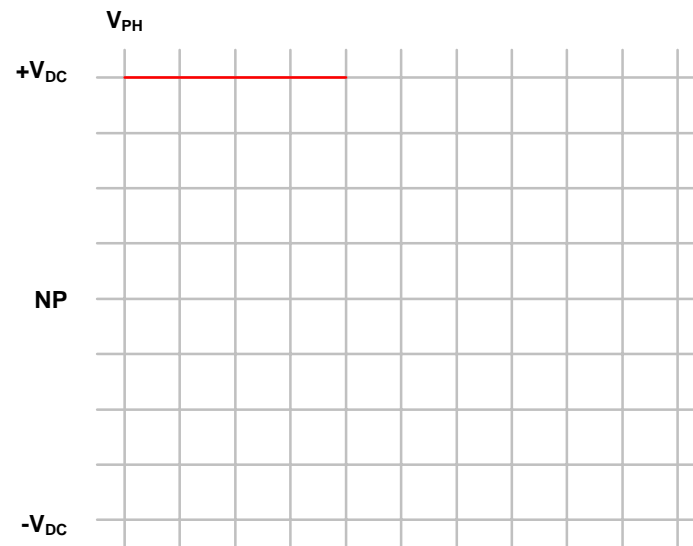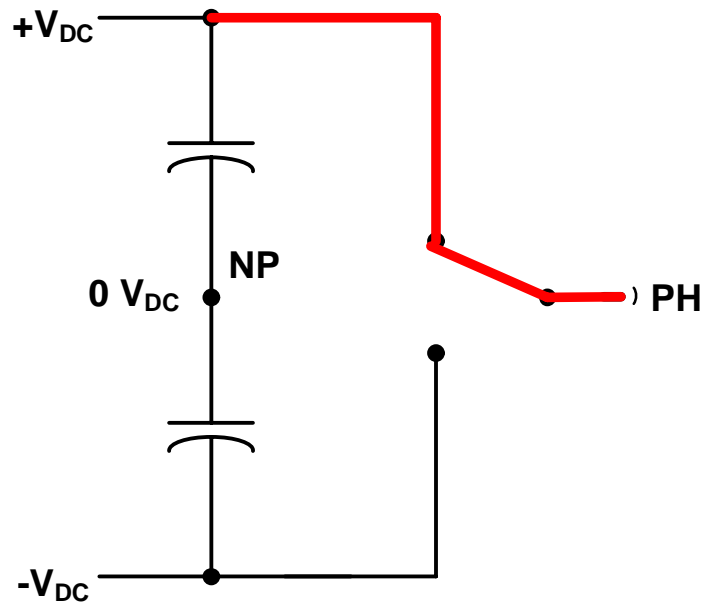

The n-level VSI topology

2-Level


- 2-Level VSI
- Phase output voltages

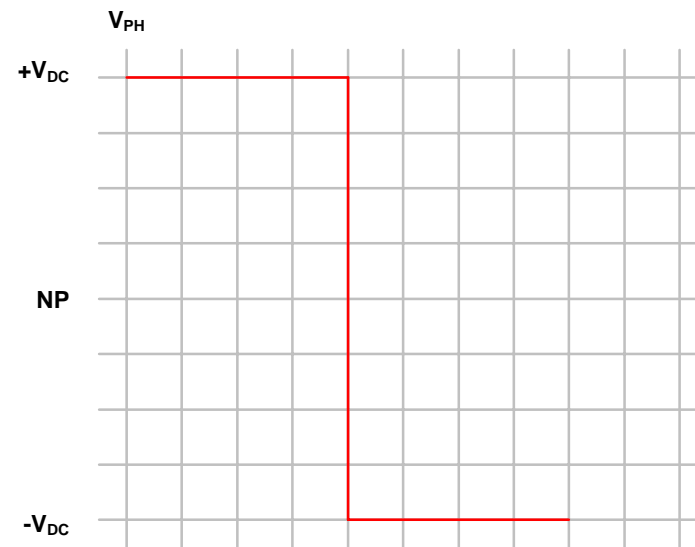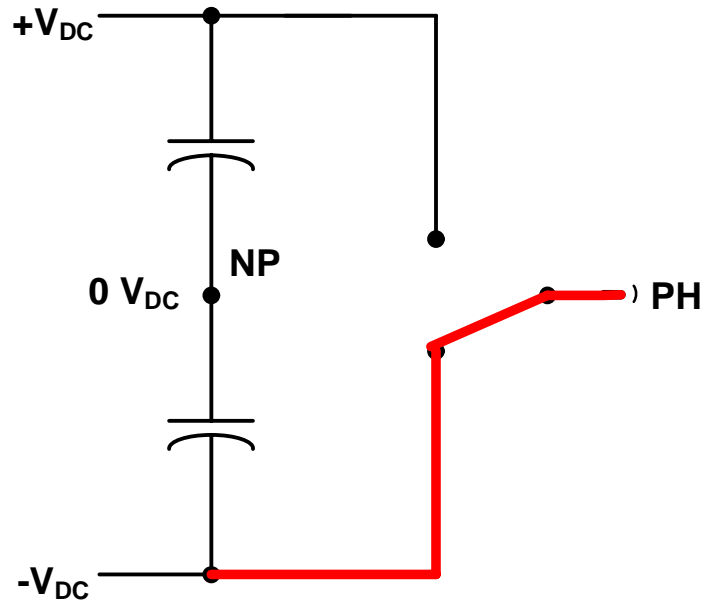

The n-level VSI topology

2-Level



- 2-Level VSI
- Phase output voltages

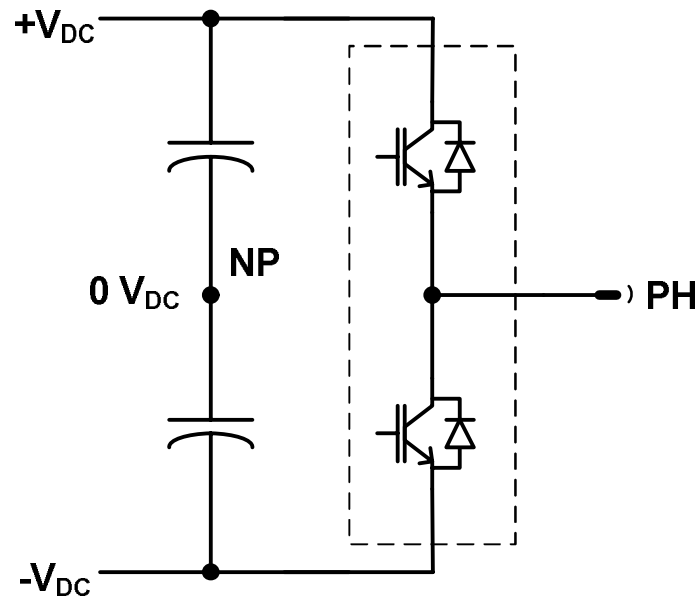

The n-level VSI topology

2-Level



- 2-Level VSI
- Phase output voltages

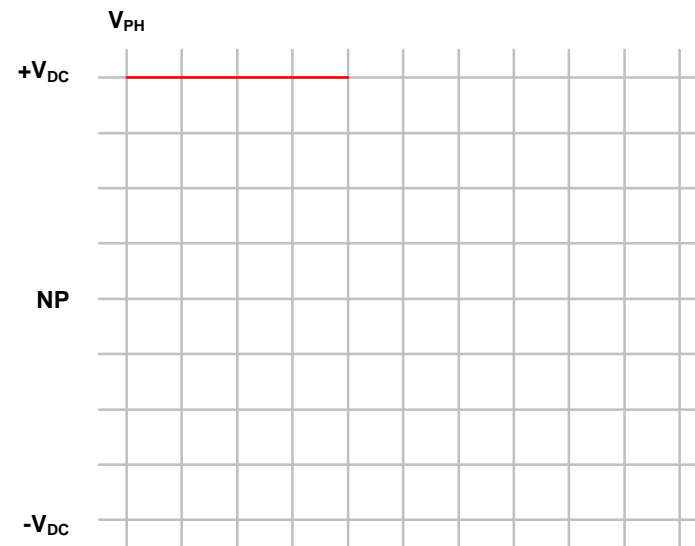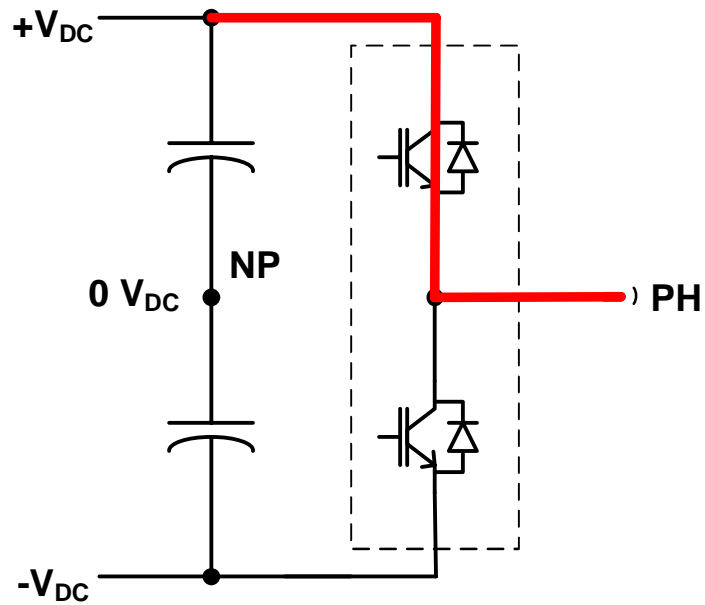


The n-level VSI topology

2-Level


- 2-Level VSI
- Phase output voltages

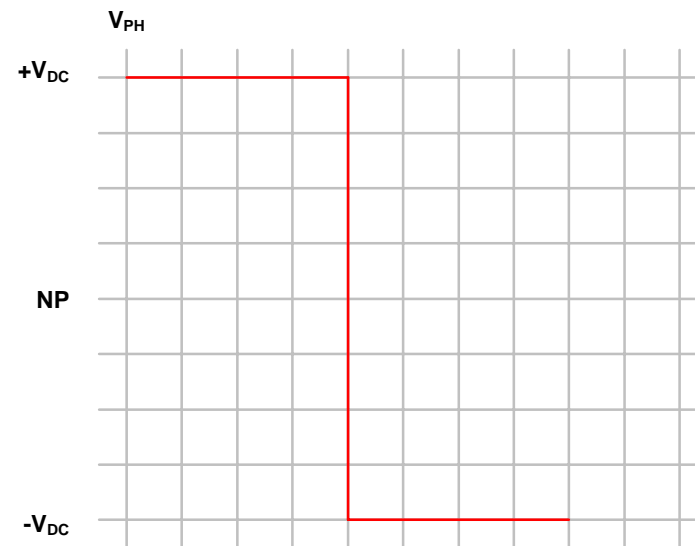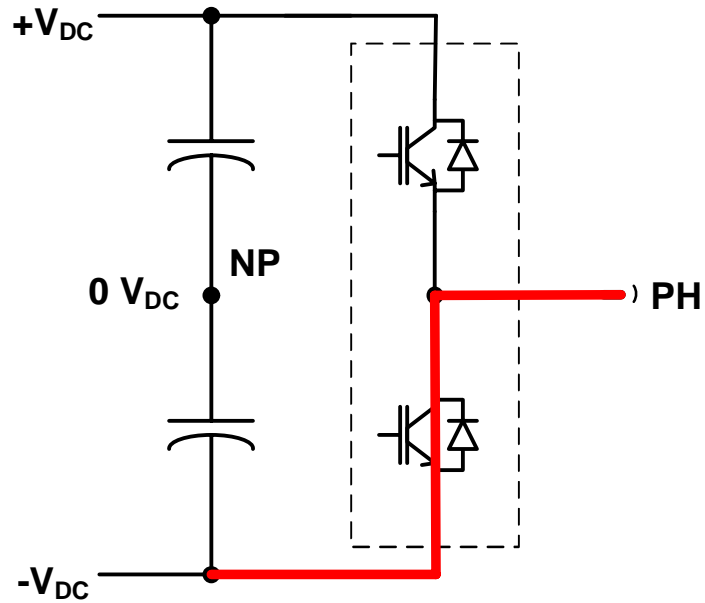


The n-level VSI topology H-Bridge

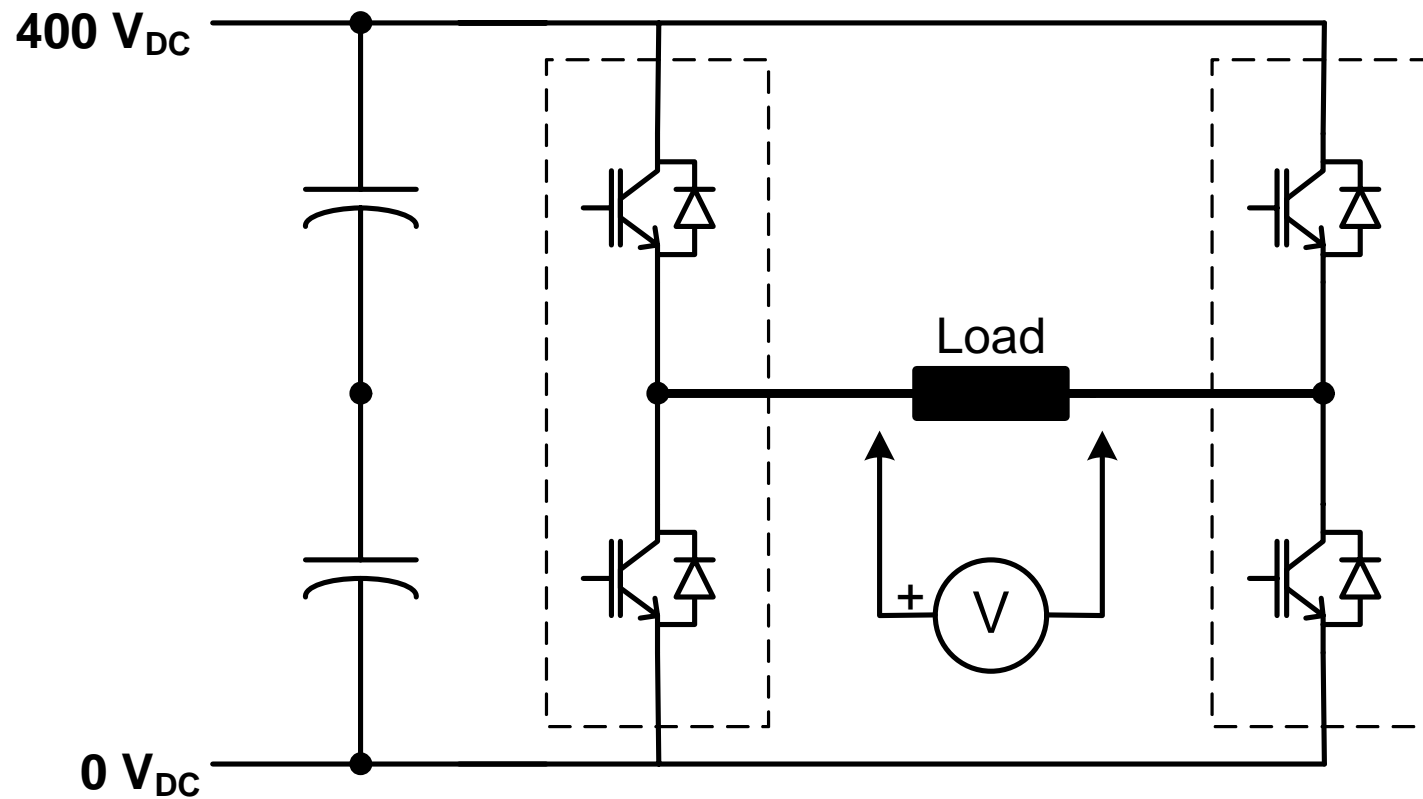

The n-level VSI topology H-Bridge




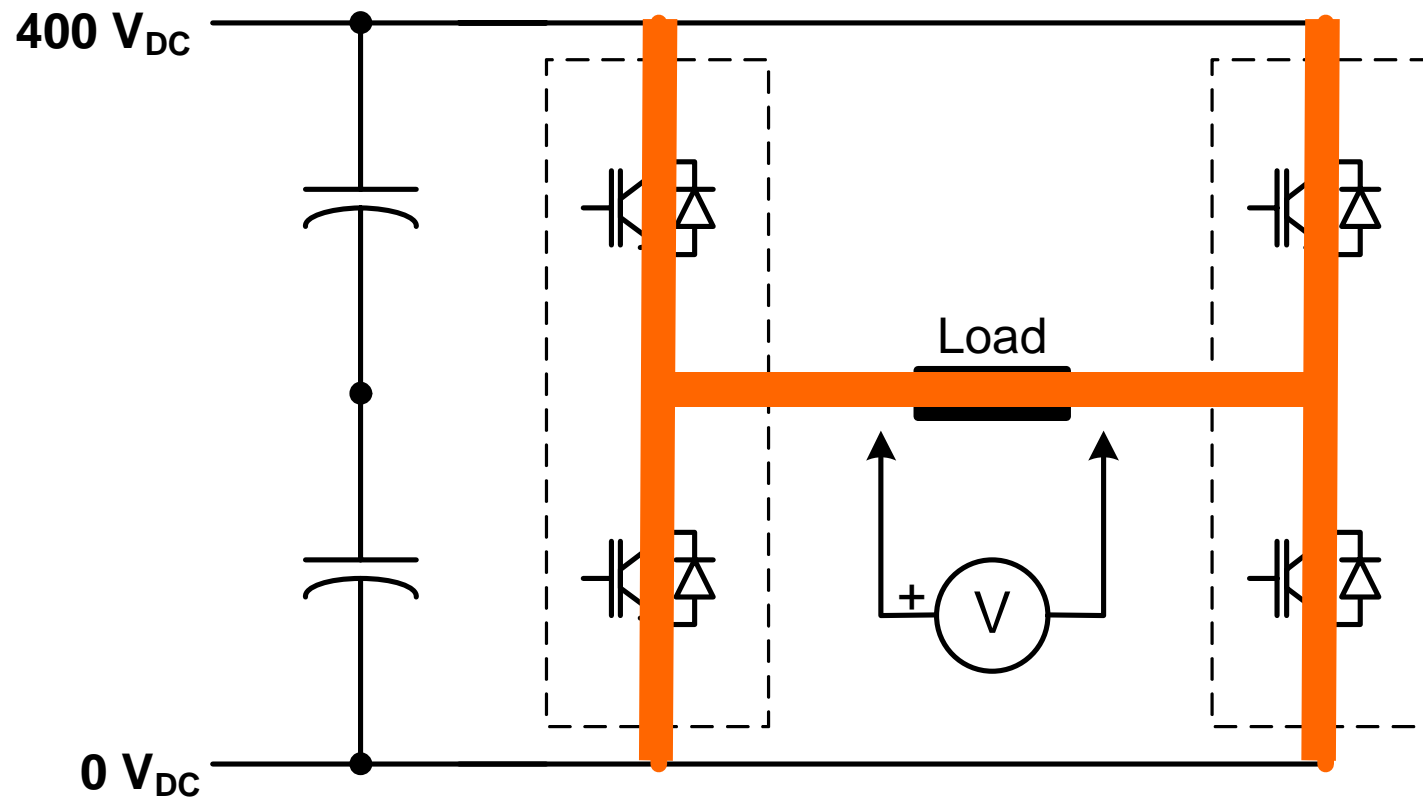


The n-level VSI topology H-Bridge

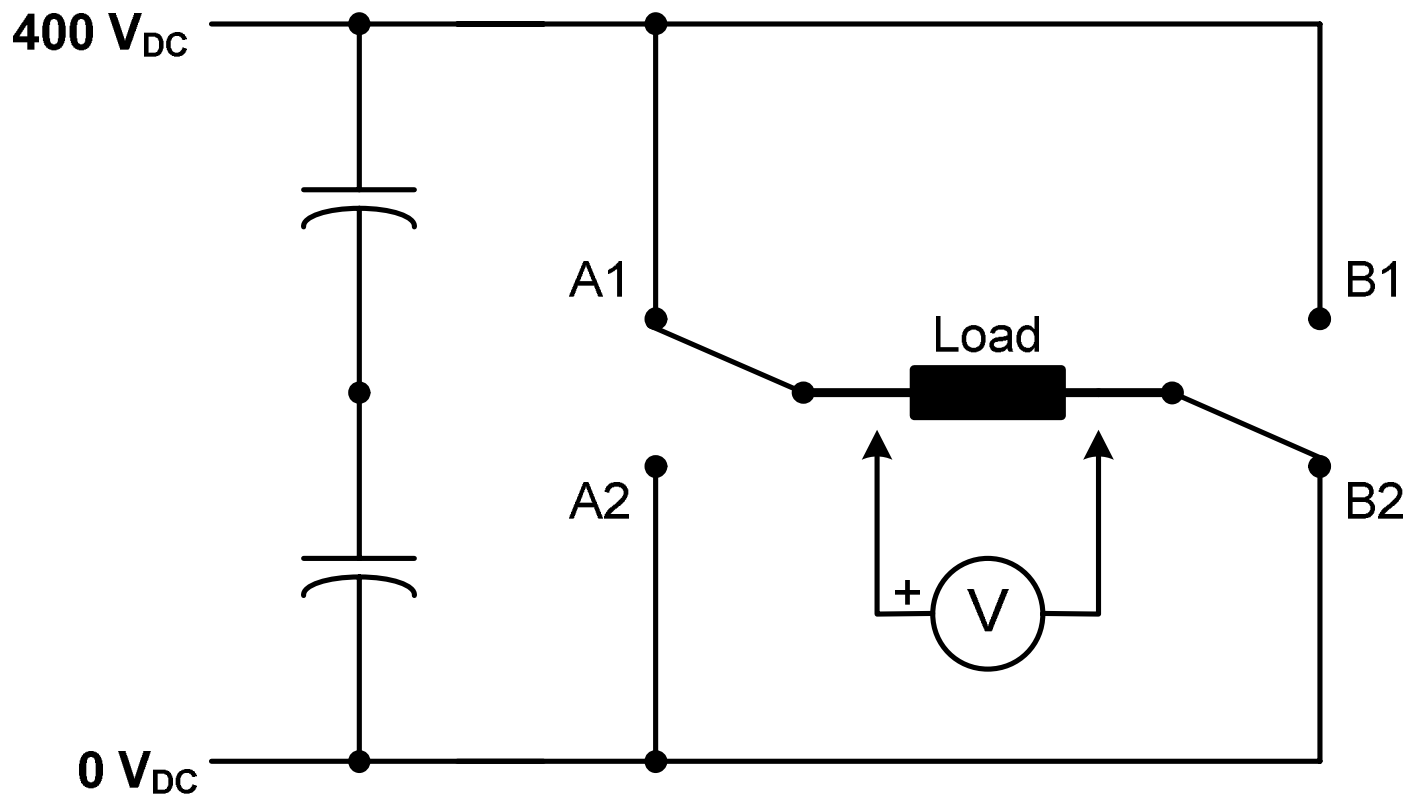

The n-level VSI topology



H-Bridge

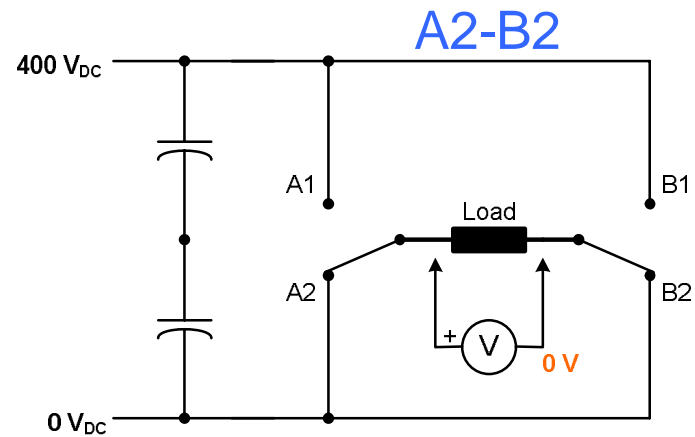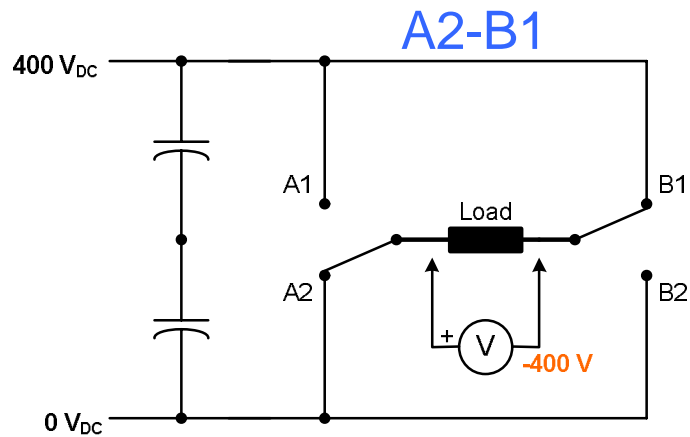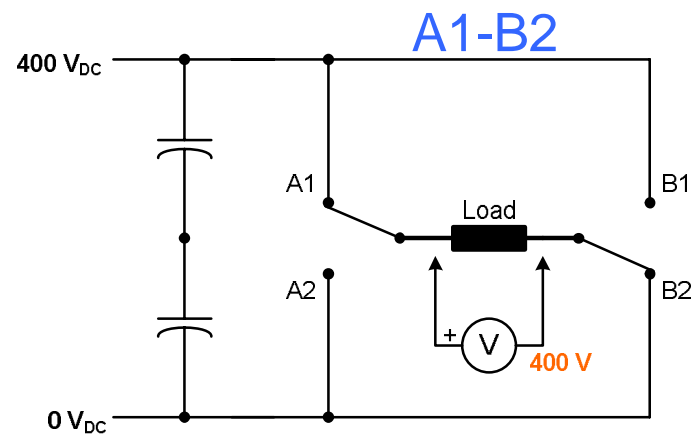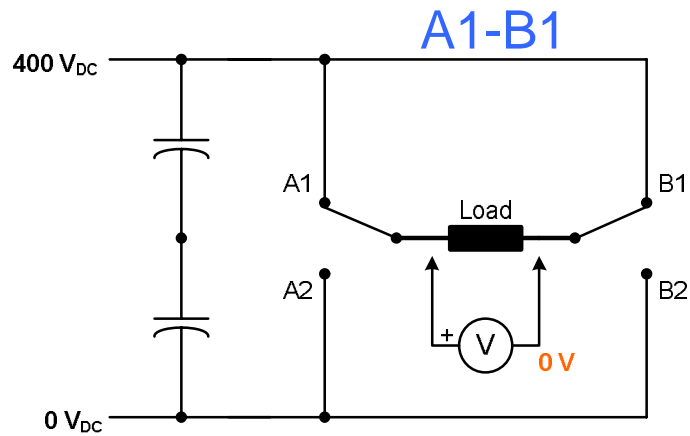

The n-level VSI topology H-Bridge


- 2-Level VSI
- Phase output voltages

	B1	B2
A1	0	400
A2	-400	0

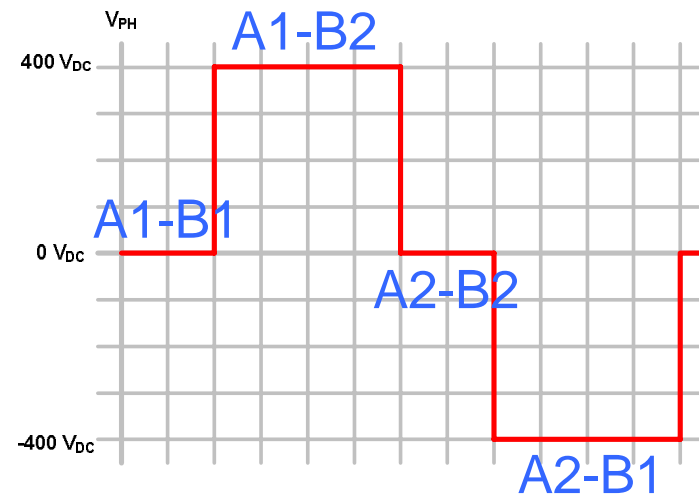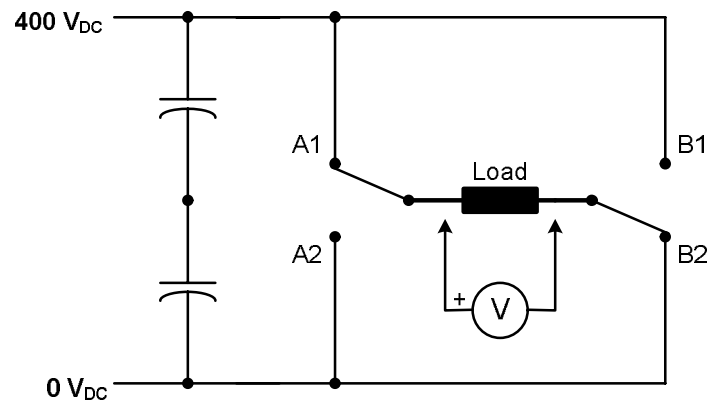

The n-level VSI topology H-Bridge

- 2-Level VSI
- Phase output voltages

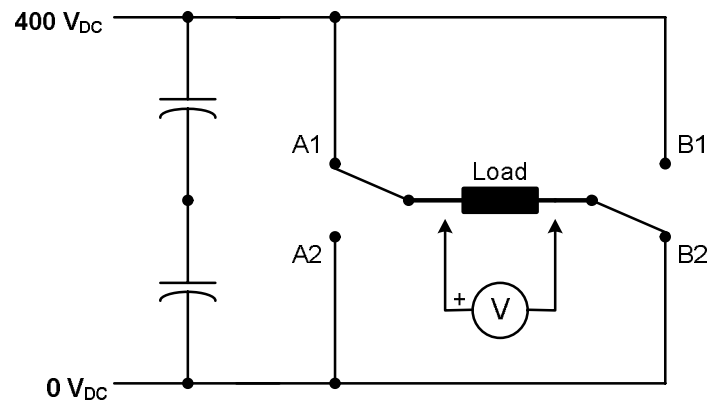

	B1	B2
A1	0	400
A2	-400	0


Number of
Levels, n

2

Number of Voltage
steps, line-to-line,
 $2n-1$

3

2-Level Waveform, Line-to-Line

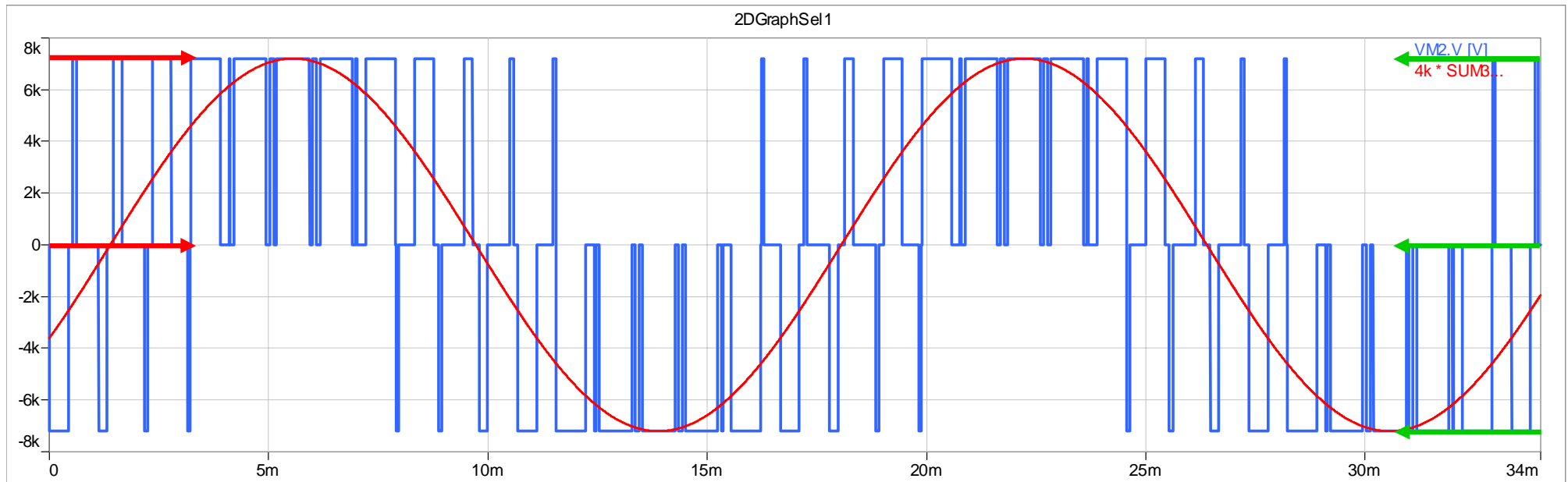


2-Levels

3-Steps

Basic Inverter

2-Level


3 Phase Bridge Configuration

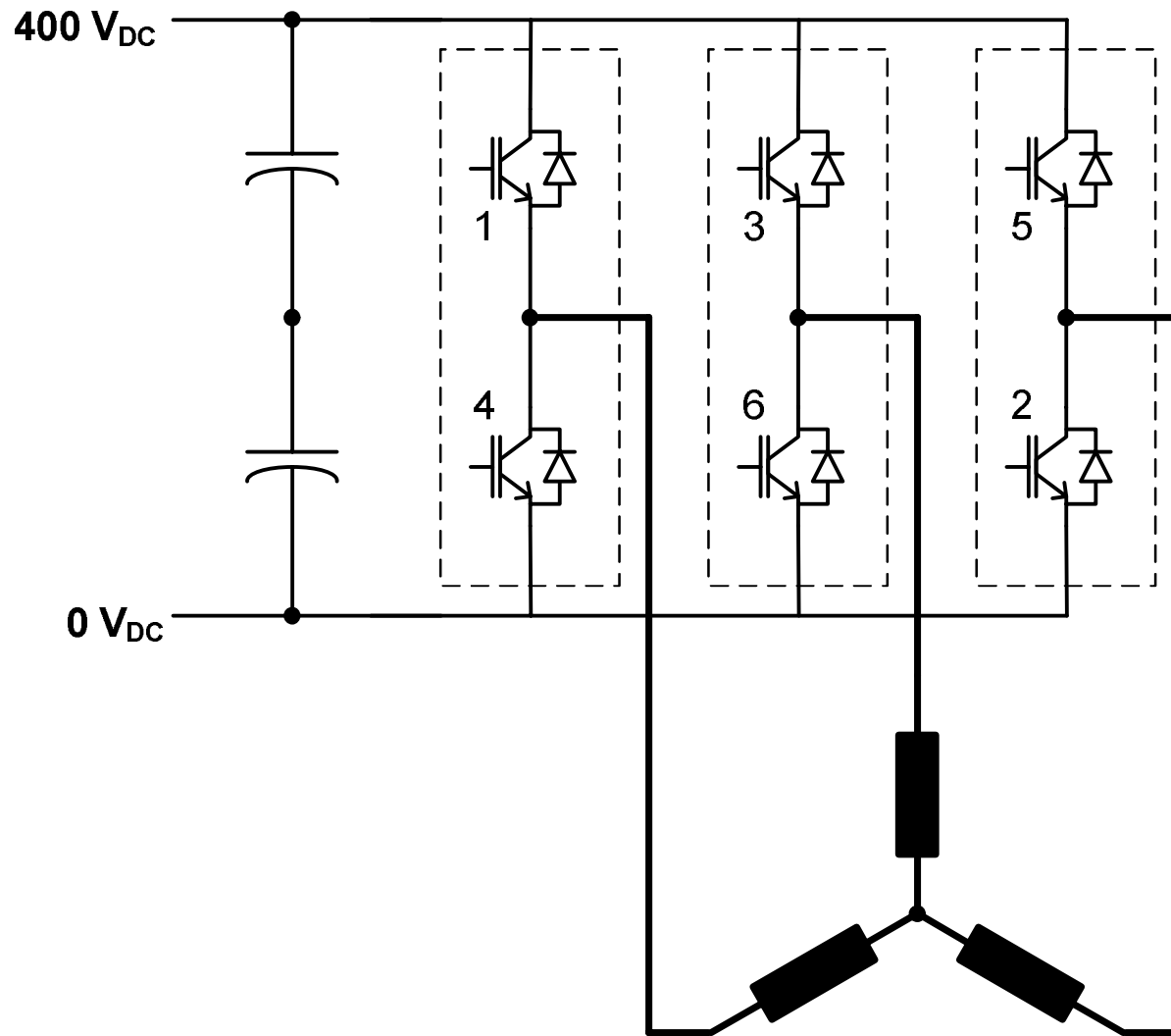

Basic Inverter

2-Level


3 Phase Bridge Configuration

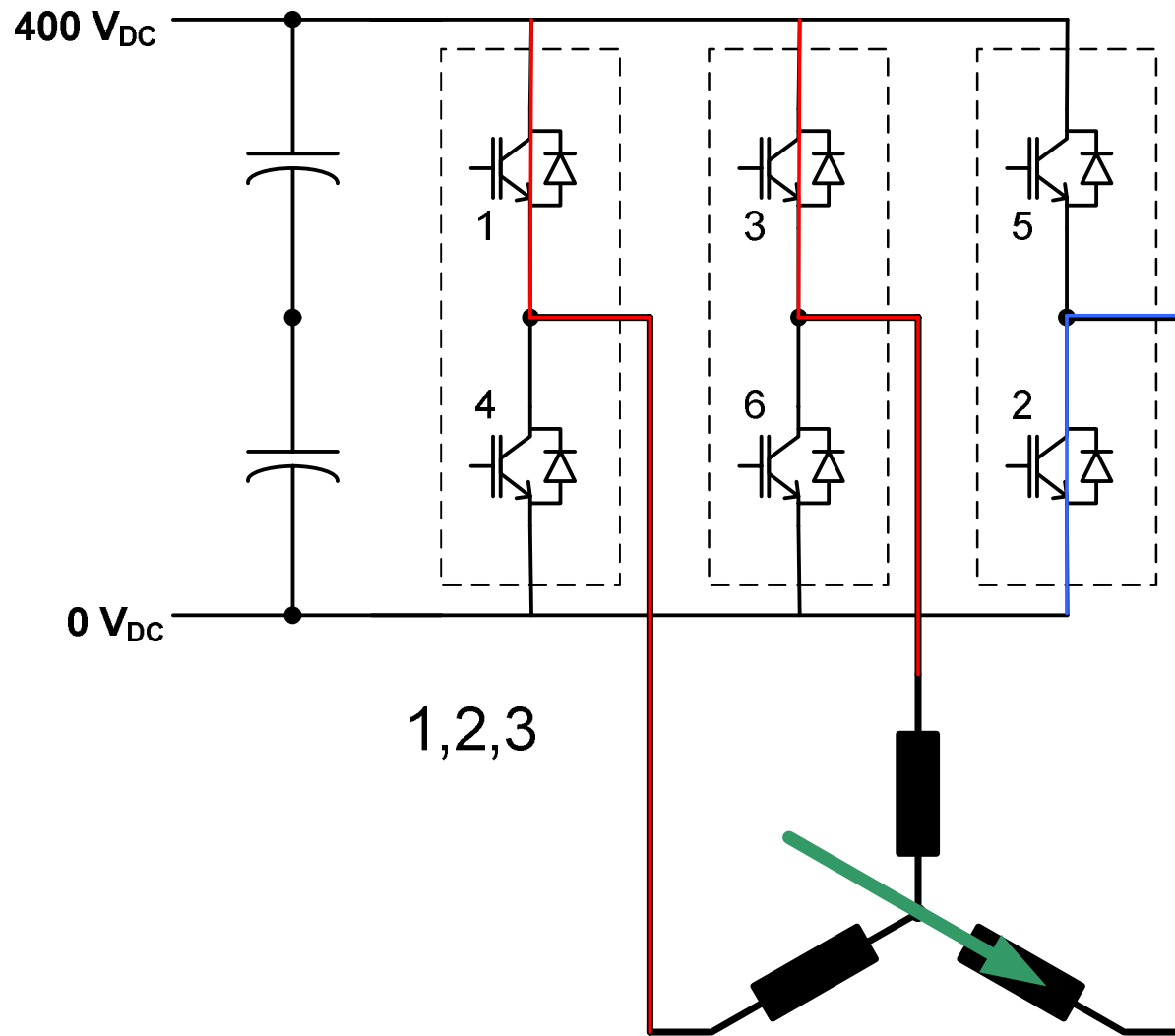

Basic Inverter

2-Level


3 Phase Bridge Configuration

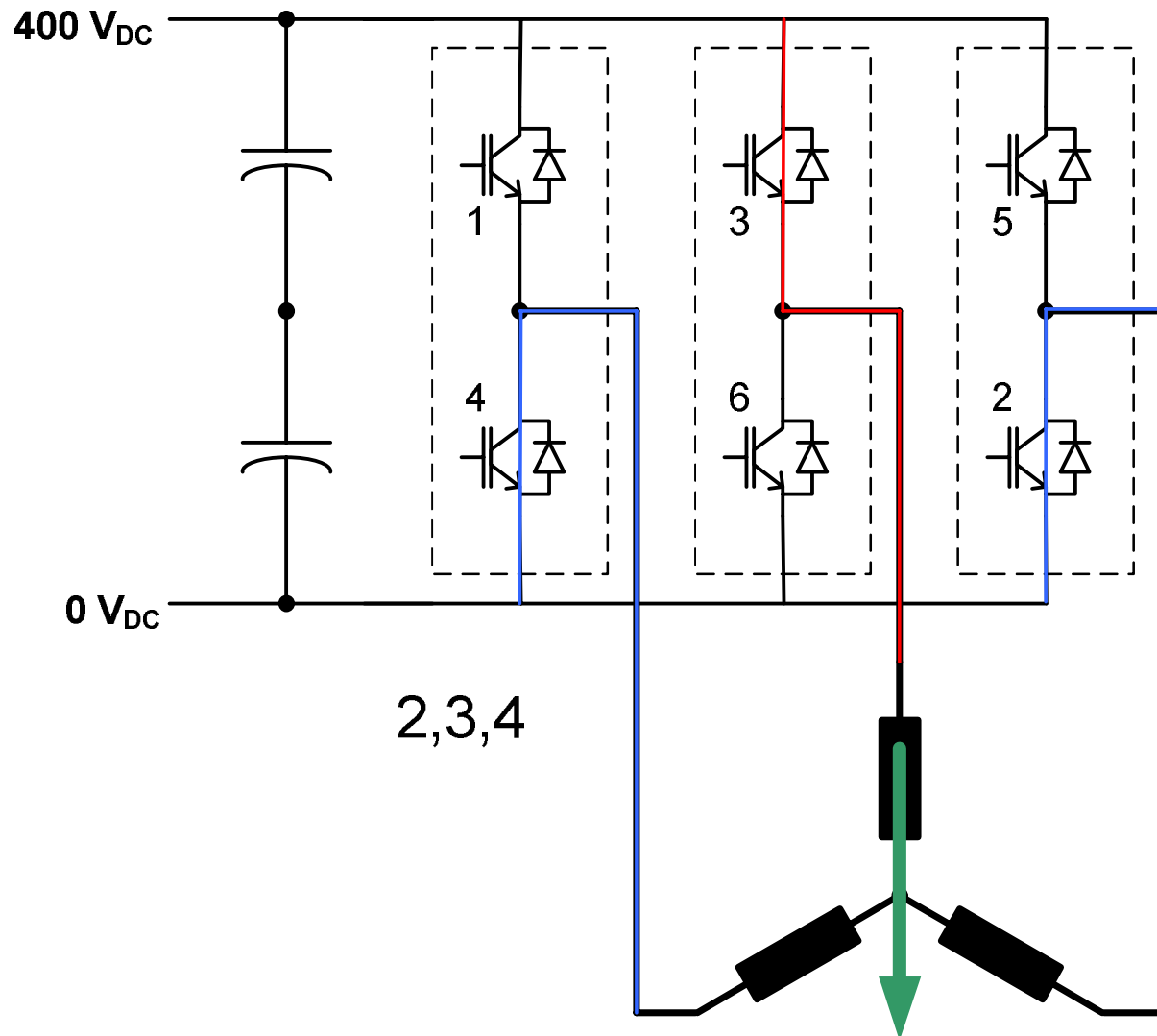

Basic Inverter

2-Level


3 Phase Bridge Configuration

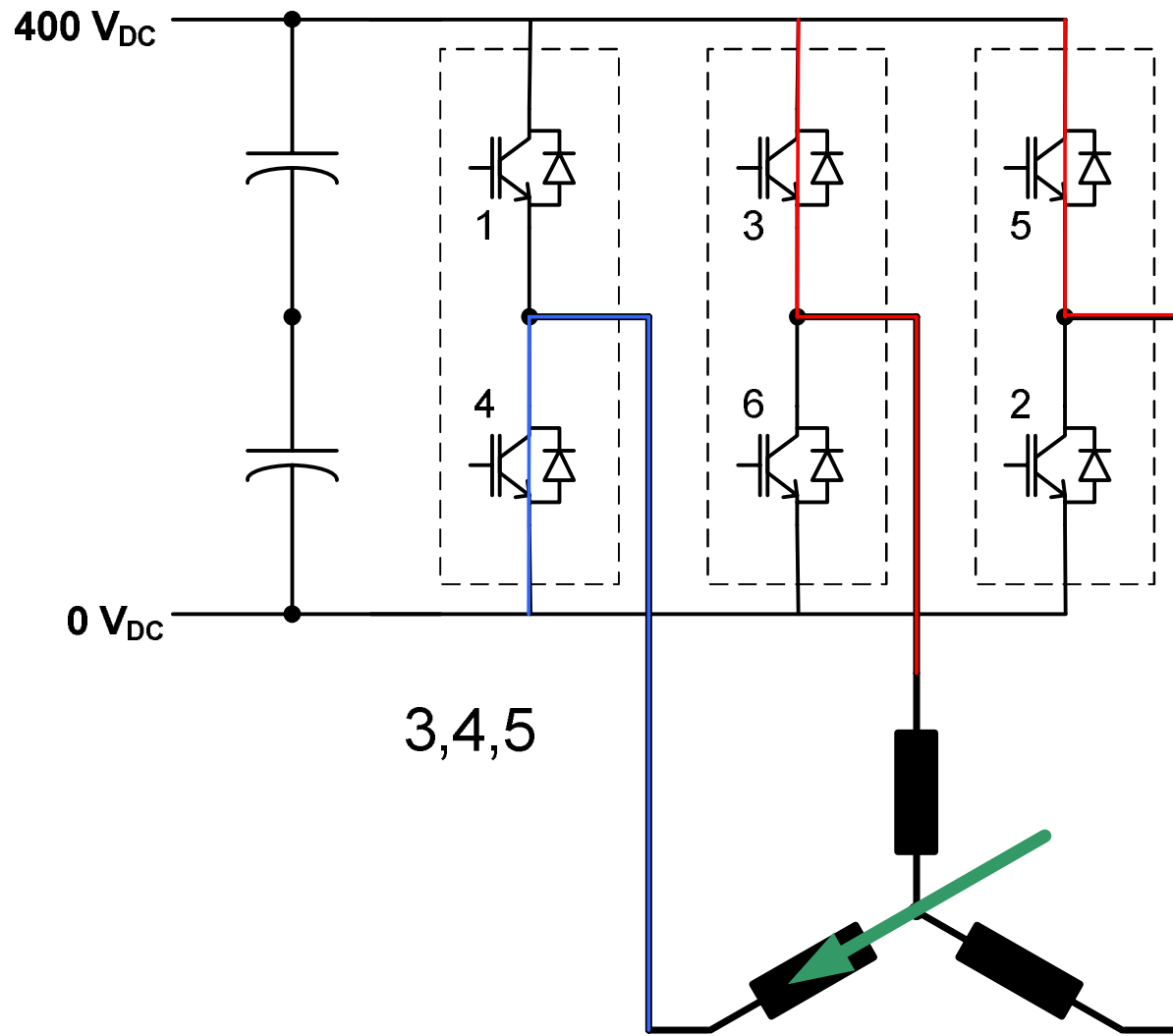

Basic Inverter

2-Level


3 Phase Bridge Configuration

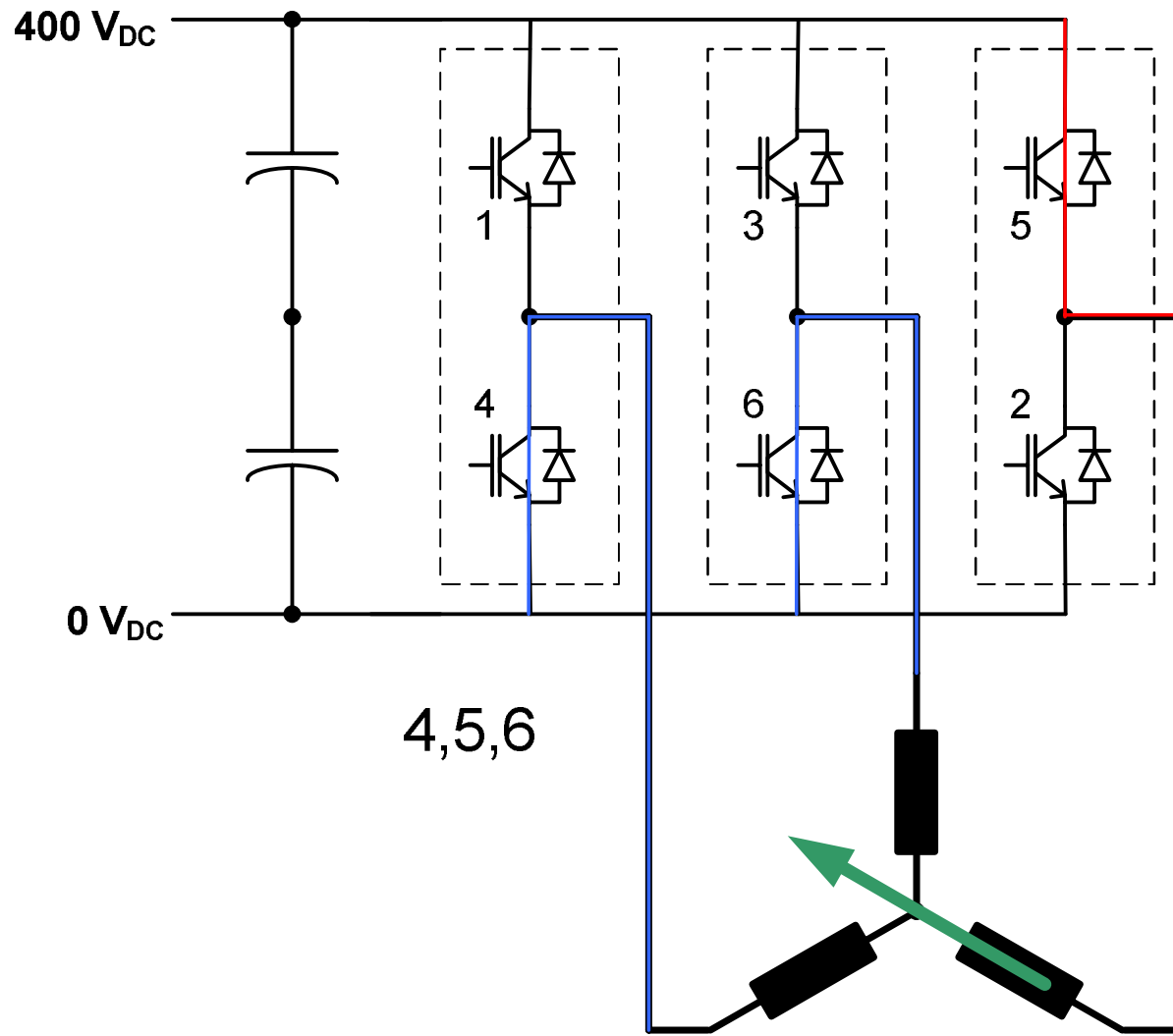

Basic Inverter

2-Level


3 Phase Bridge Configuration

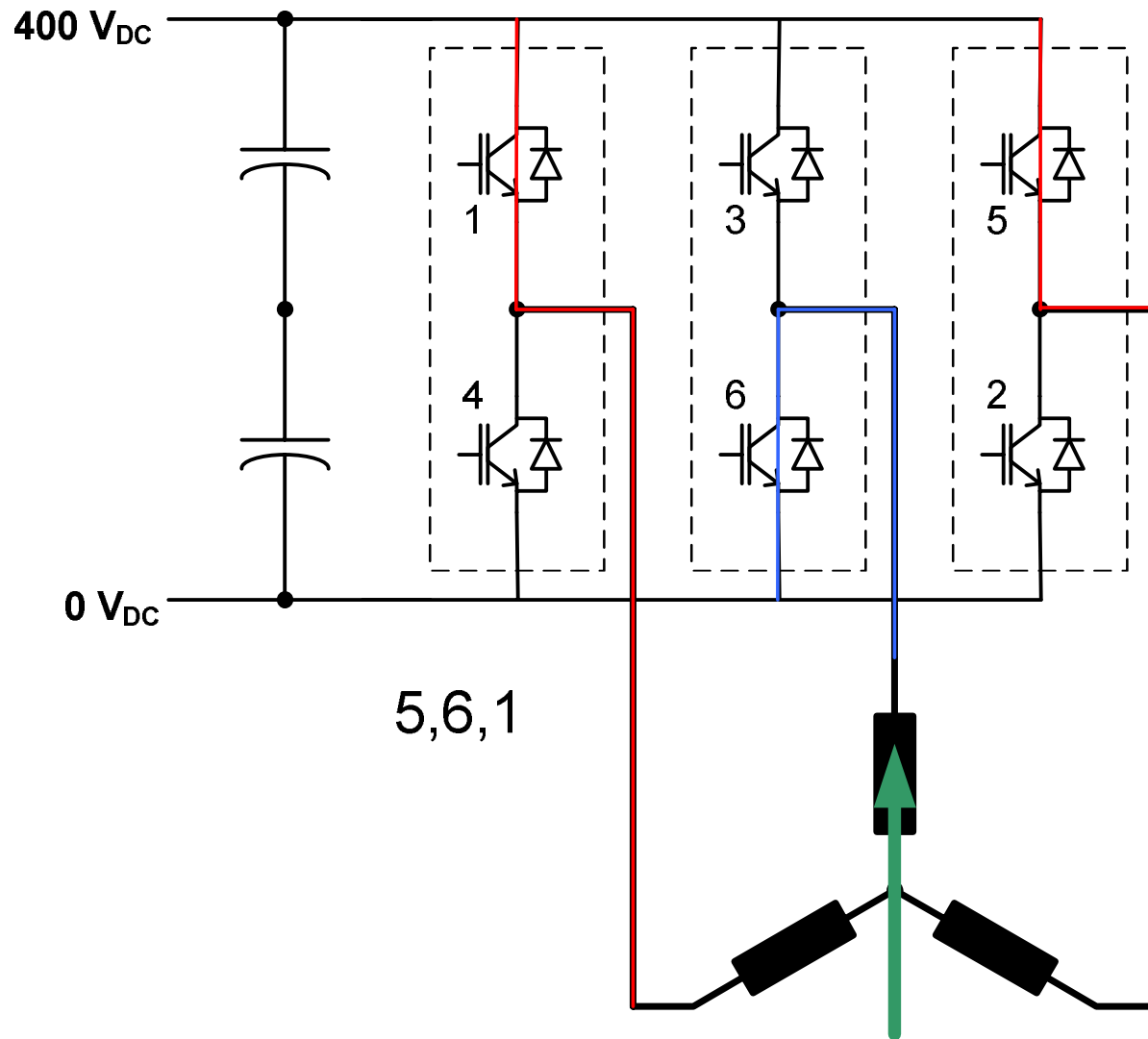

Basic Inverter

2-Level


3 Phase Bridge Configuration

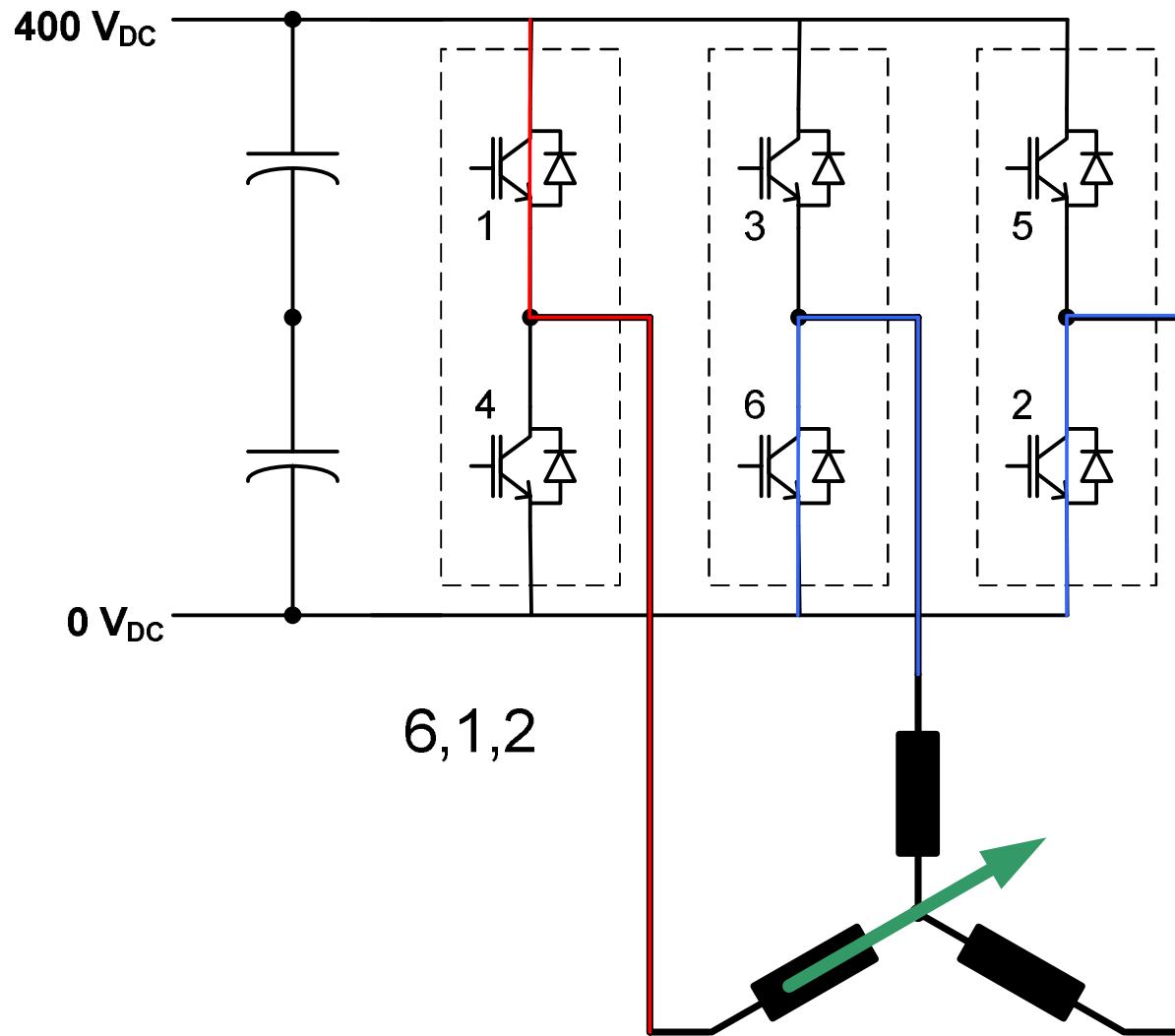

Basic Inverter

2-Level




3 Phase Bridge Configuration

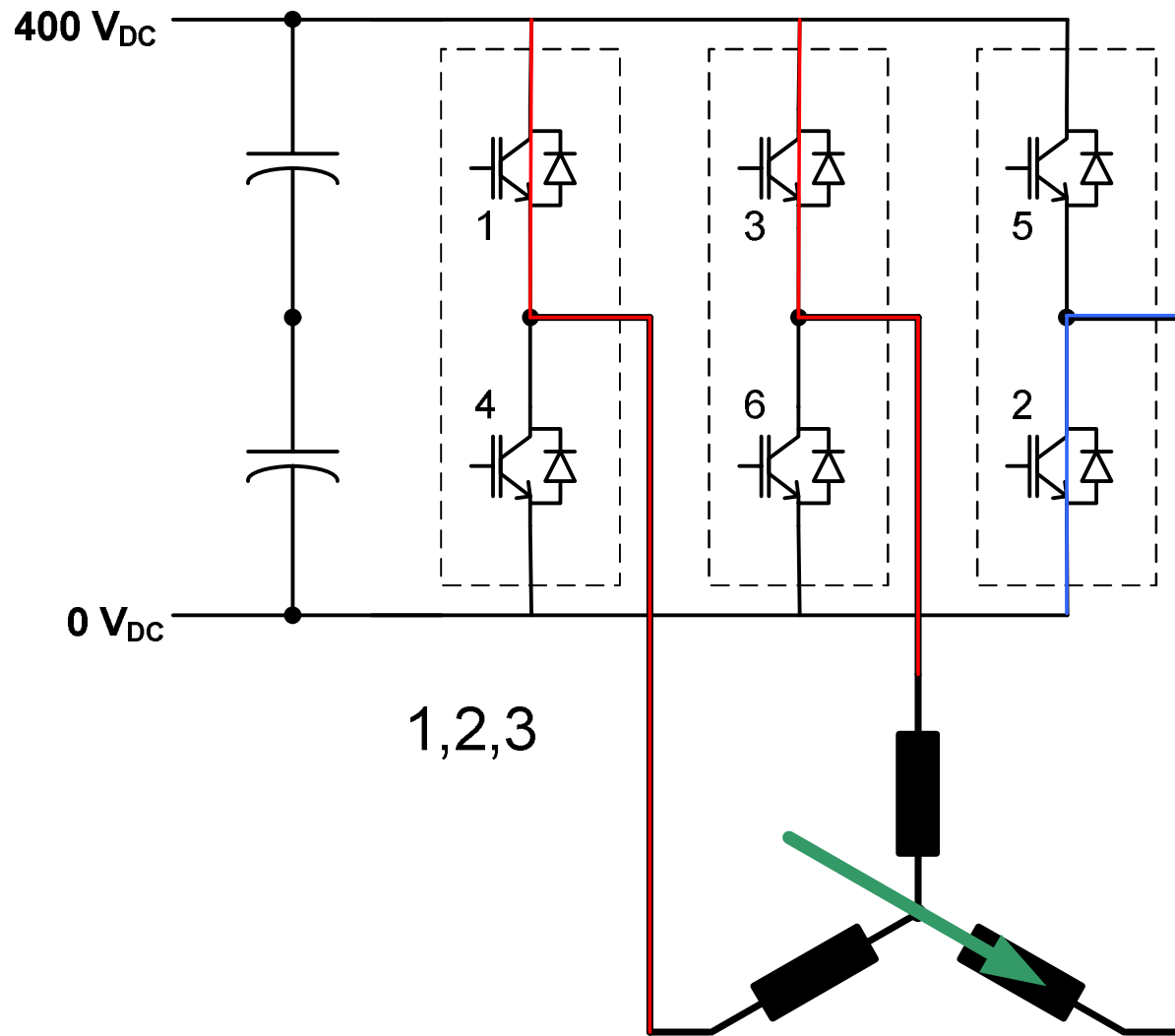

The n-level VSI topology

3-Level

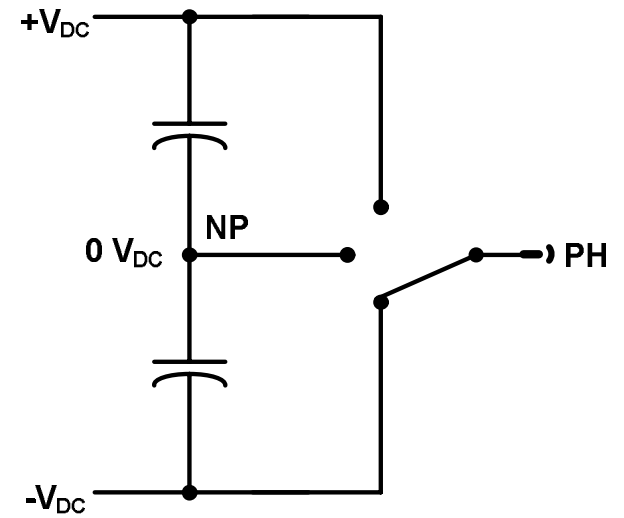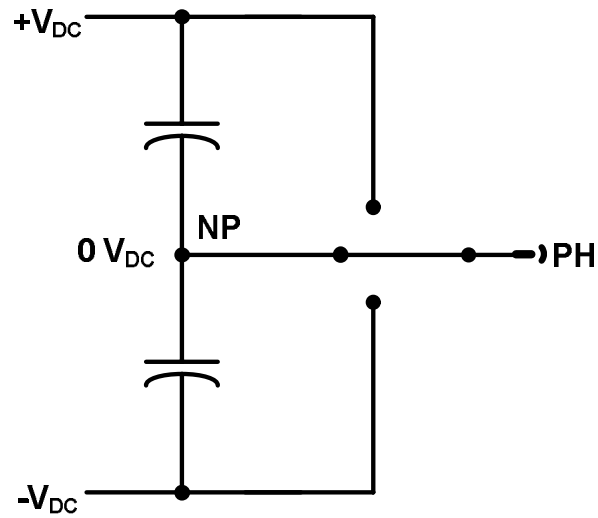
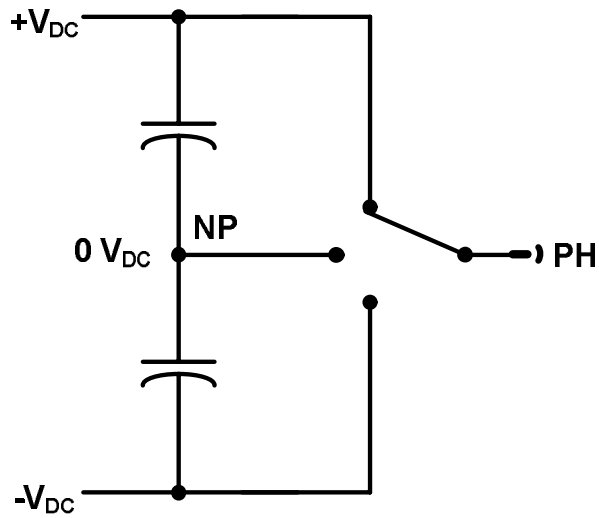
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology

3-Level

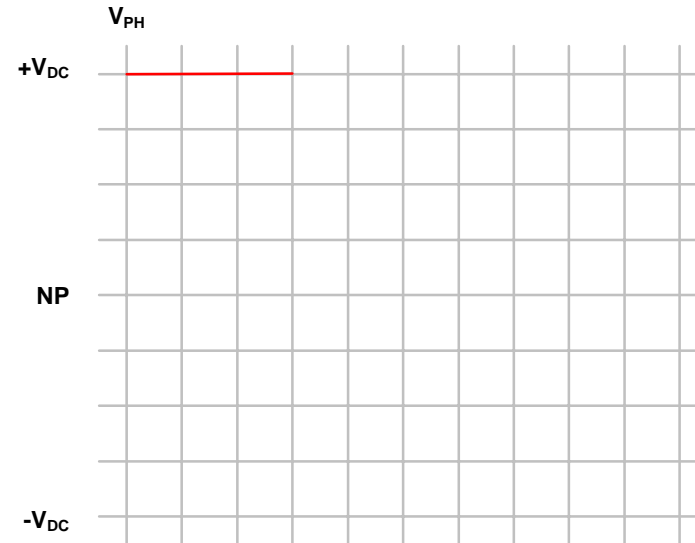
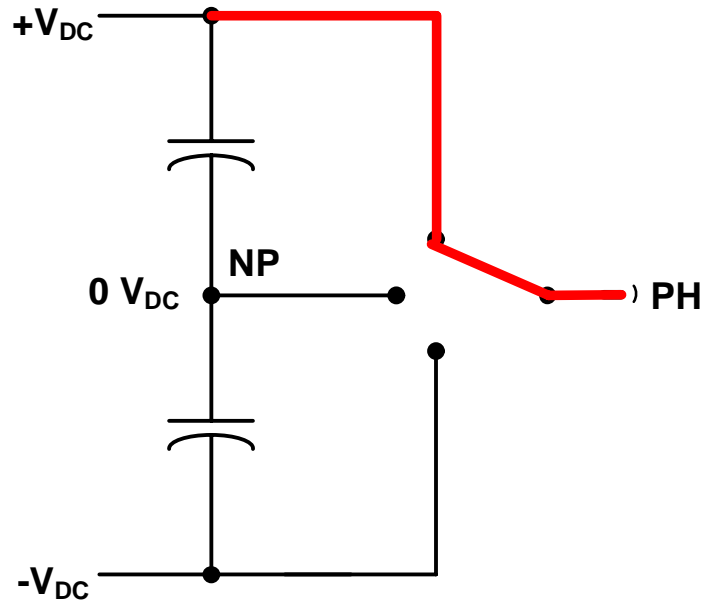
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology

3-Level

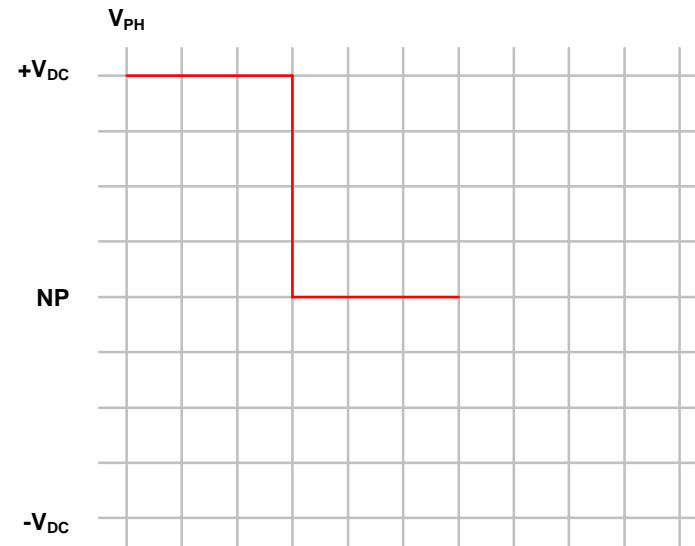
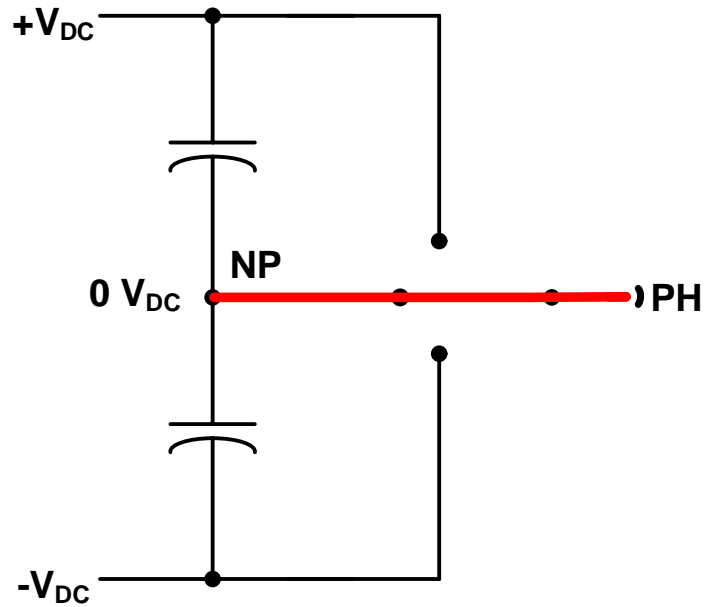
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology


3-Level

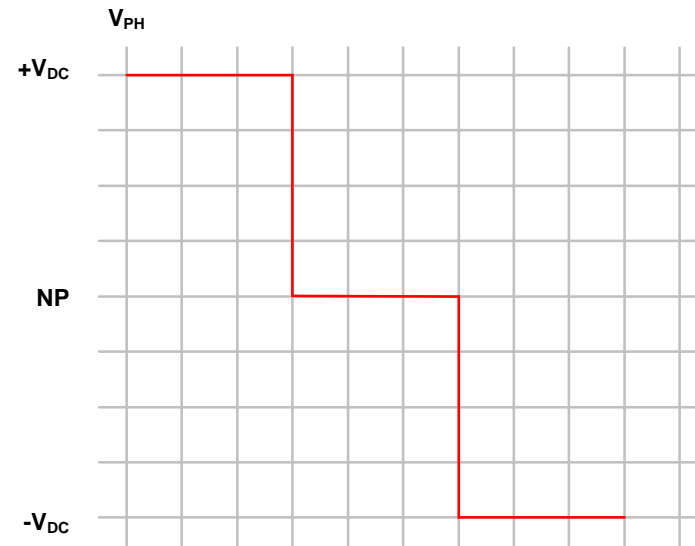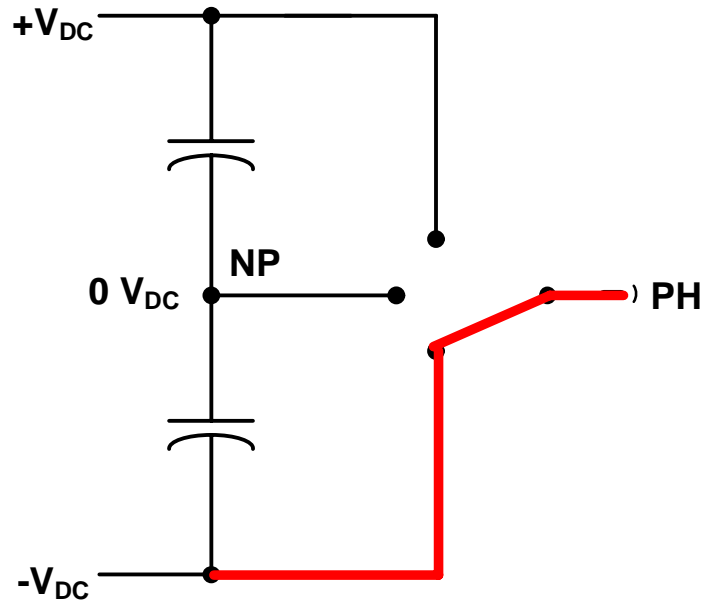- 3-Level NPC VSI
- Phase output voltages




The n-level VSI topology

Going from 2-Level to 3-Level

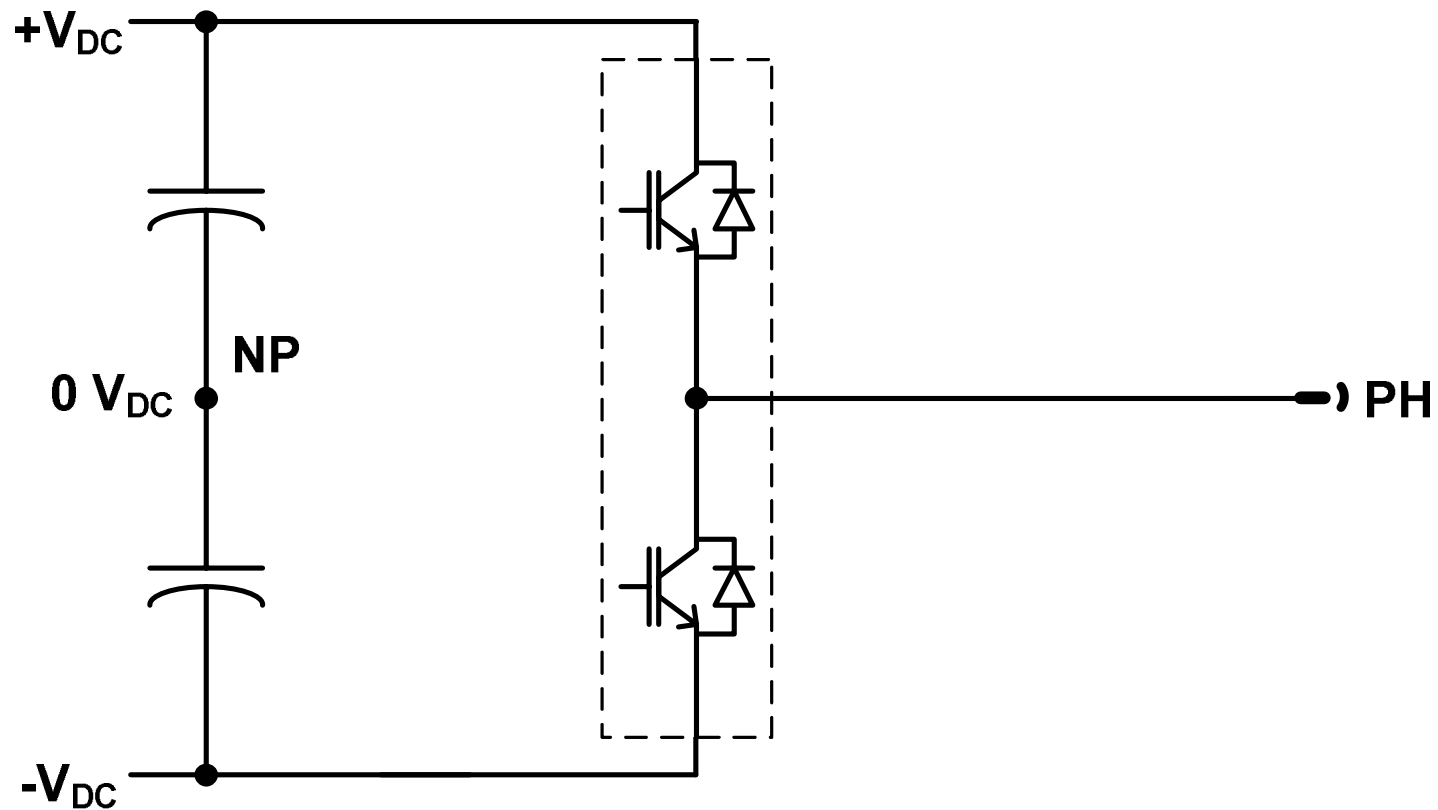


The n-level VSI topology

Going from 2-Level to 3-Level

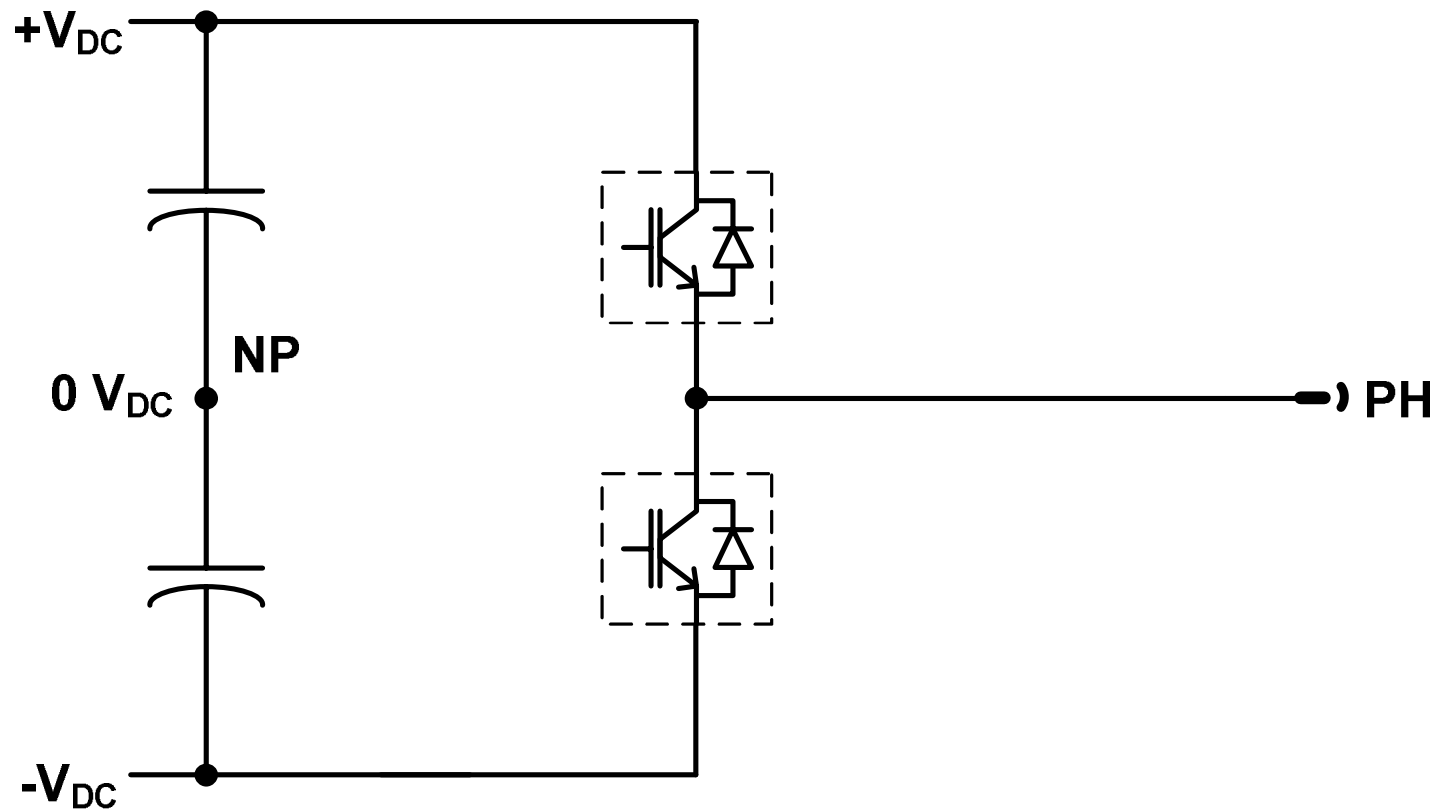


The n-level VSI topology

Going from 2-Level to 3-Level

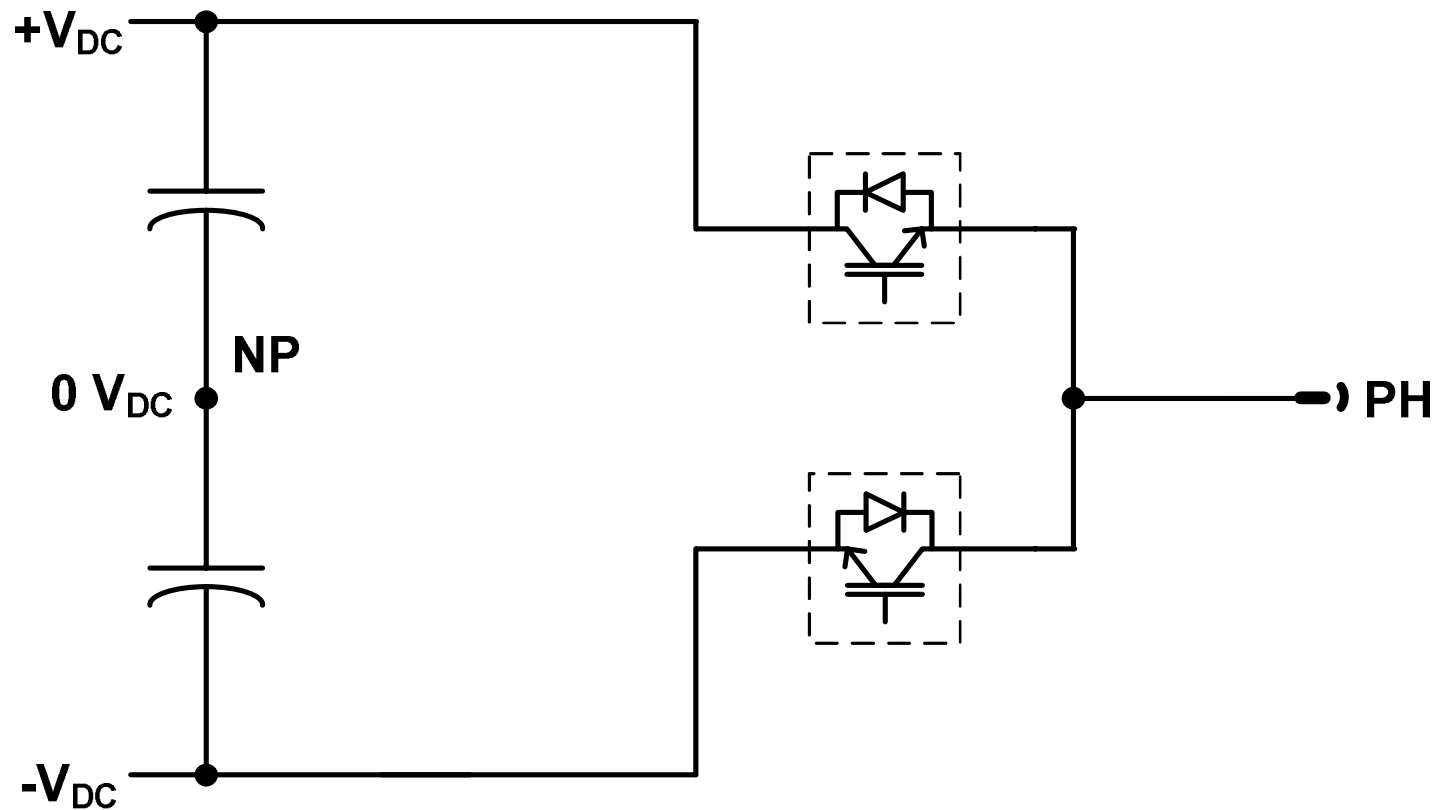


The n-level VSI topology

Going from 2-Level to 3-Level

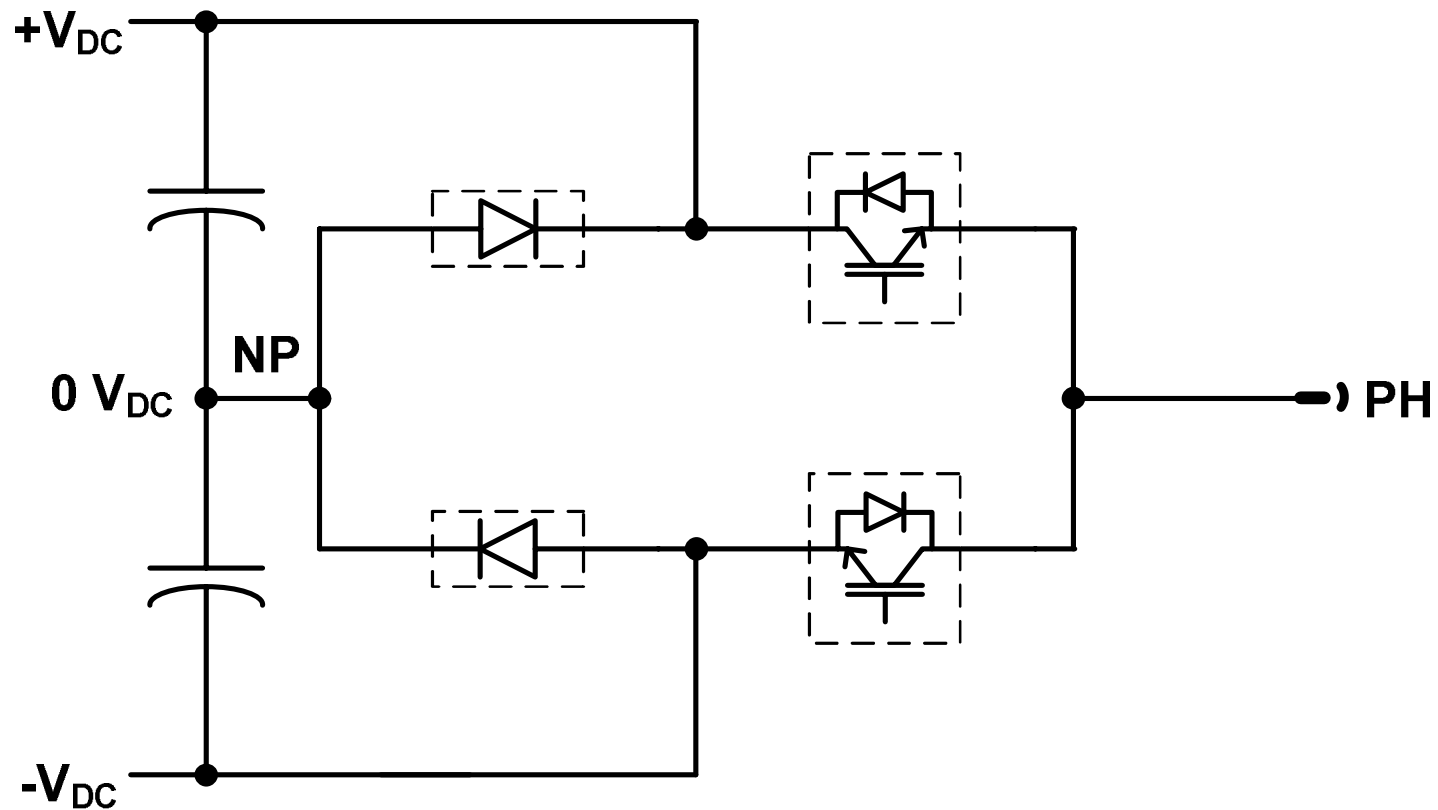

The n-level VSI topology


3-Level

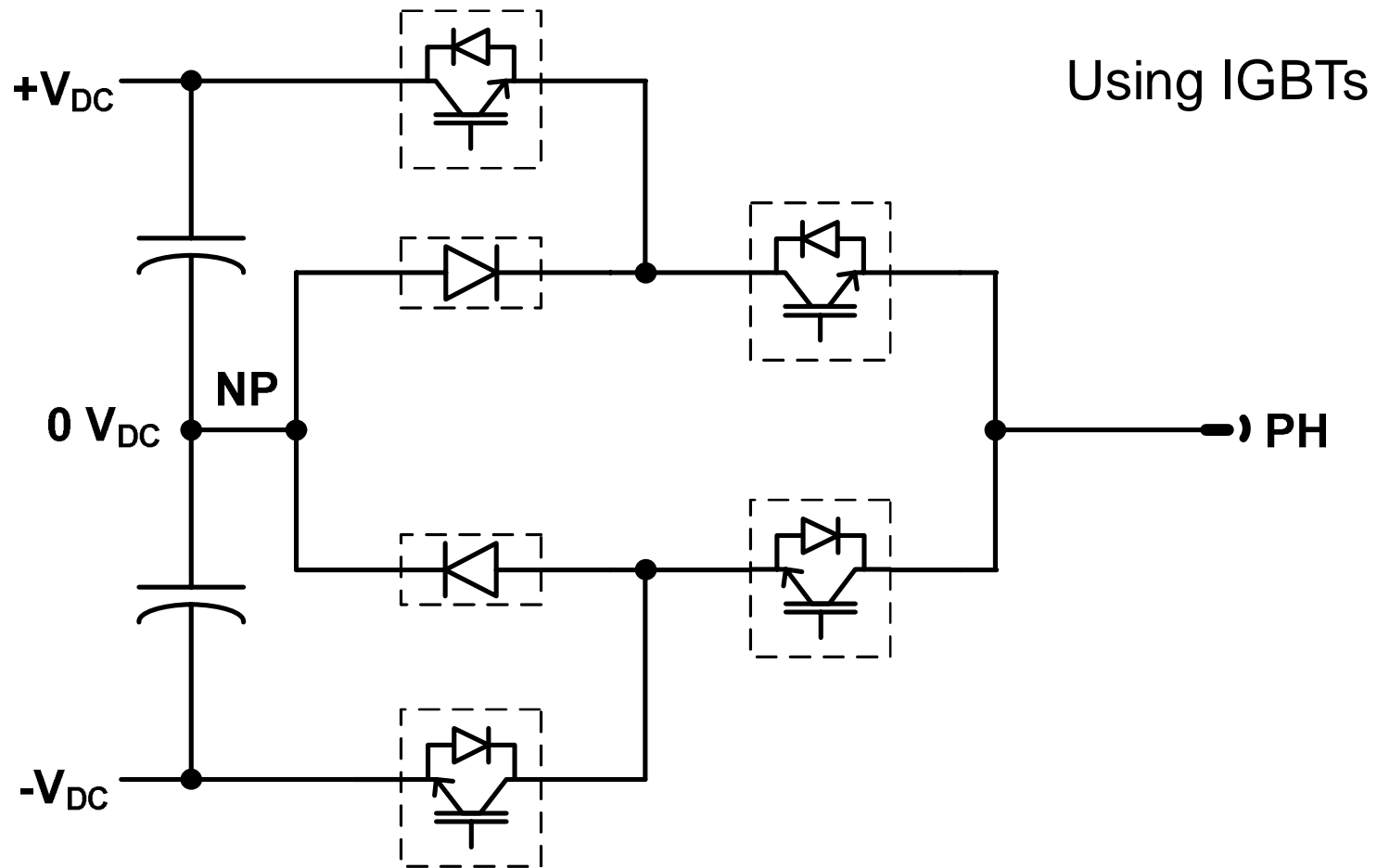

The n-level VSI topology

3-Level


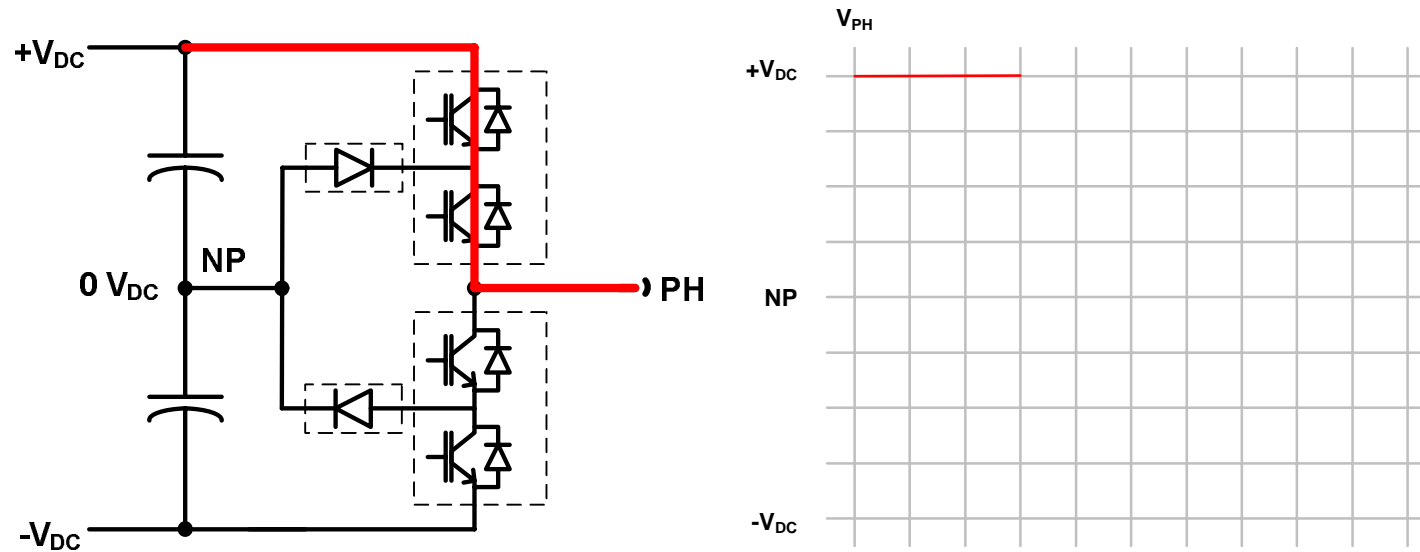
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology

3-Level

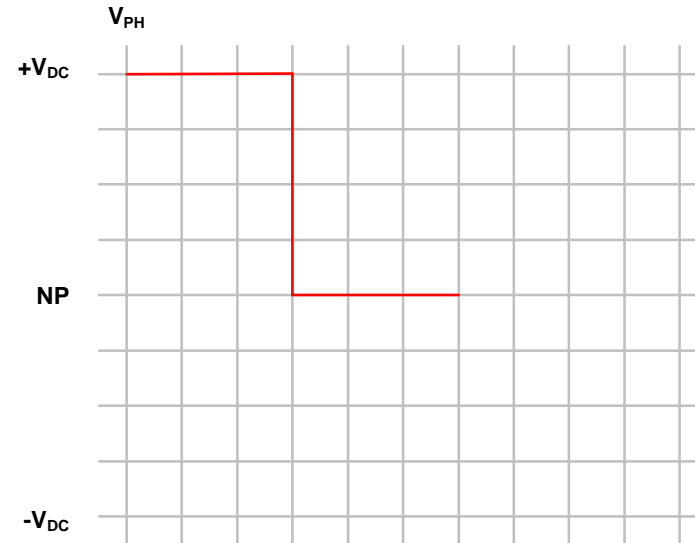
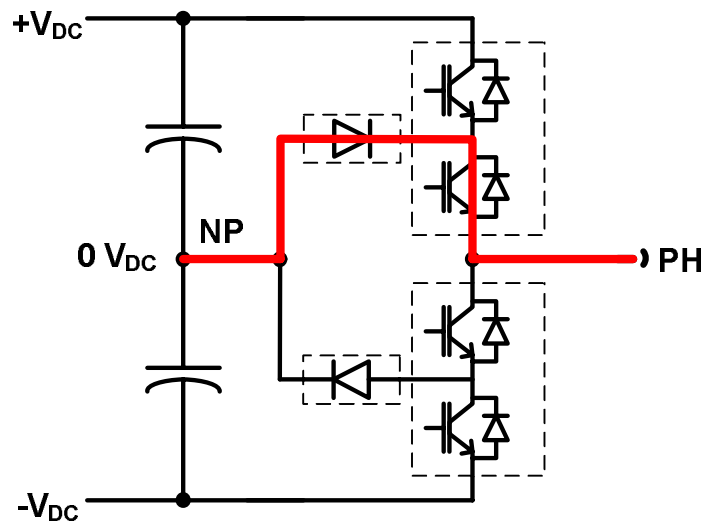
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology

3-Level

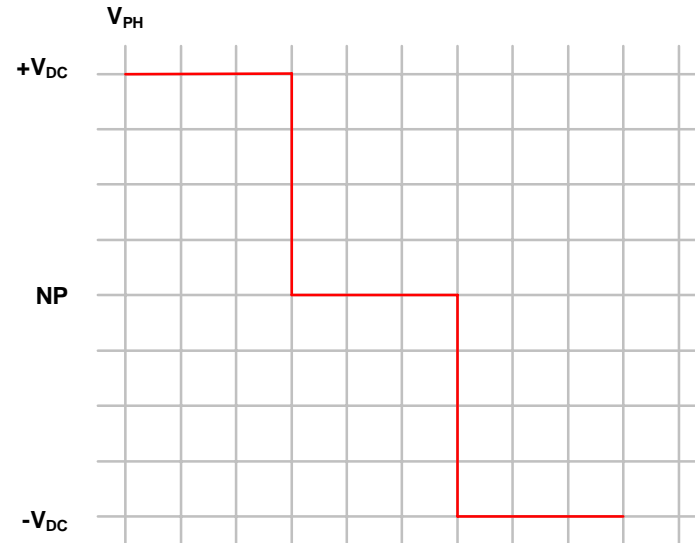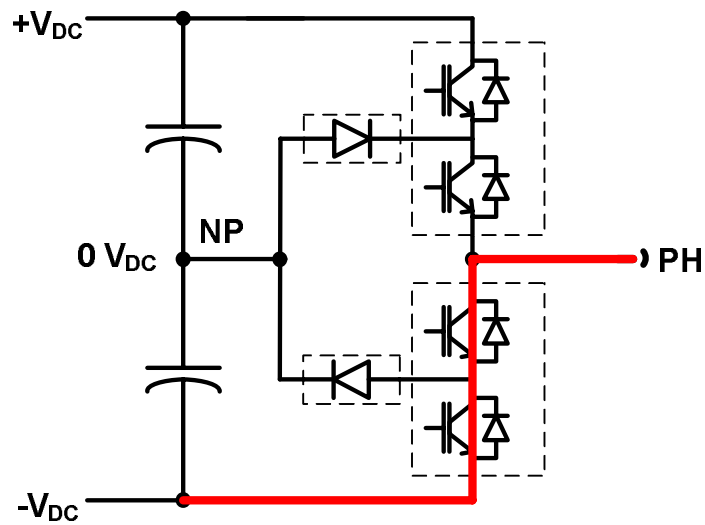
- 3-Level NPC VSI
- Phase output voltages



The n-level VSI topology

3-Level

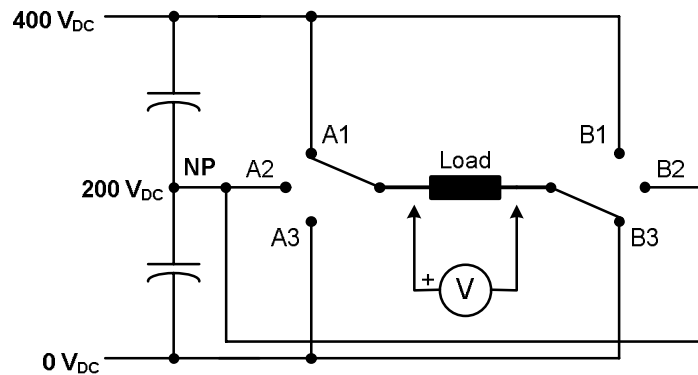- 3-Level NPC VSI
- Phase output voltages



	B1	B2	B3
A1	0	200	400
A2	-200	0	200
A3	-400	-200	0


Number of
Levels, n

3

Number of Voltage
steps, line-to-line,
 $2n-1$

5

3-Level Waveform, Line-to-Line

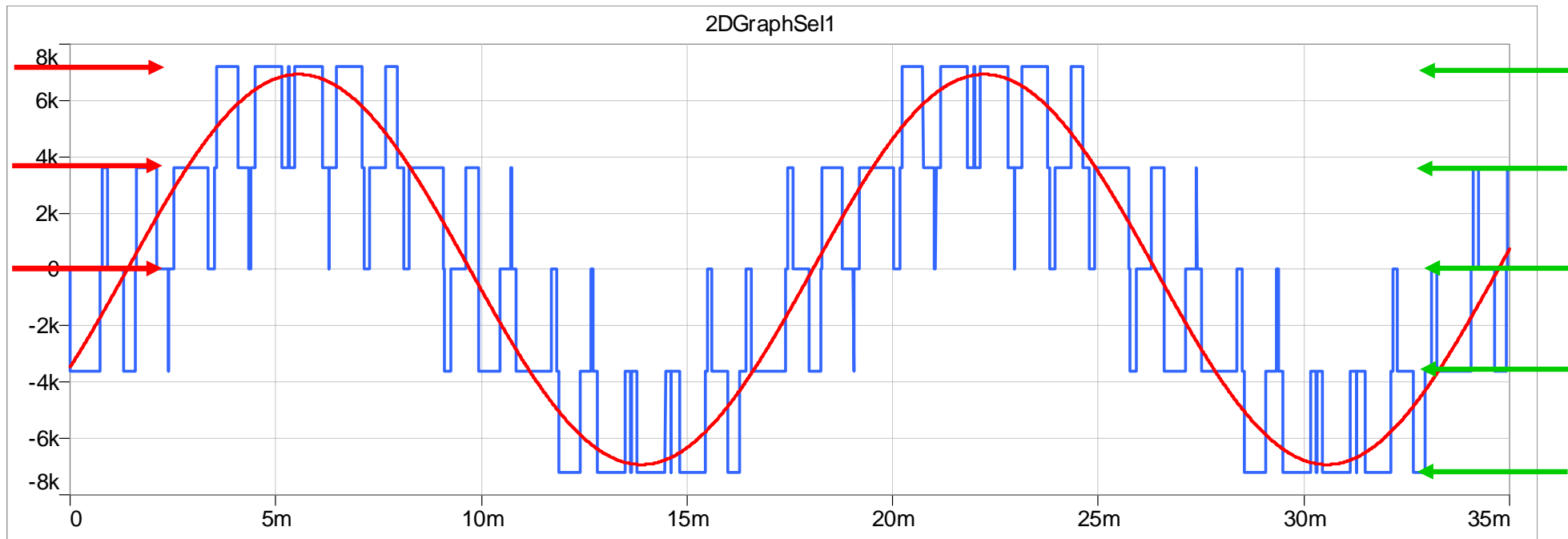


3-Levels

5-Steps

The n-level VSI topology



5-Level

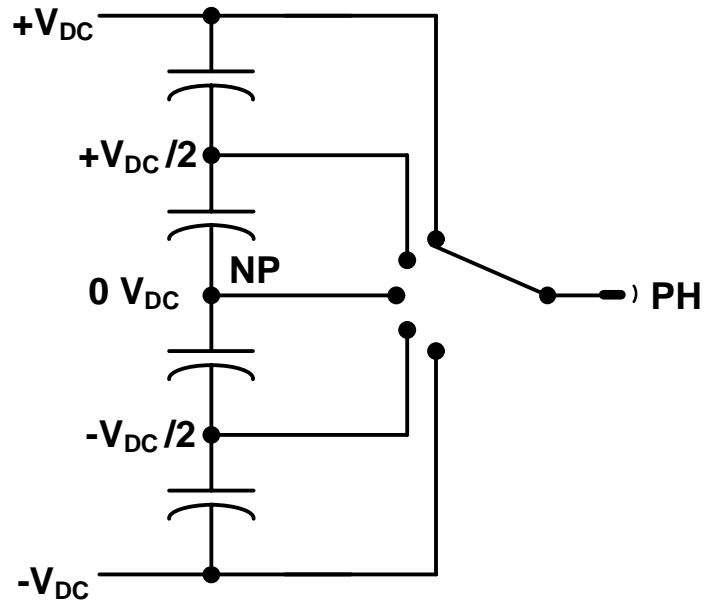

The n-level VSI topology

5-Level

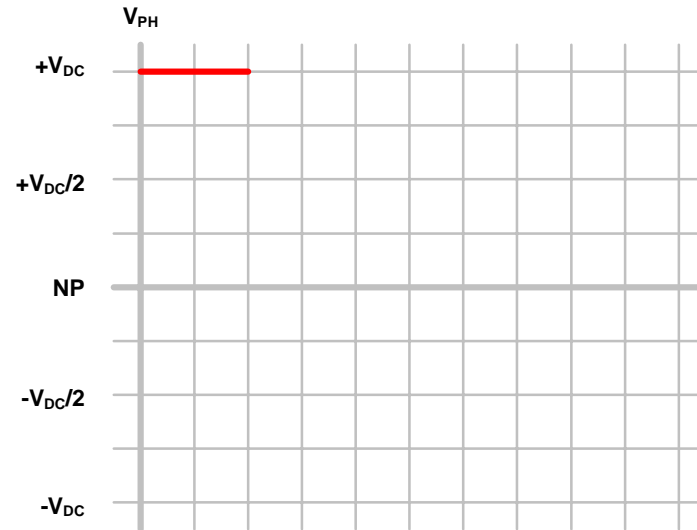
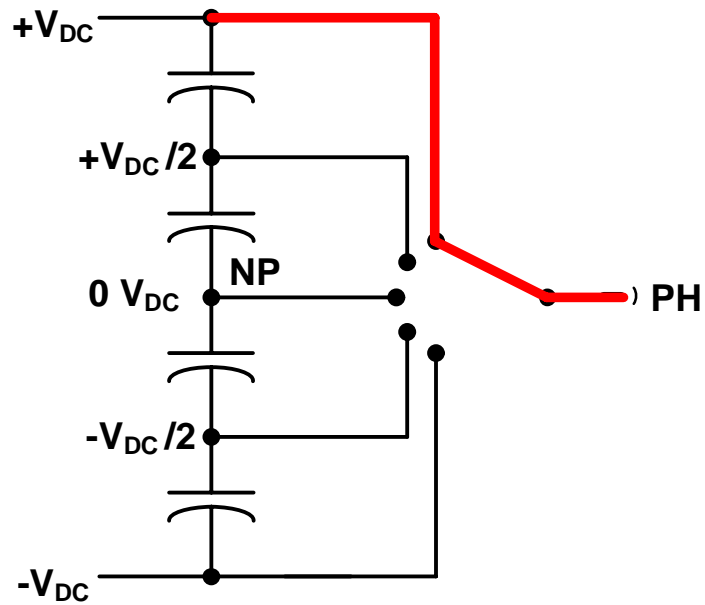
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

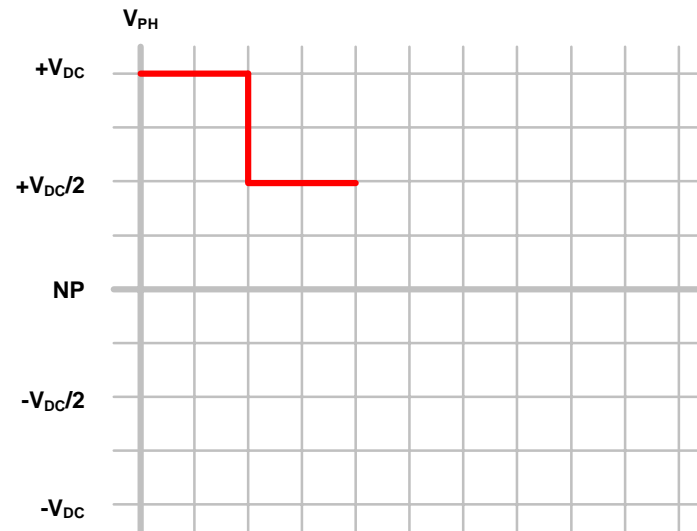
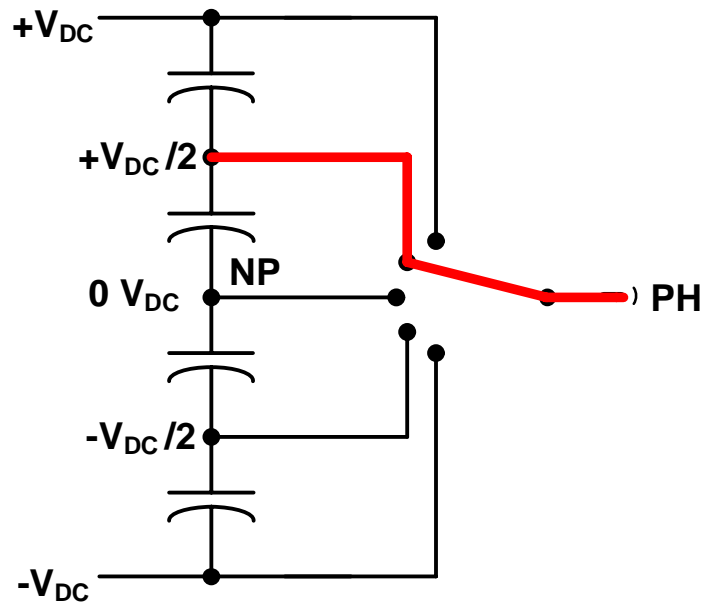
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

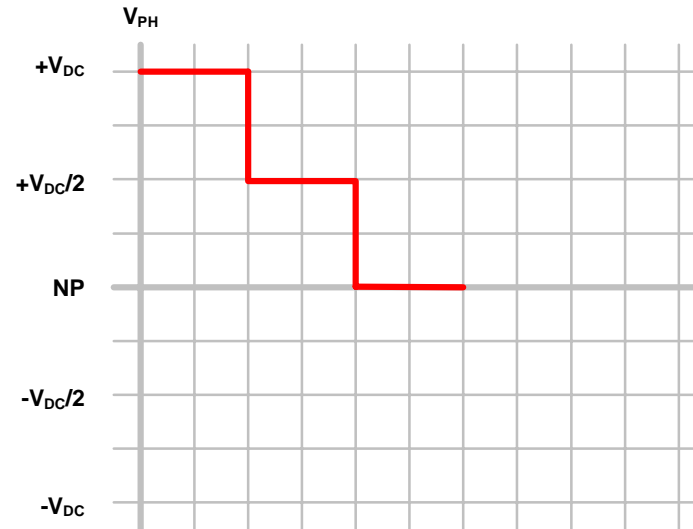
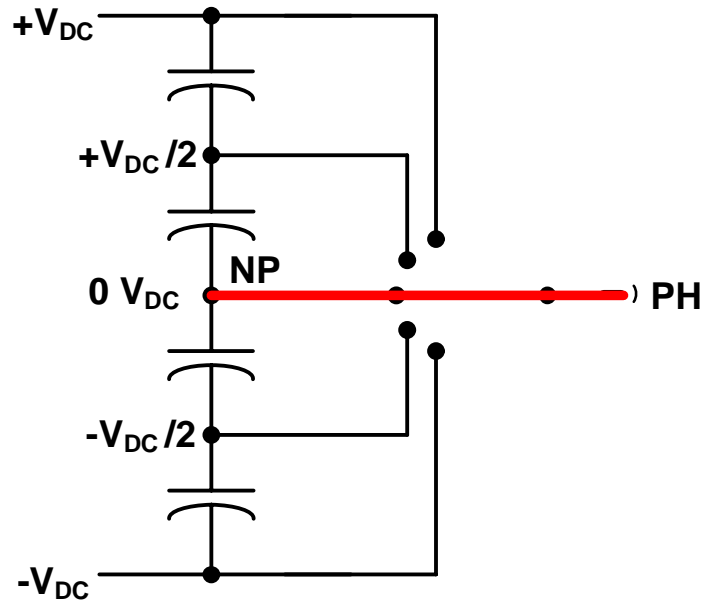
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

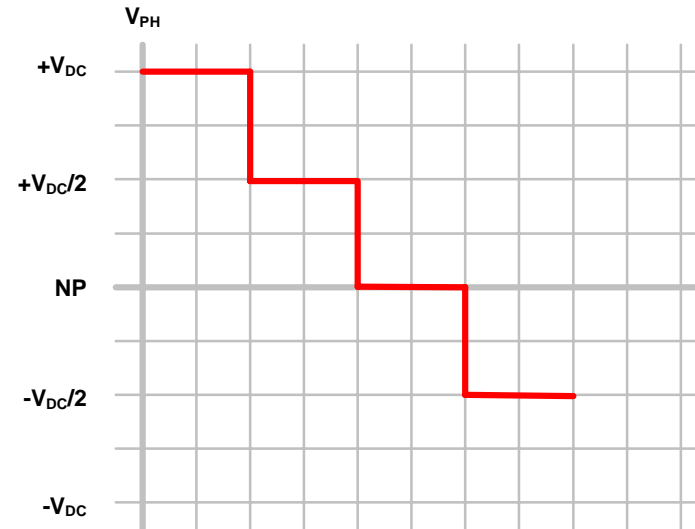
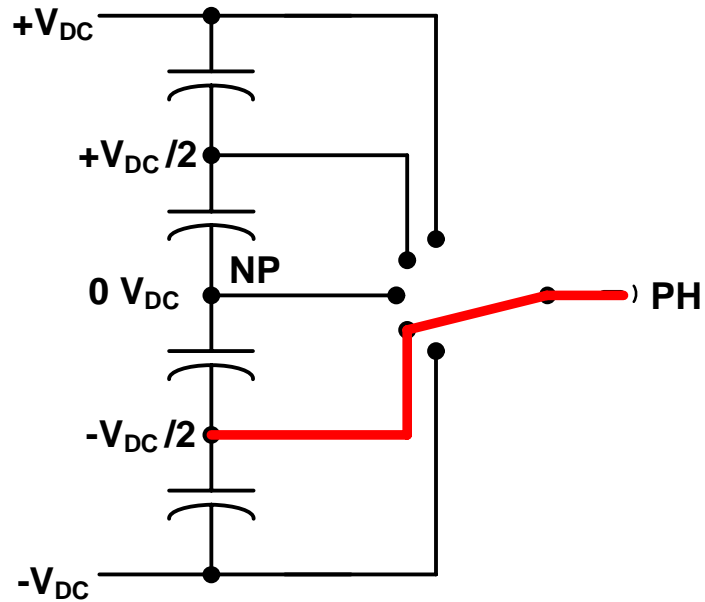
- 5-Level ANPC VSI
- Phase output voltages




The n-level VSI topology

5-Level

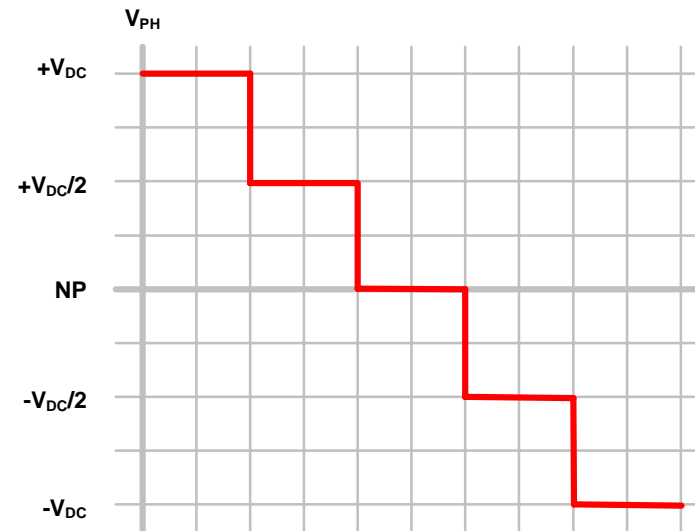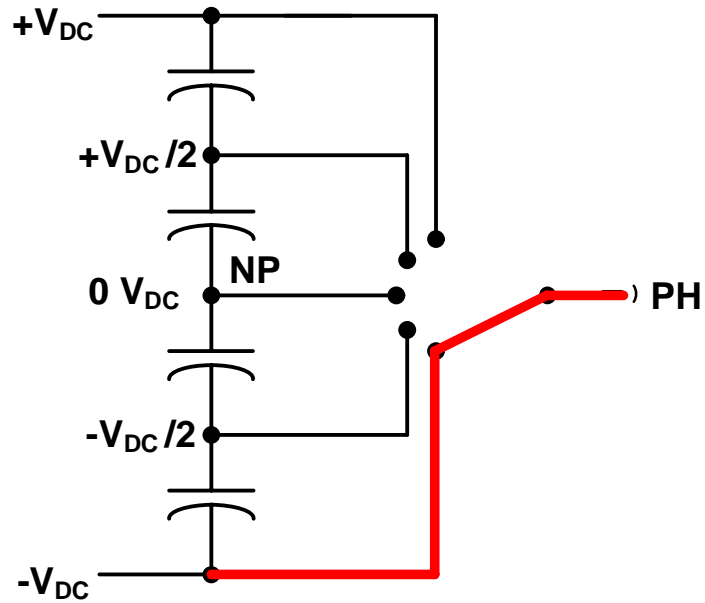- 5-Level ANPC VSI
- Phase output voltages




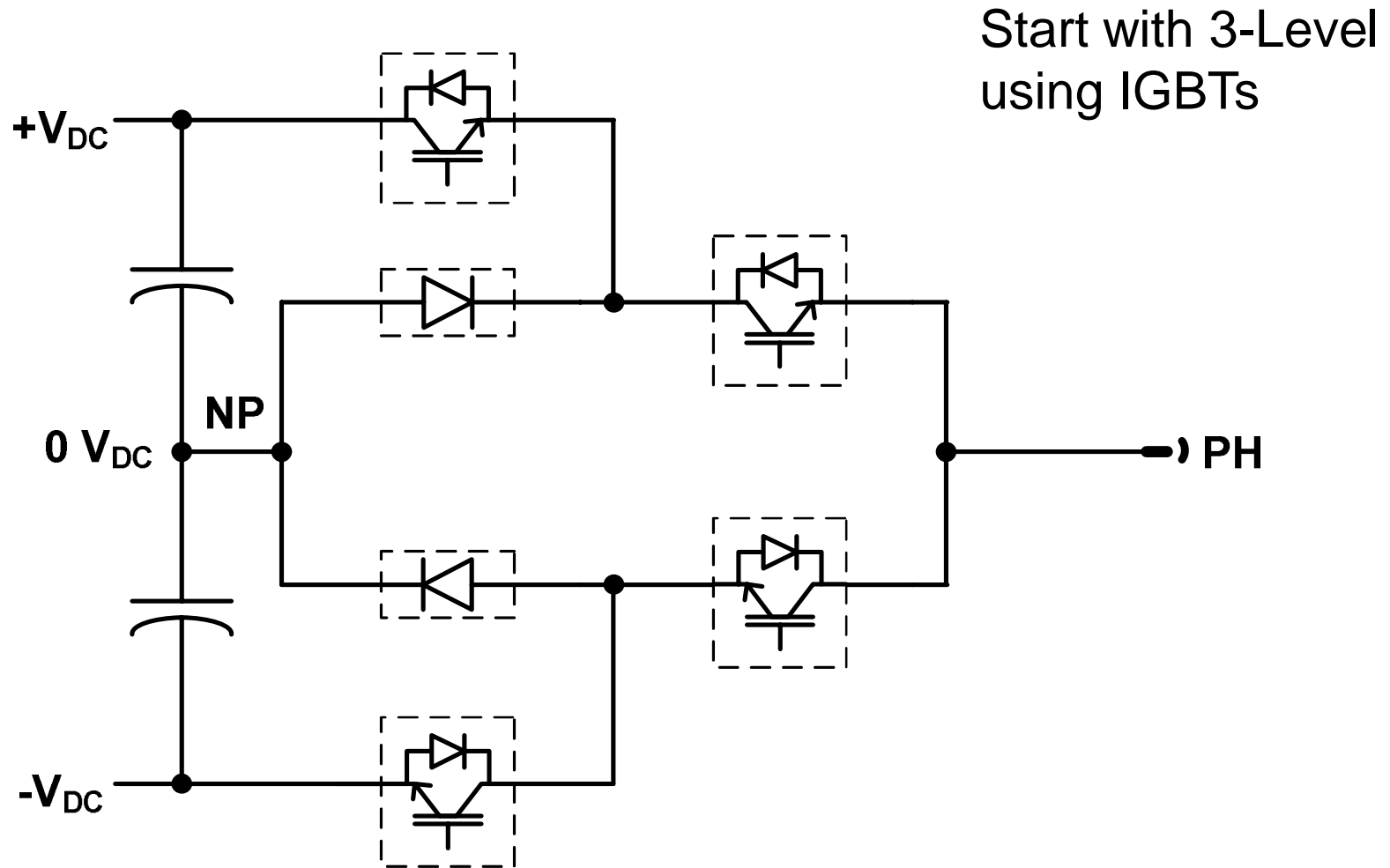The n-level VSI topology Going from 3-Level to 5-Level




The n-level VSI topology

Going from 3-Level to 5-Level

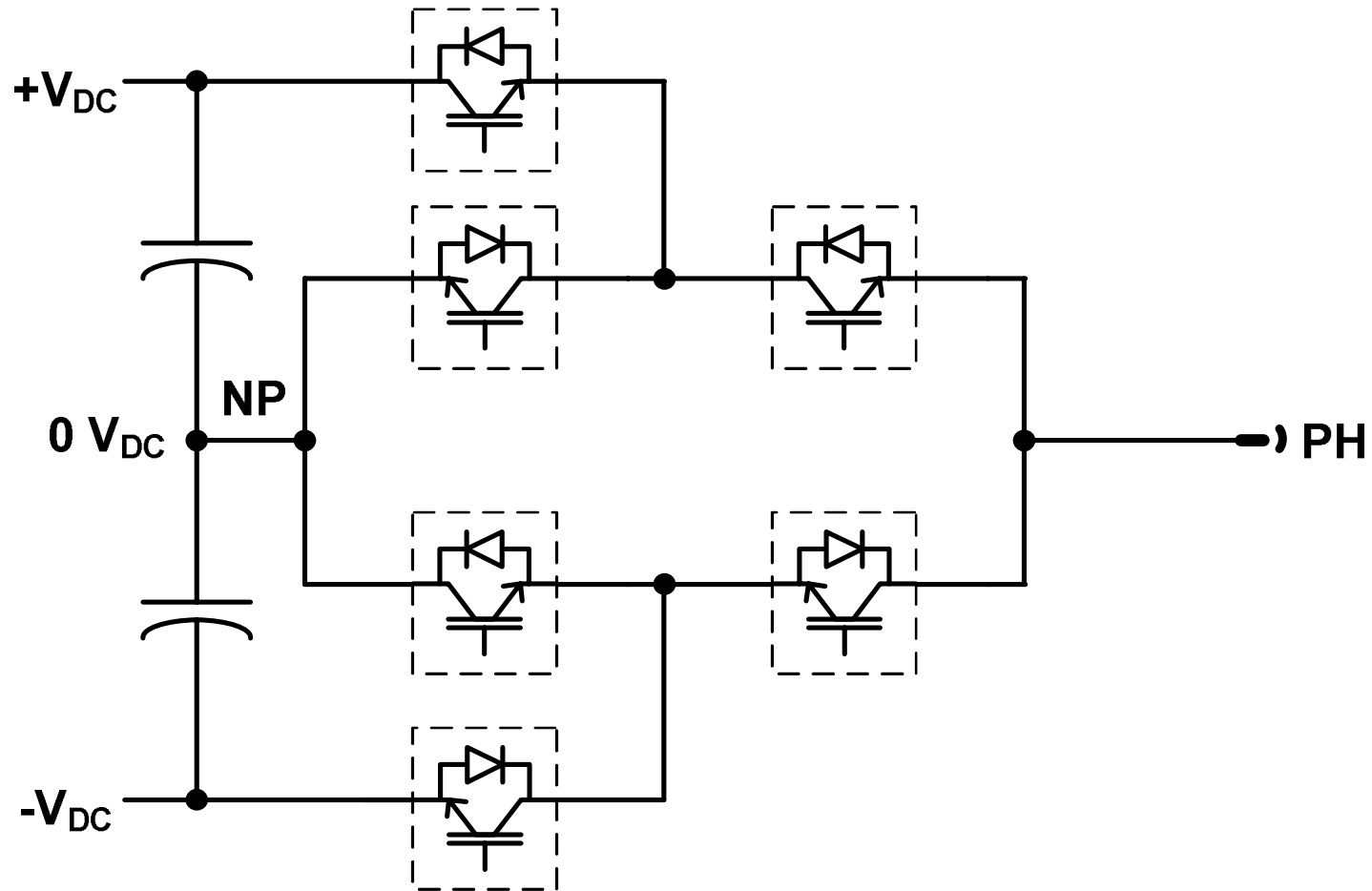


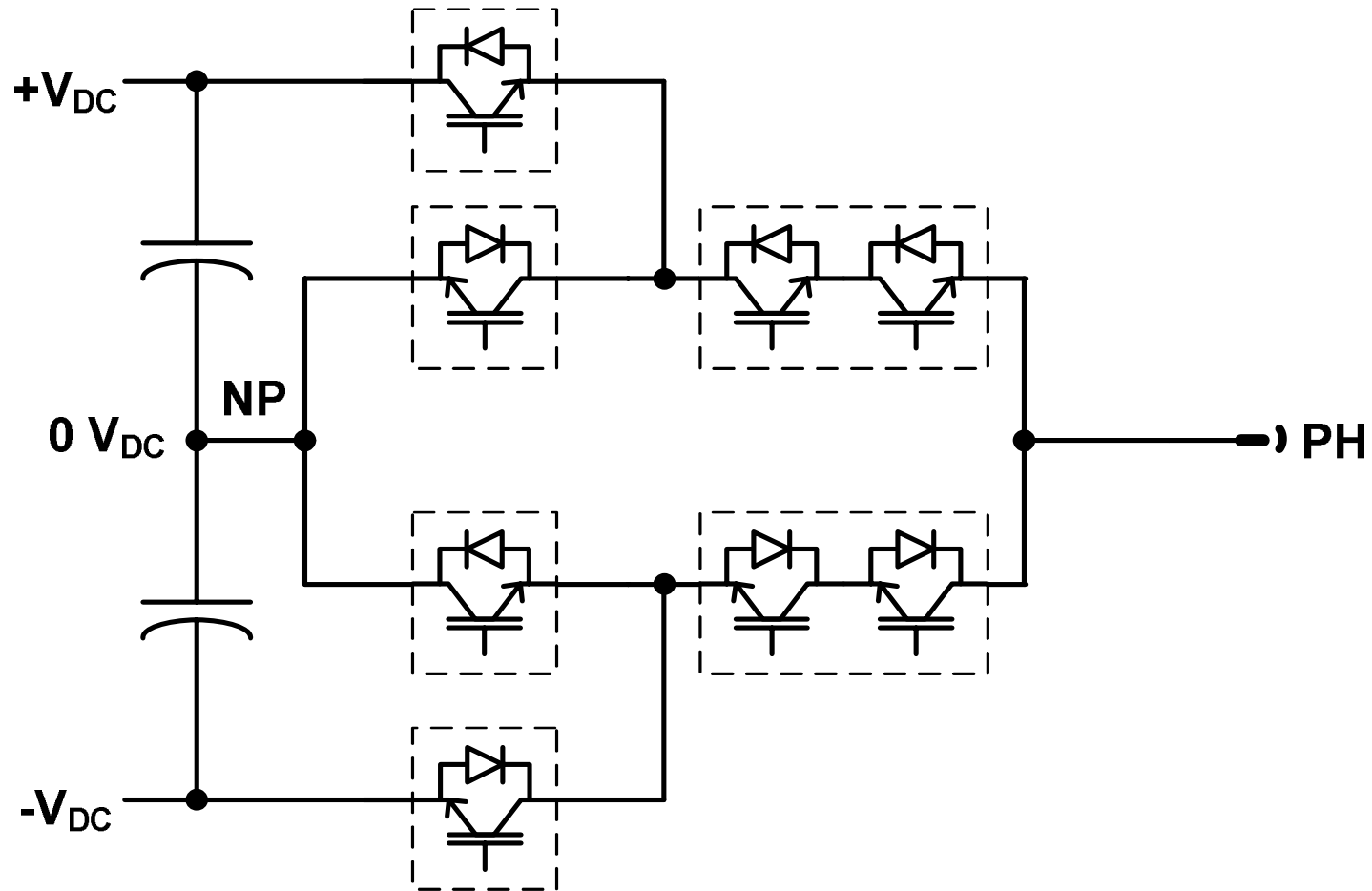The n-level VSI topology Going from 3-Level to 5-Level



The n-level VSI topology

Going from 3-Level to 5-Level

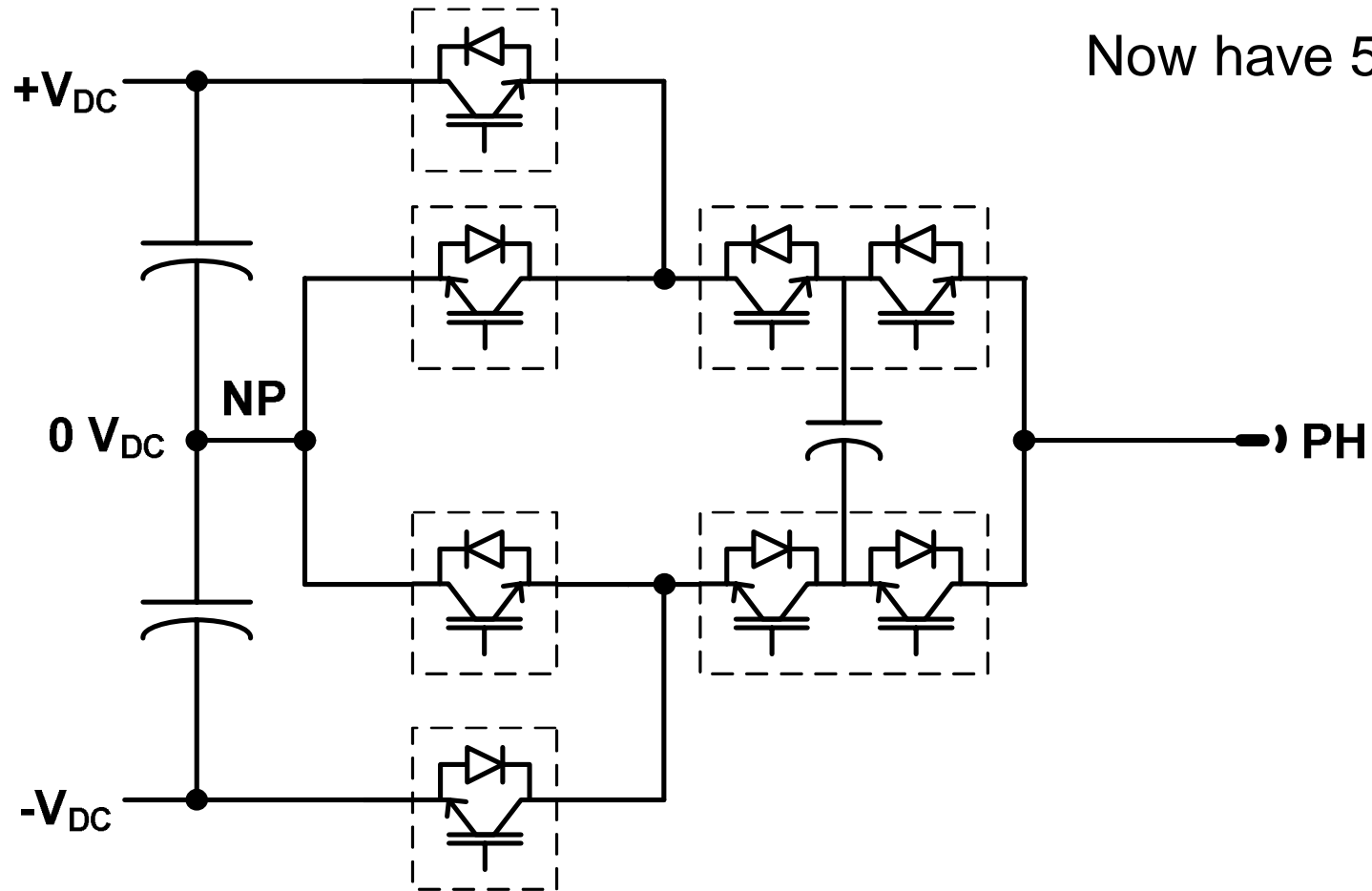


Added cap at $V_{dc}/2$

Now have 5-Level

The n-level VSI topology



Going from 3-Level to 5-Level

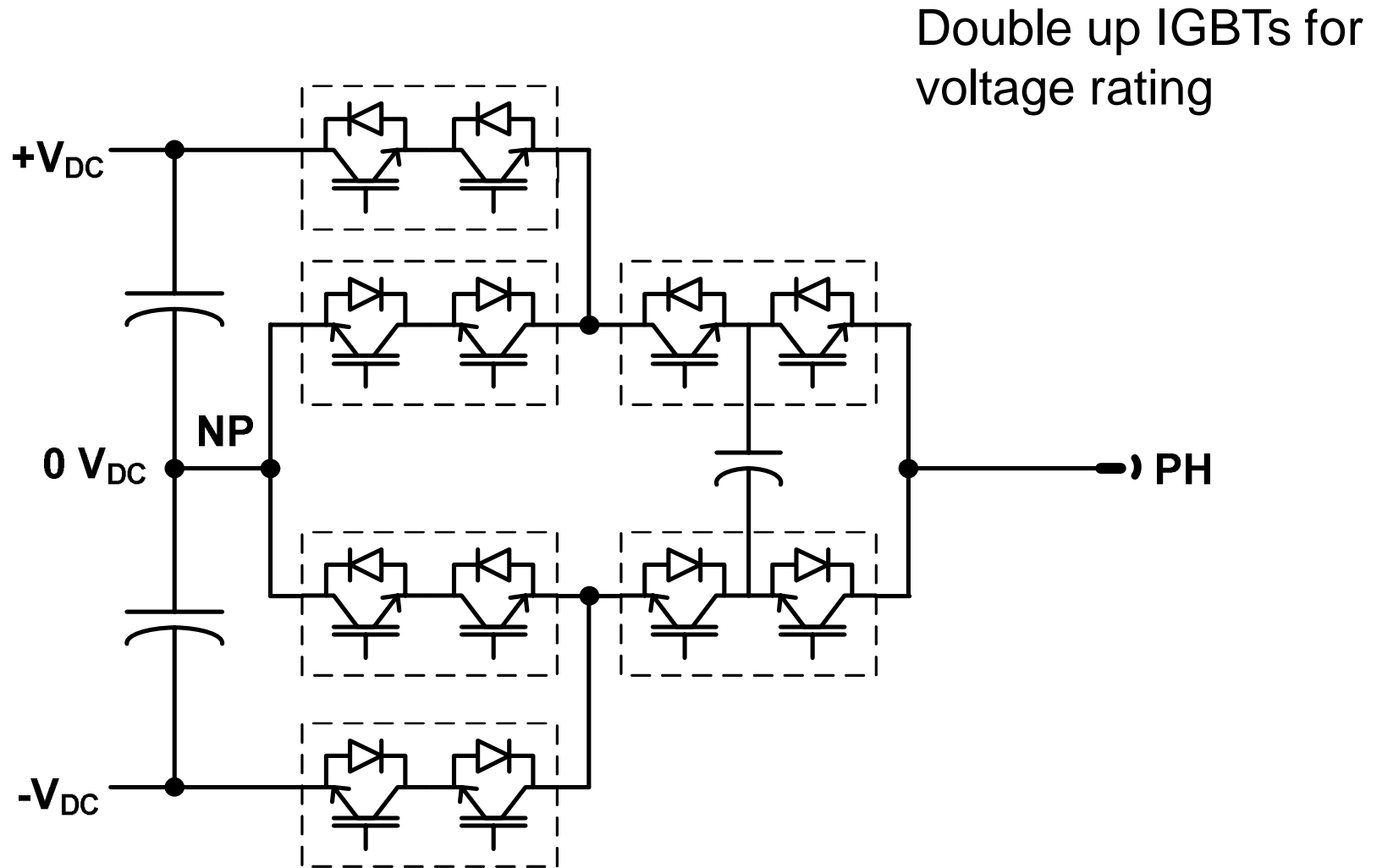

The n-level VSI topology

5-Level

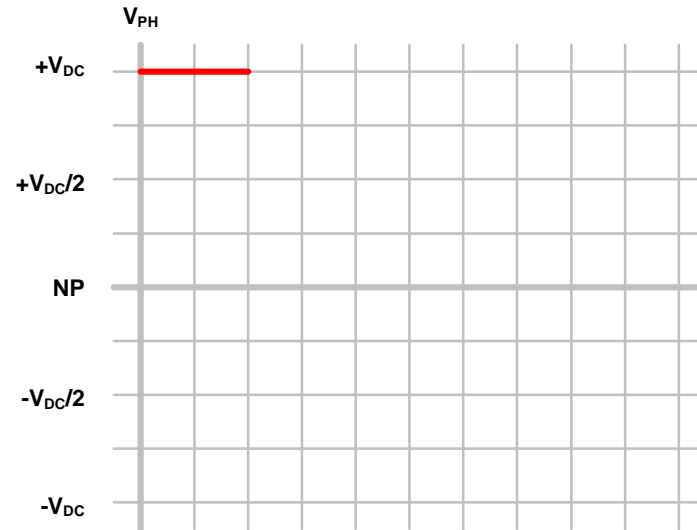
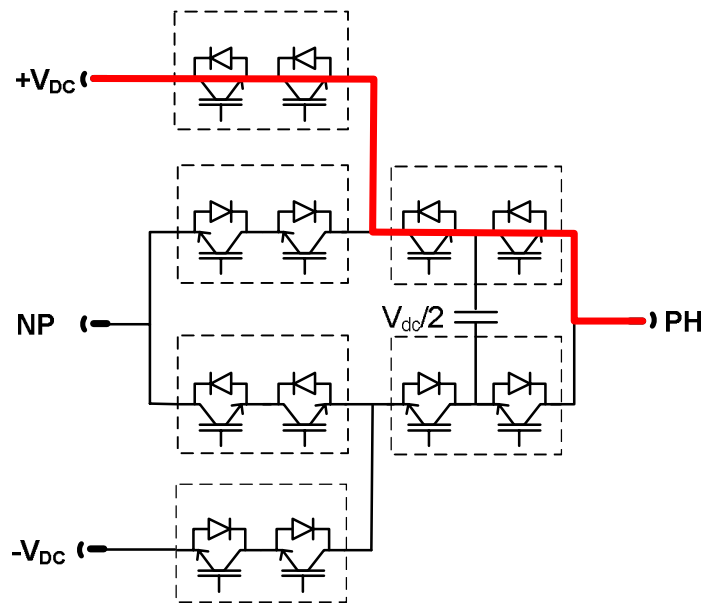
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

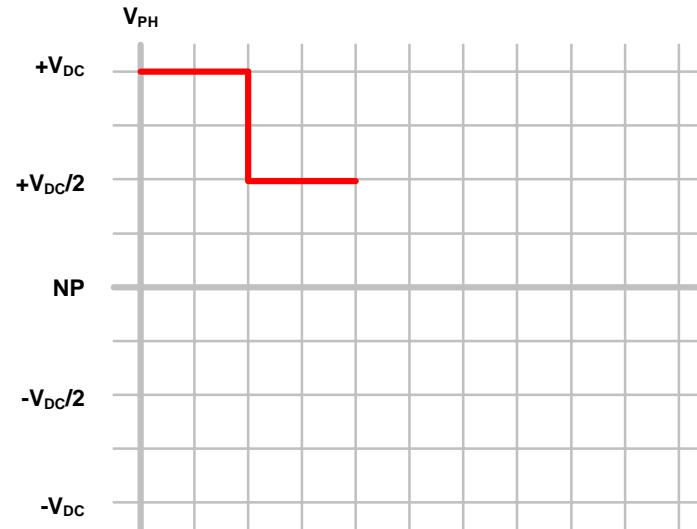
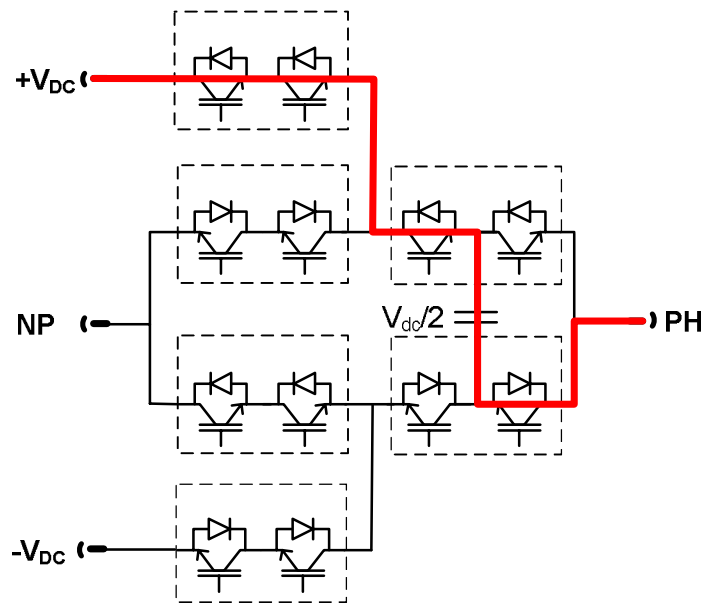
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

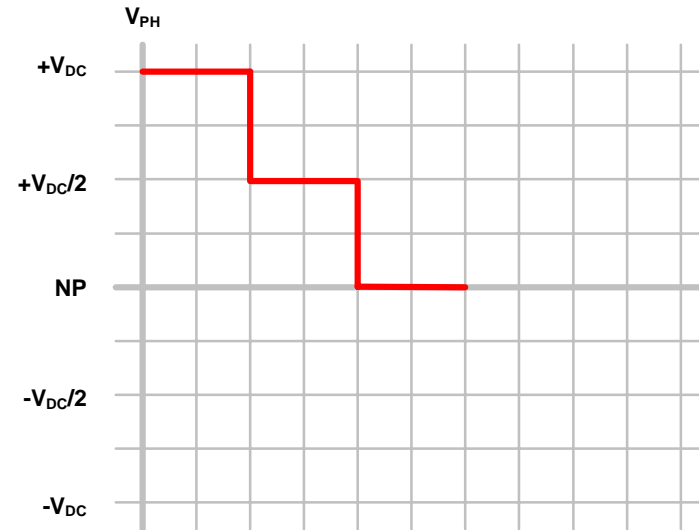
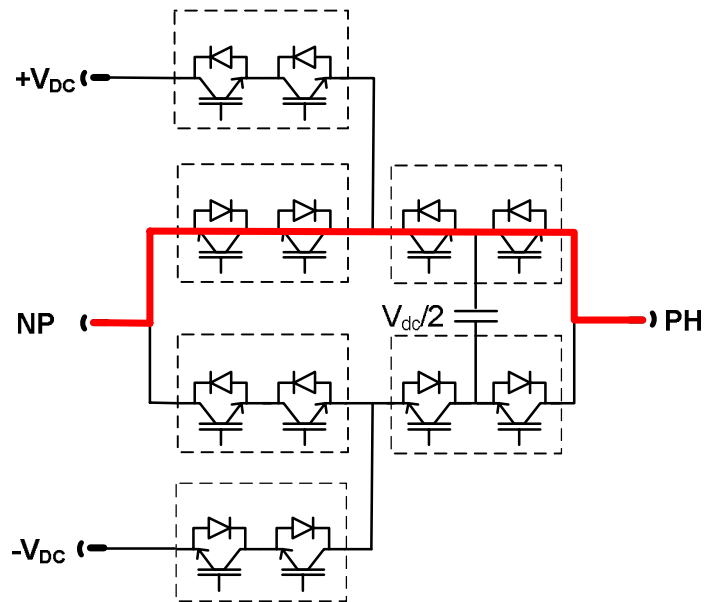
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

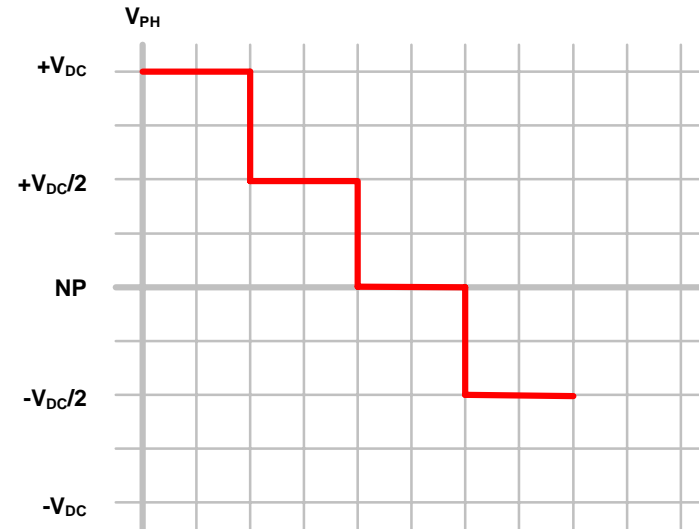
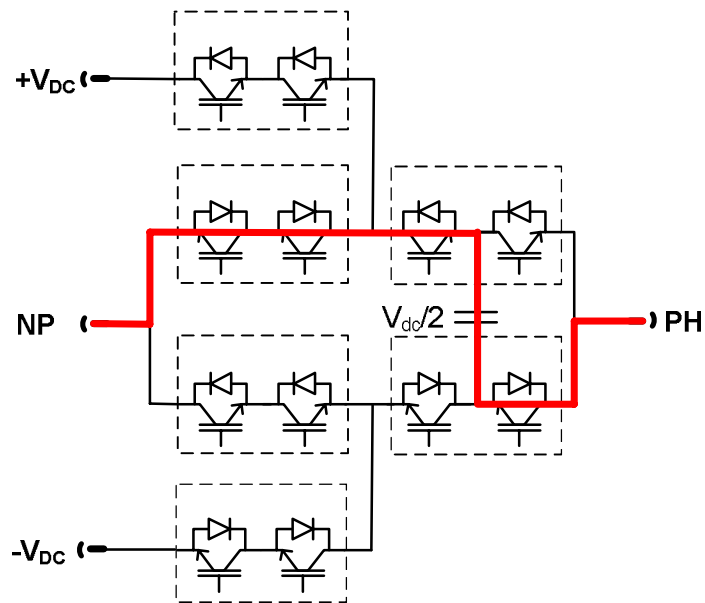
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

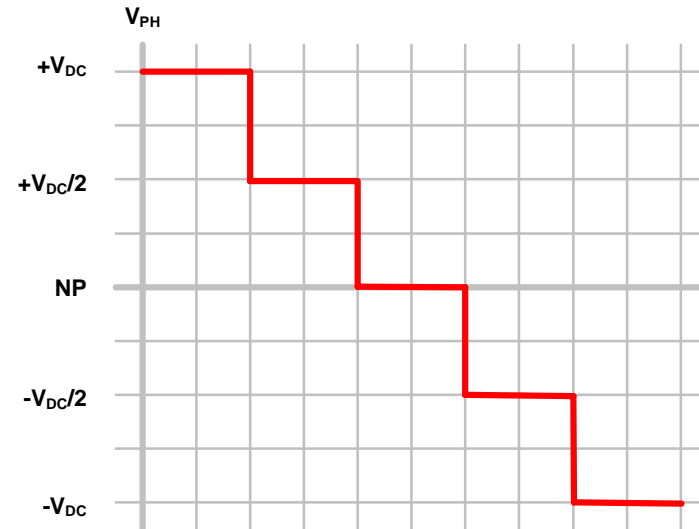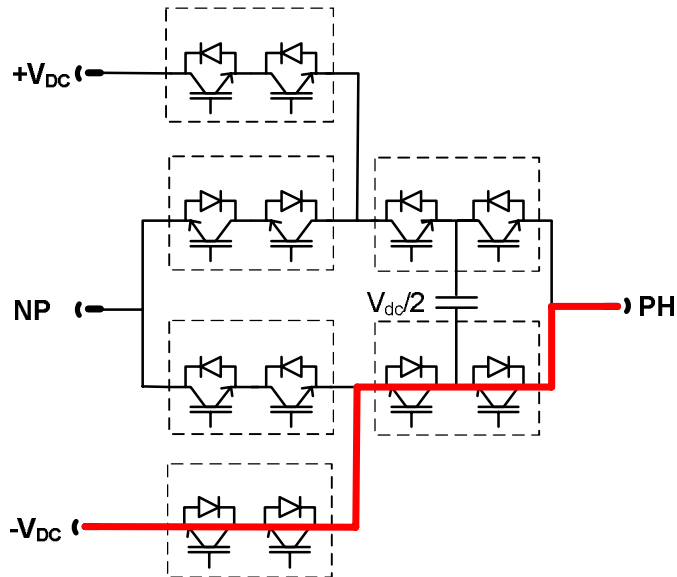
- 5-Level ANPC VSI
- Phase output voltages



The n-level VSI topology

5-Level

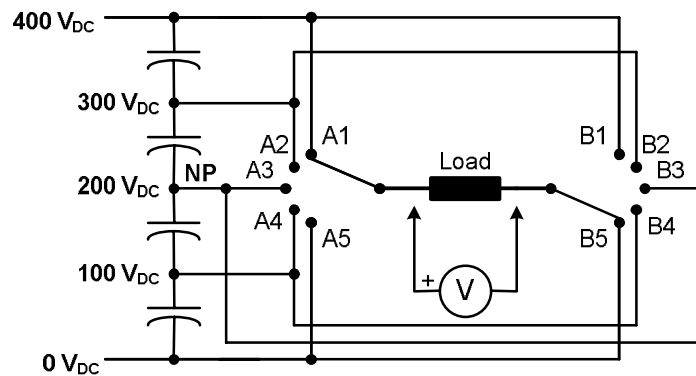- 5-Level ANPC VSI
- Phase output voltages



	B1	B2	B3	B4	B5
A1	0	100	200	300	400
A2	-100	0	100	200	300
A3	-200	-100	0	100	200
A4	-300	-200	-100	0	100
A5	-400	-300	-200	-100	0


Number of Levels, n

5

Number of Voltage steps, line-to-line, $2n-1$

9


5-Level Waveform, Line-to-Line

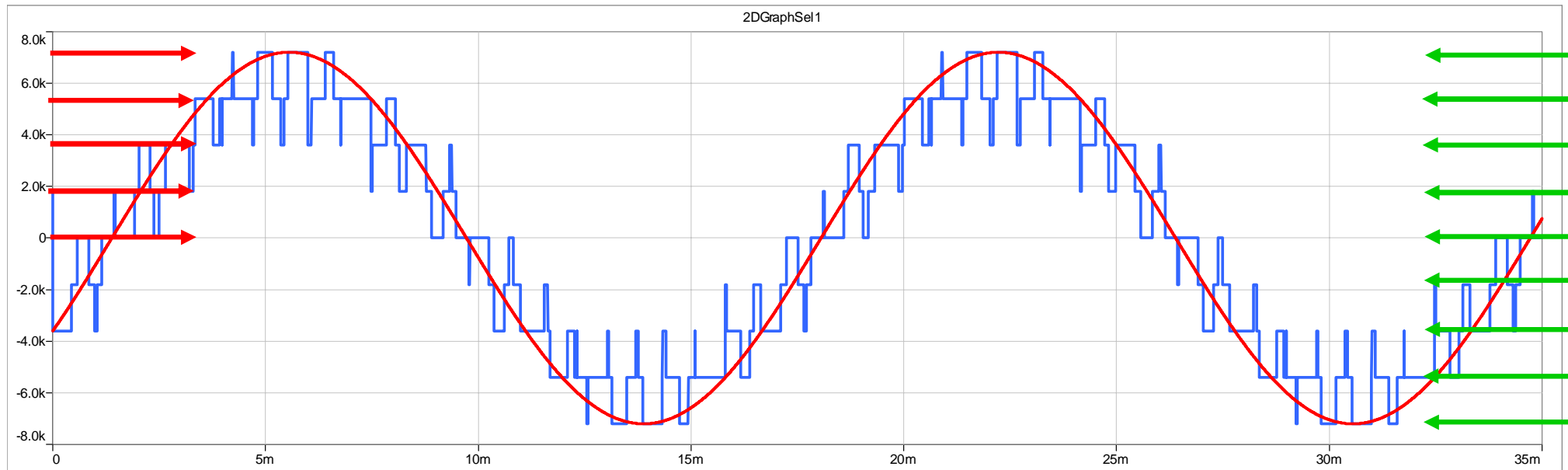


5-Levels

9-Steps


Cascaded H-Bridge

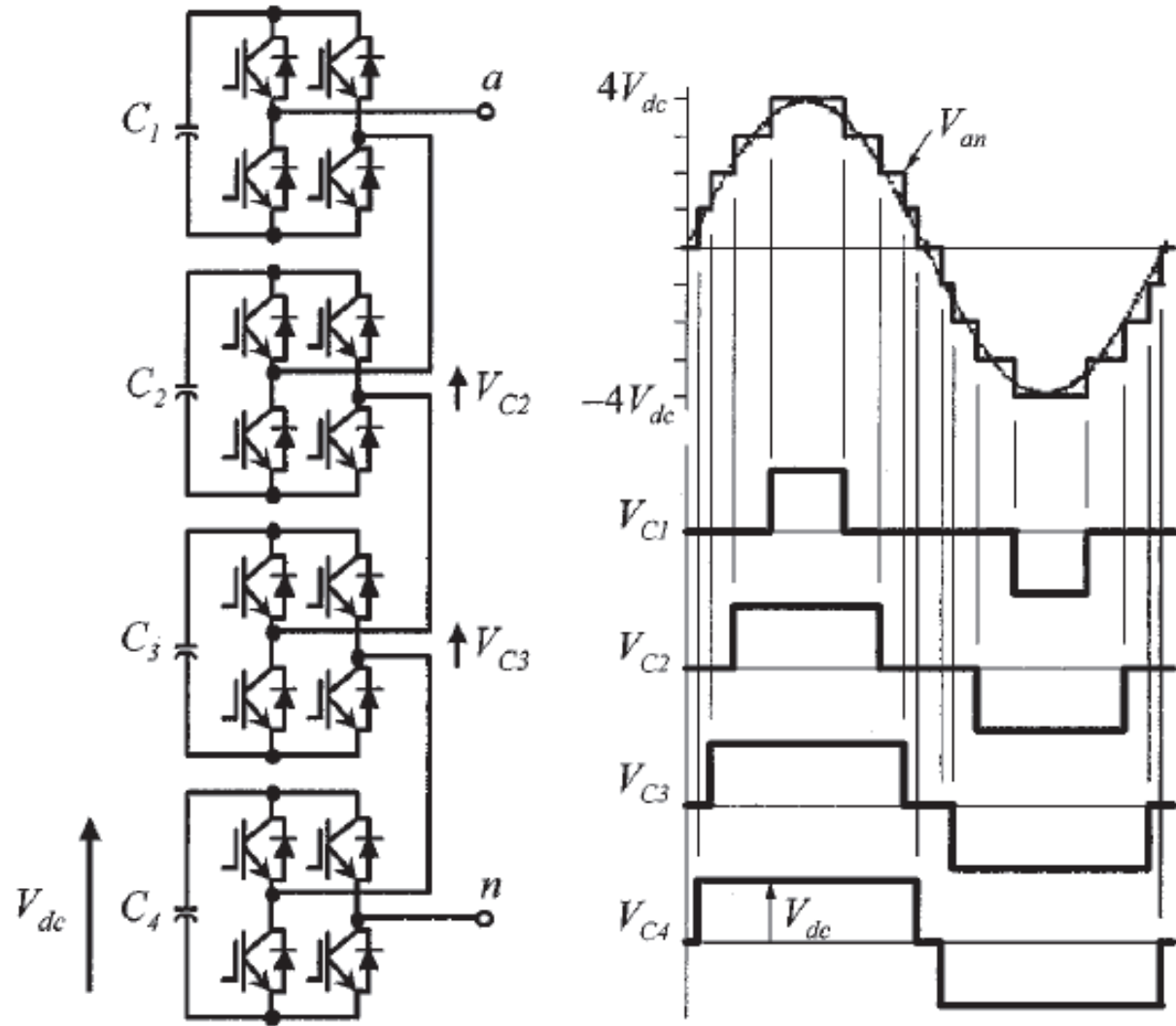


How are VSI and CSI similar?

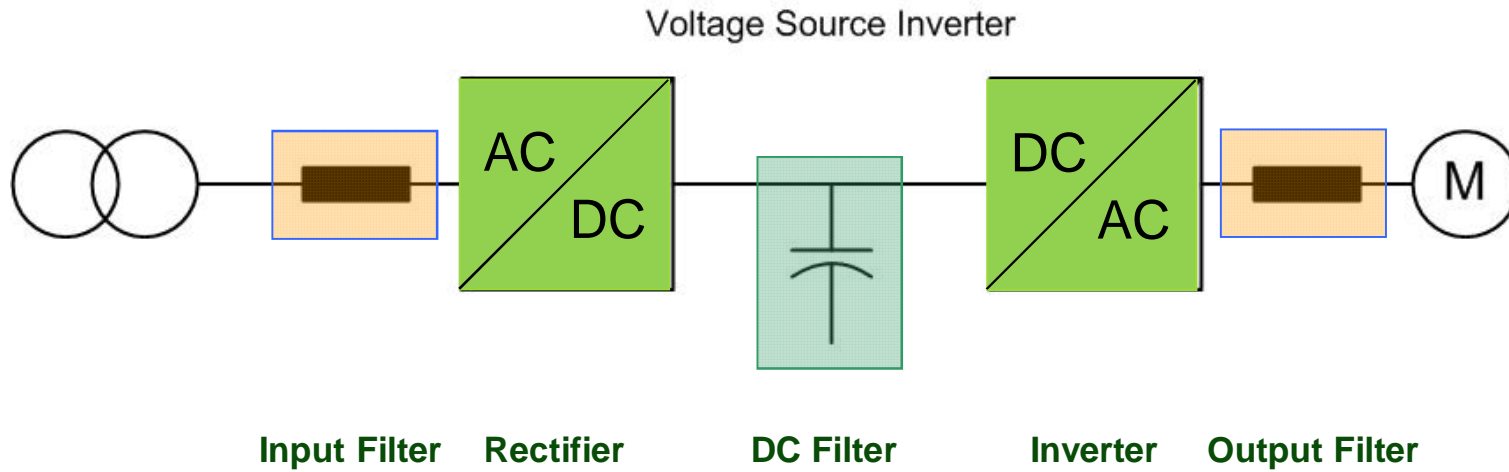


How are VSI and CSI similar?

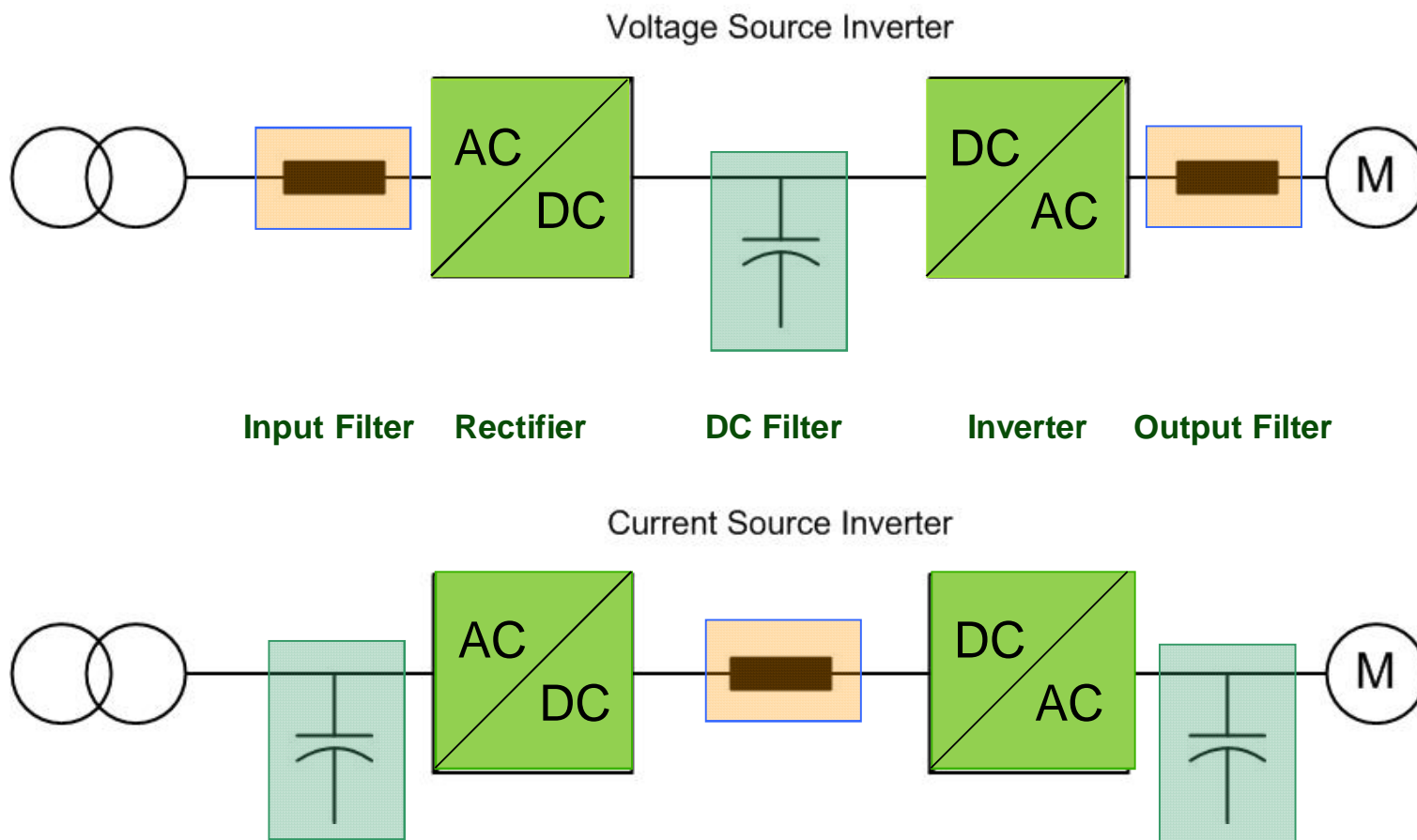

CSI, PWM Converter, Isolated

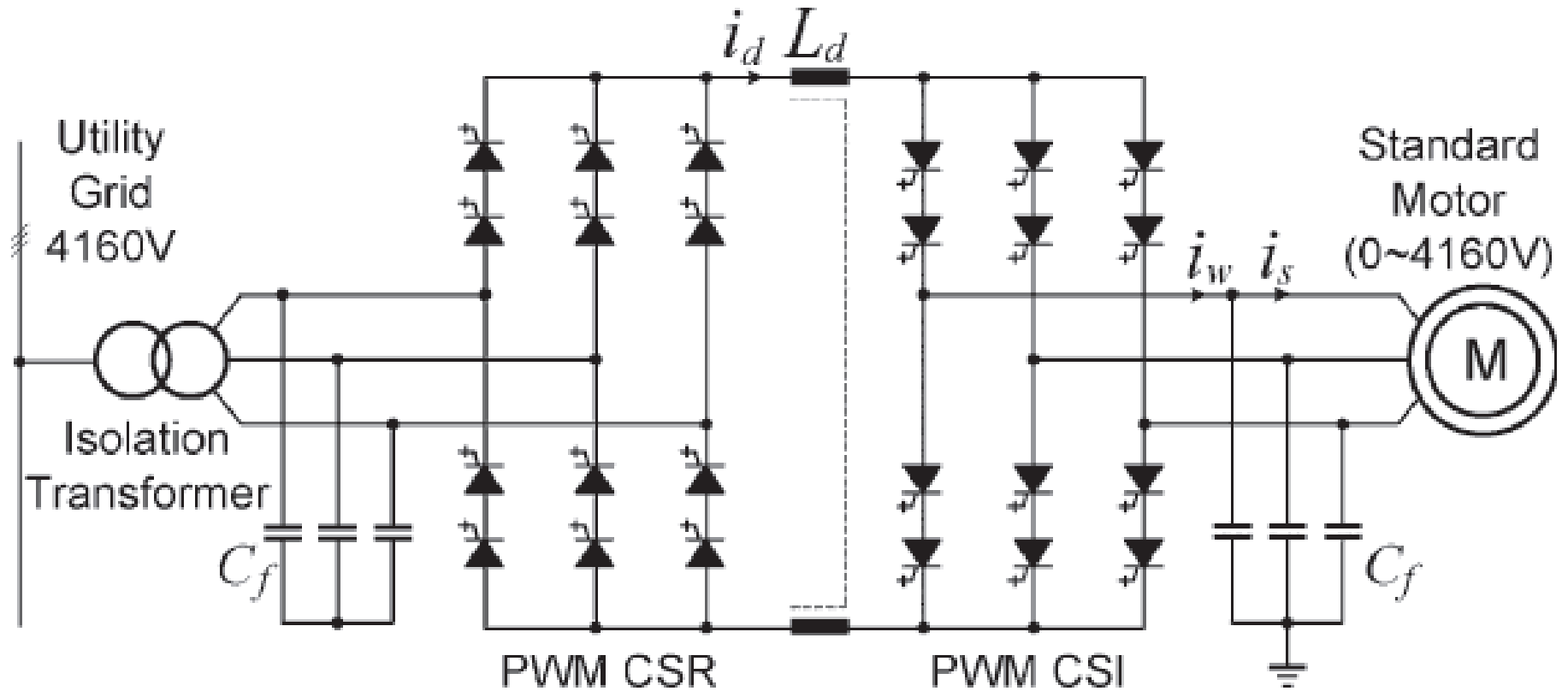


CSI, 18P Converter, Isolated

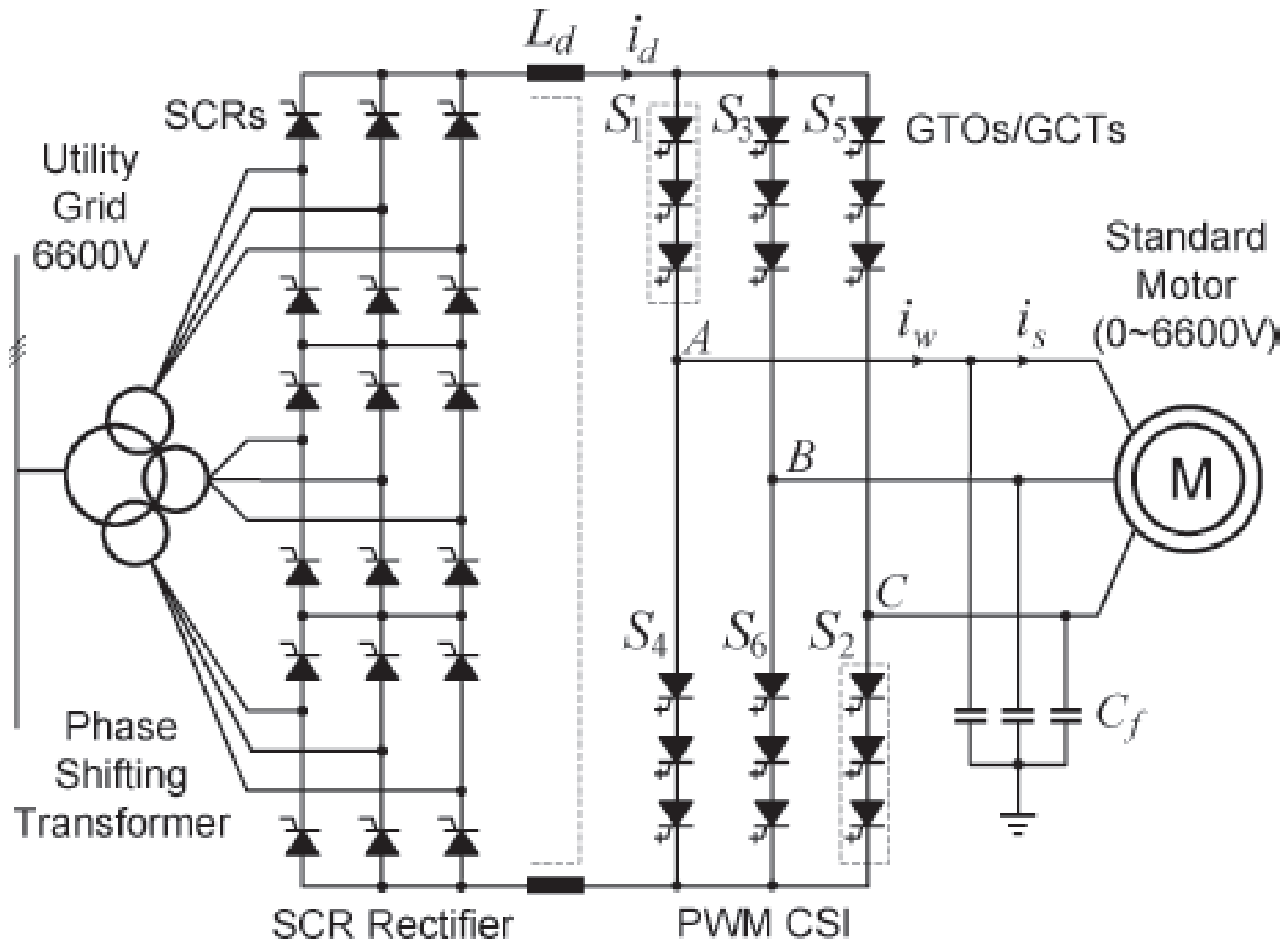


LCI, PWM Converter, Isolated



Load Commutated Inverter

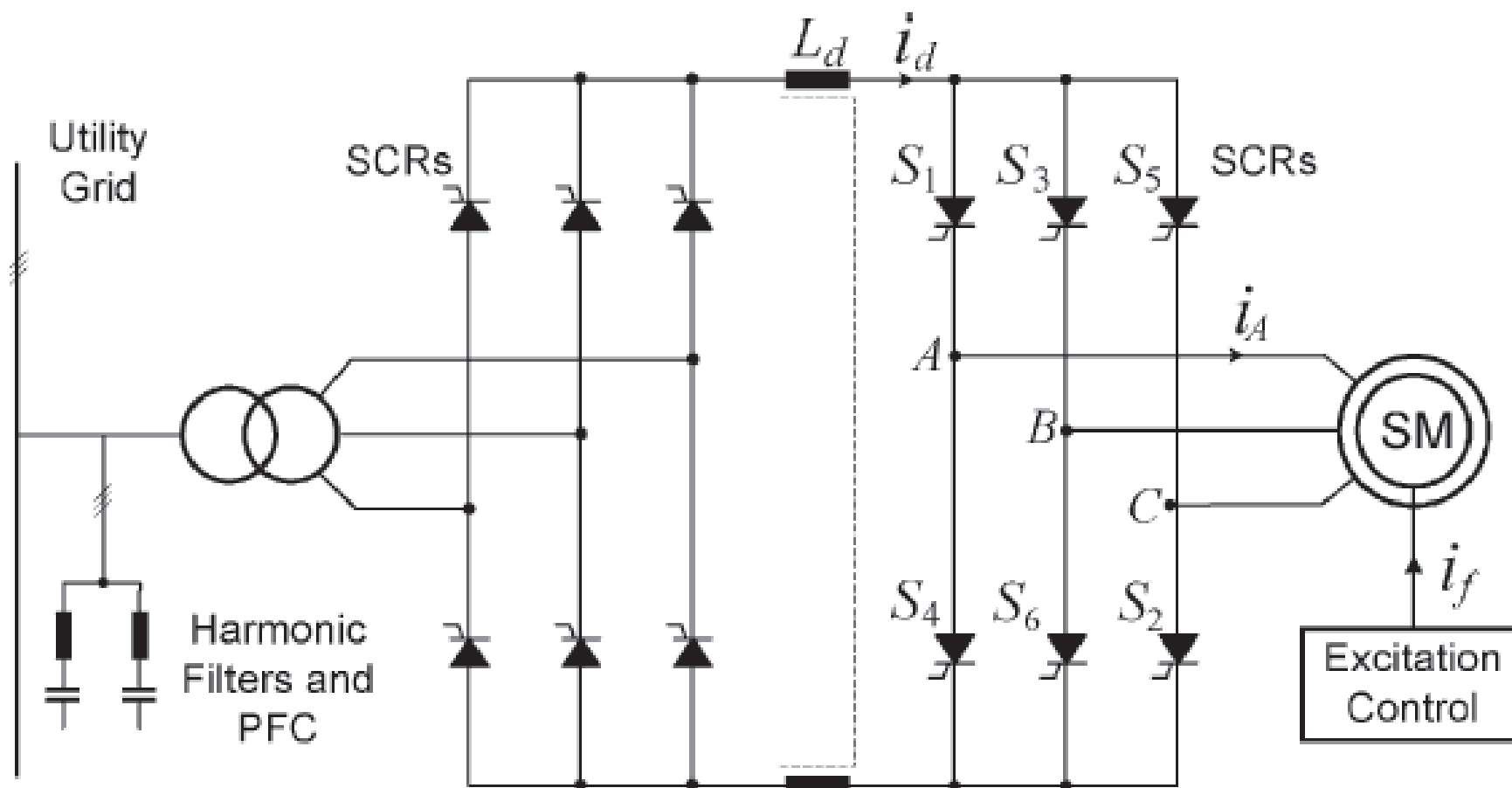



LCI, 12P Converter, Isolated

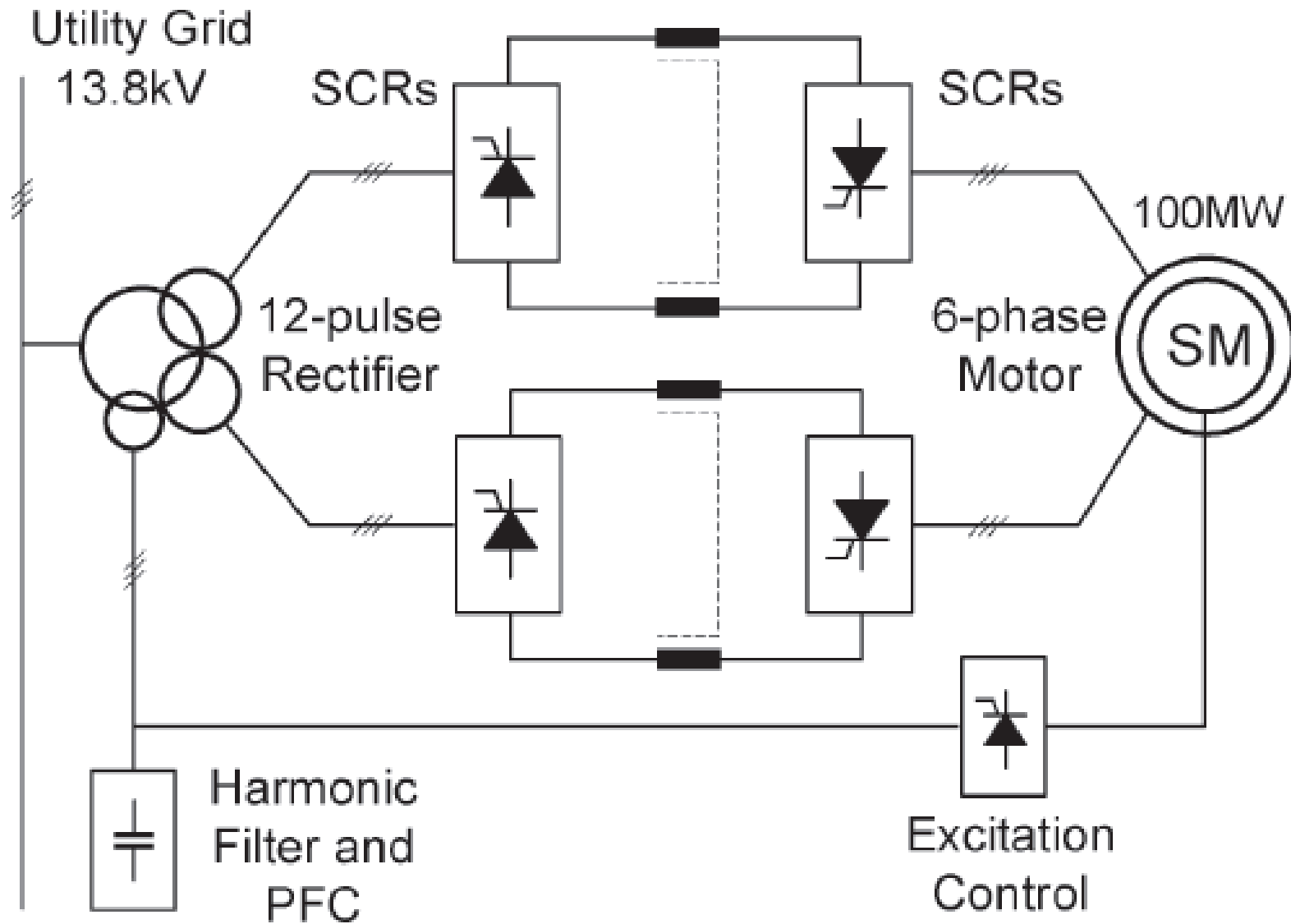

6P CCV (Cyclo-Converter)

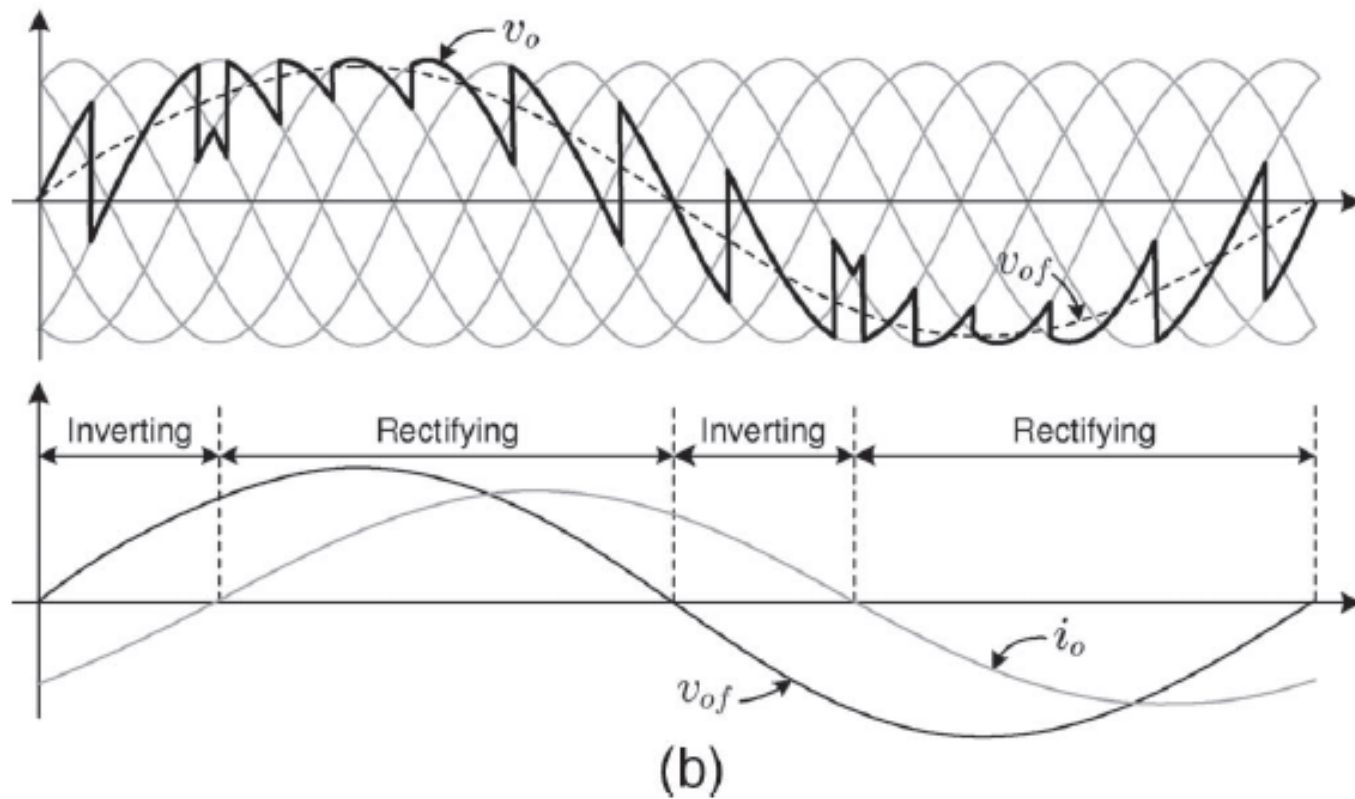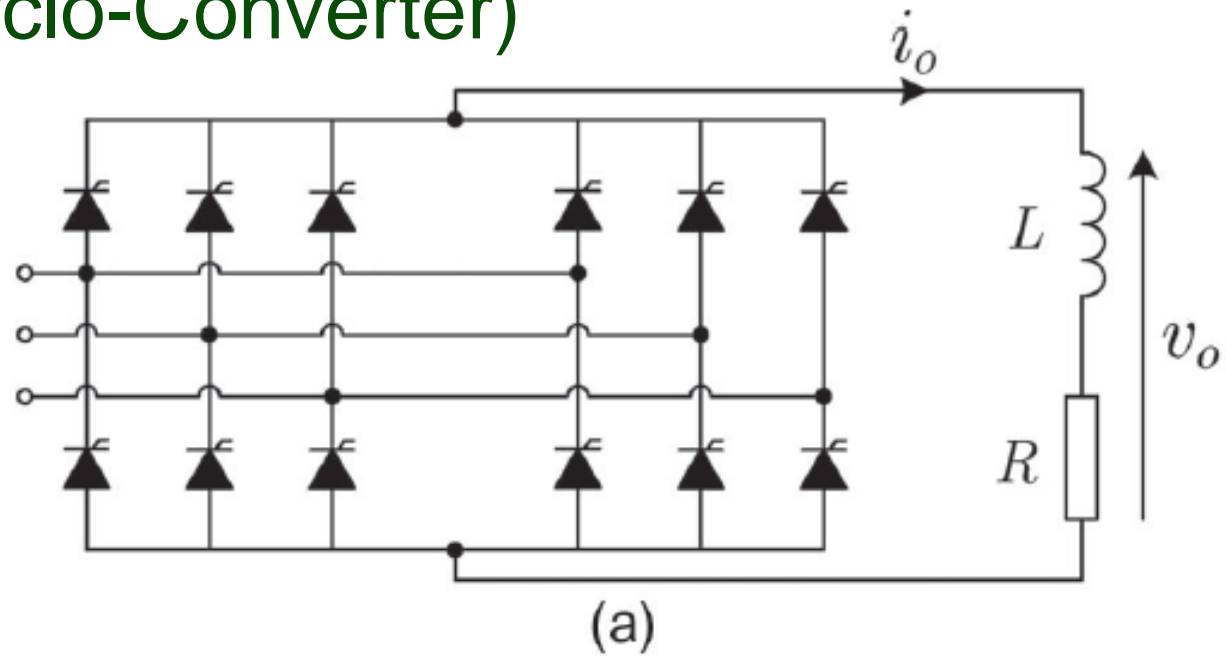



12P CCV

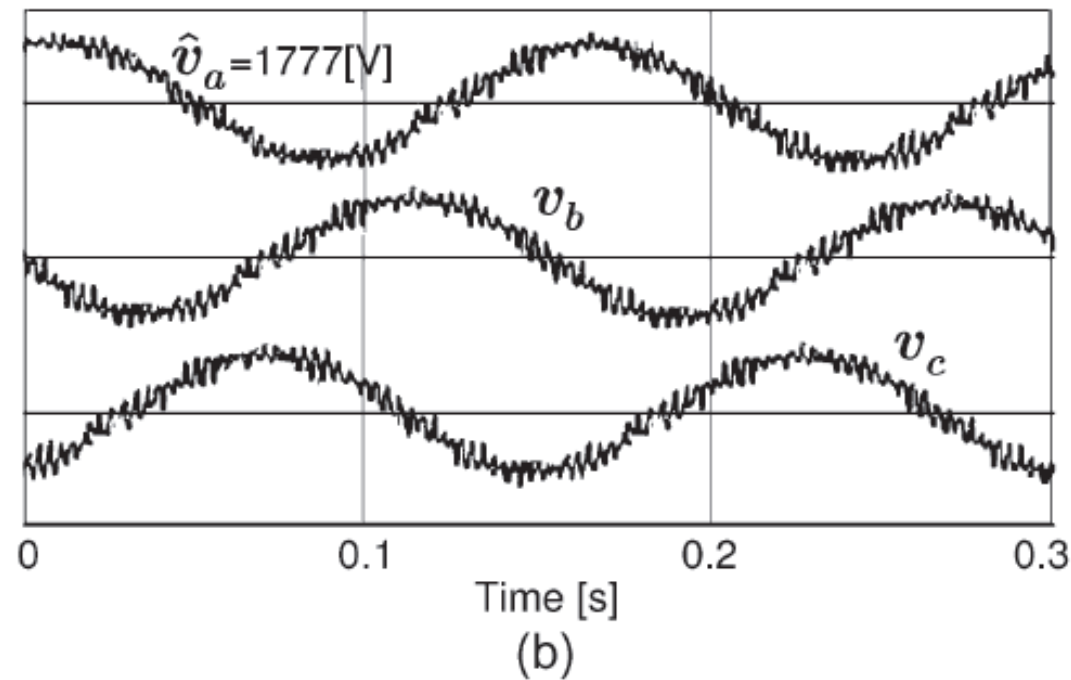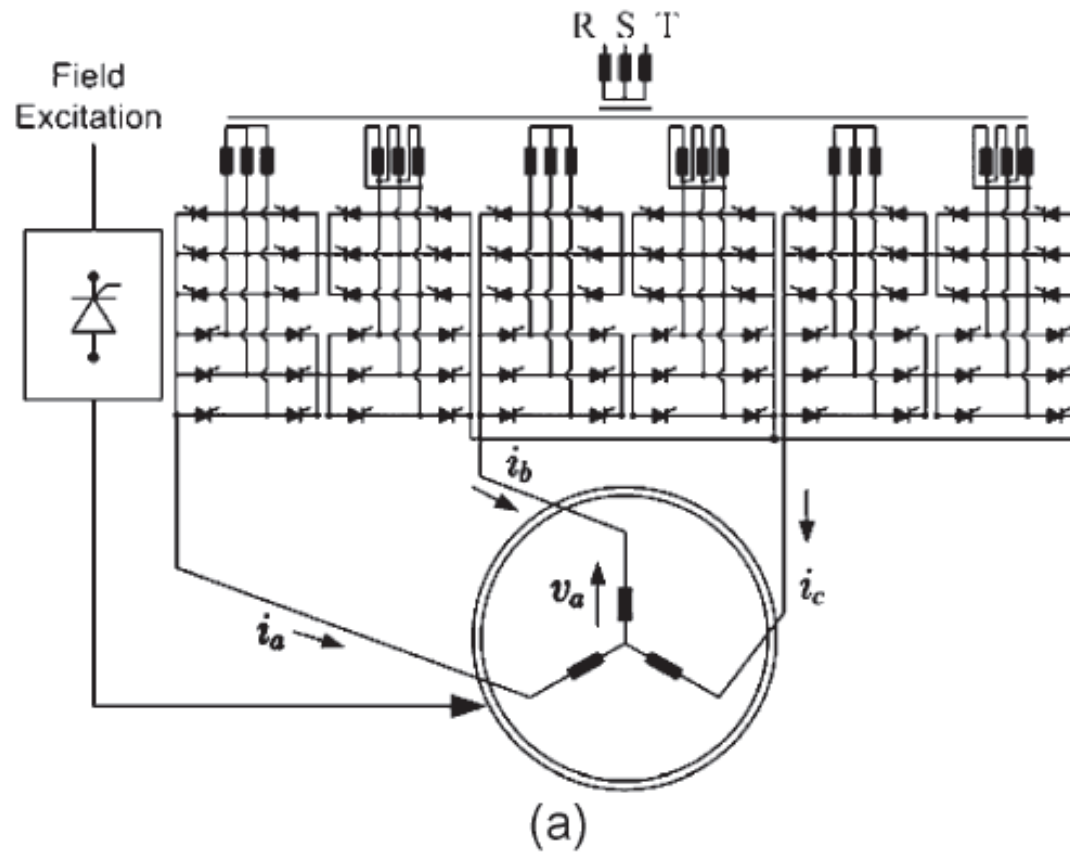



Reflected Waves

- Affected by:
 - Length of cable between drive and motor
 - Rate of rise of voltage (dV/dt)
 - Voltage step size
 - Pulse width



short

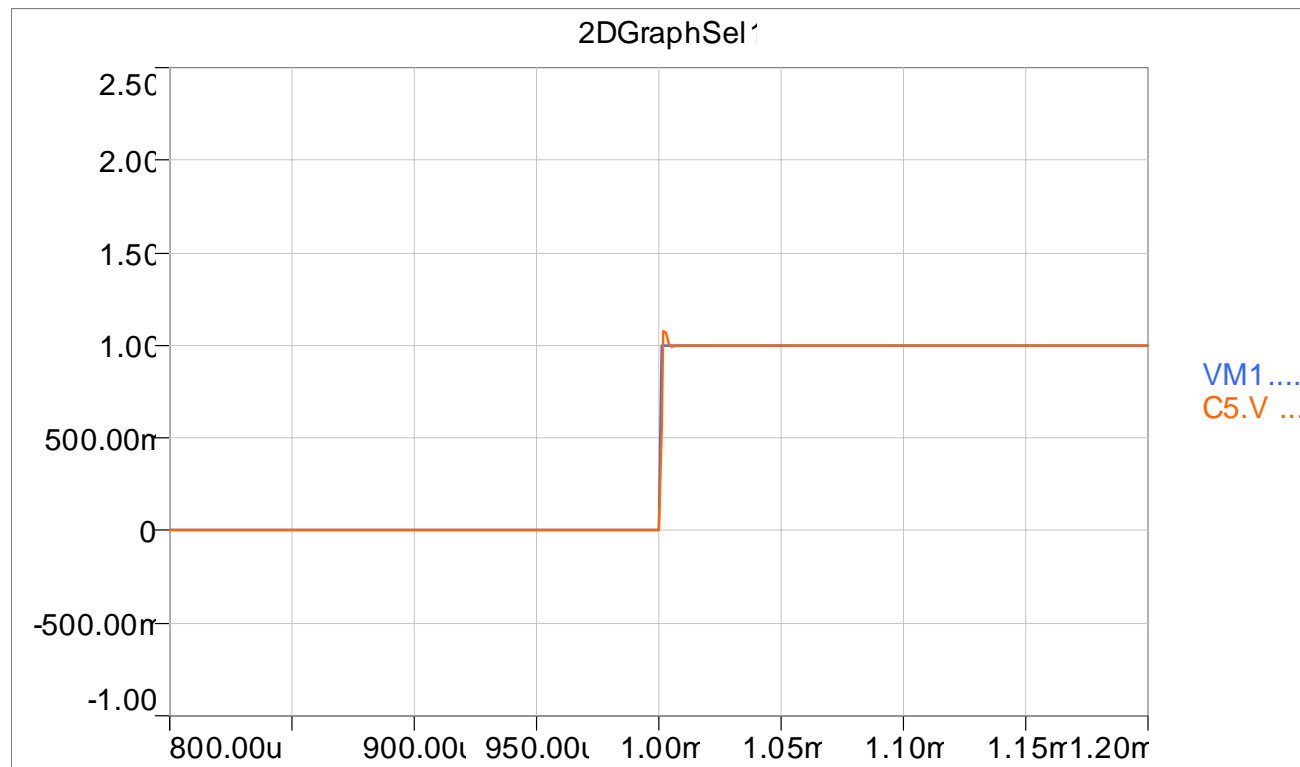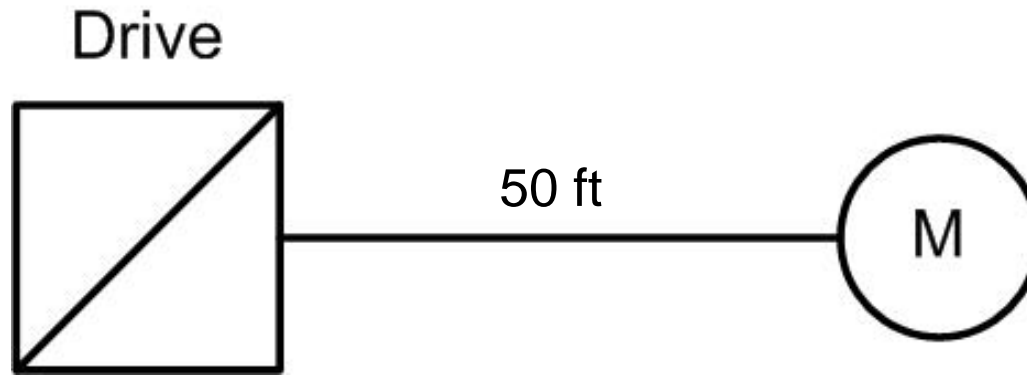

longer

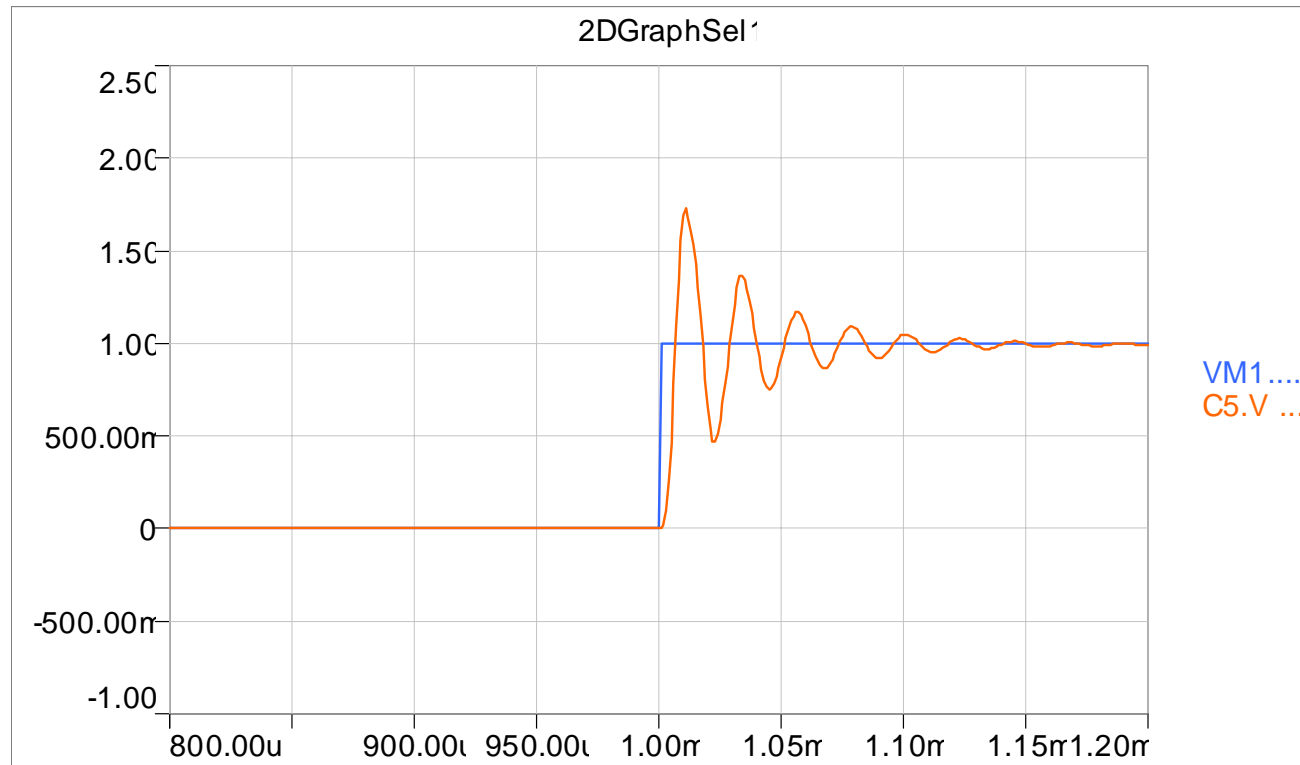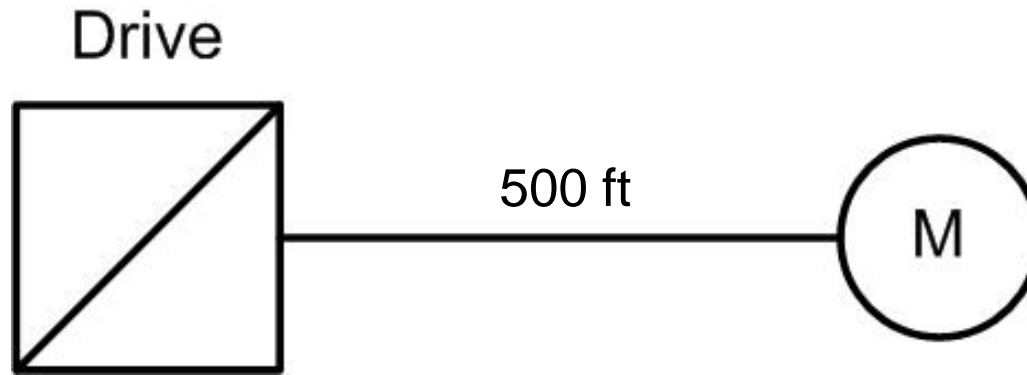


longest


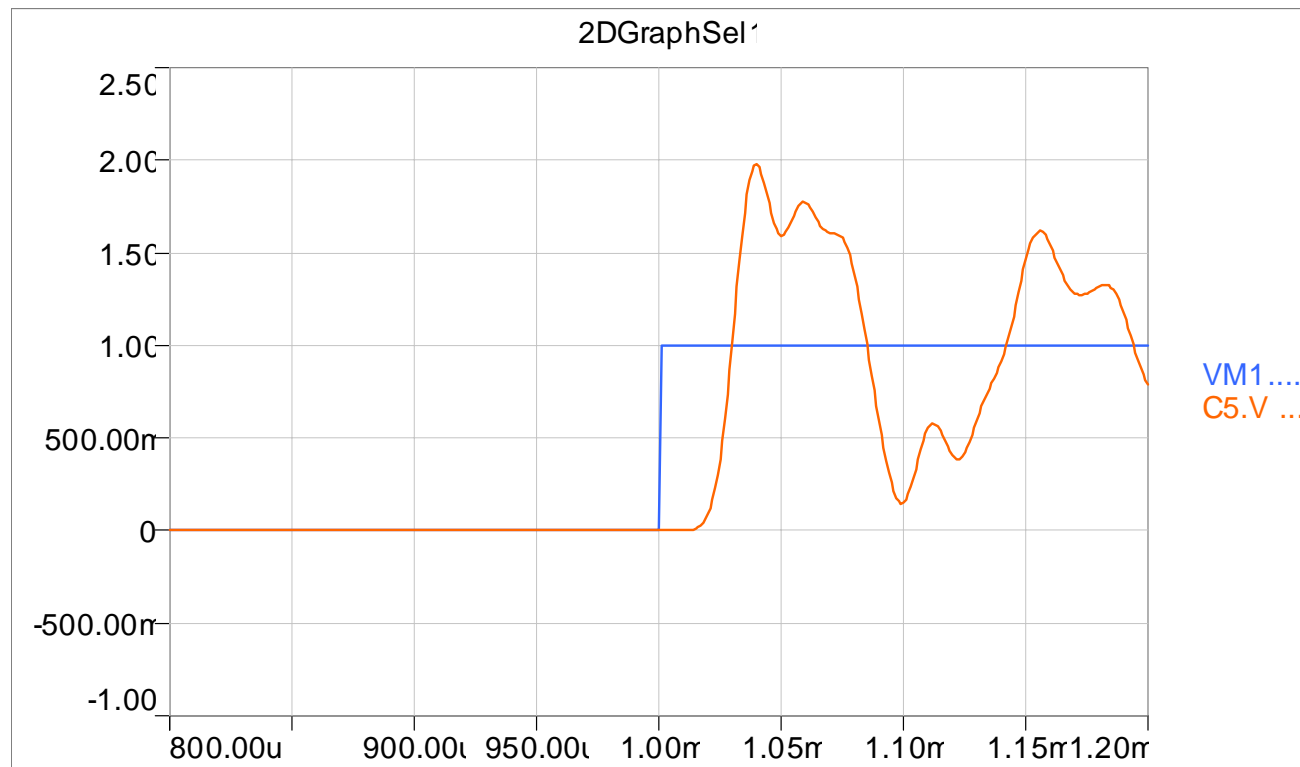
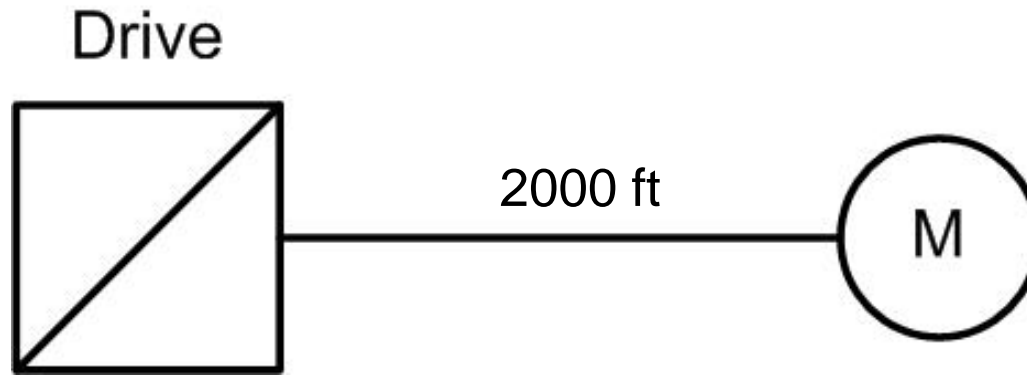


When does PD (Corona) occur?

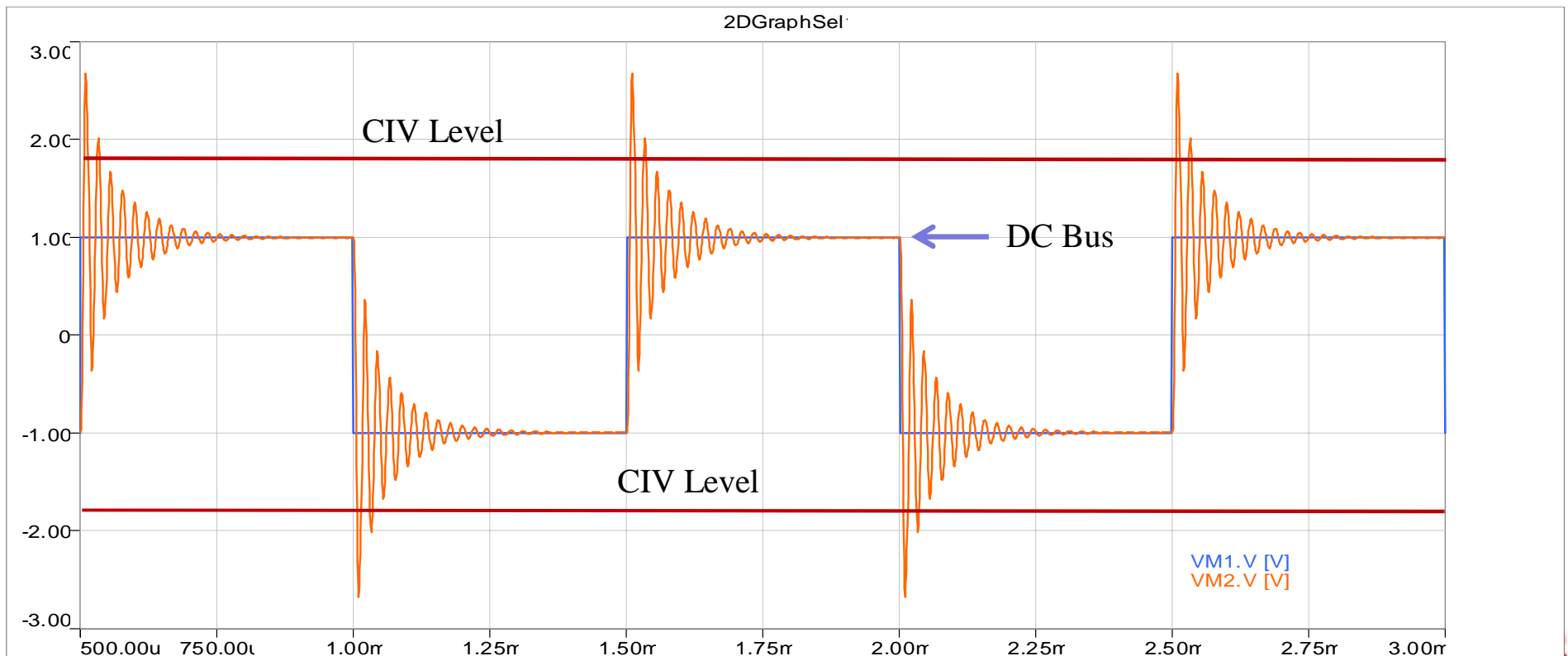- Reflected wave produces voltage peaks at the motor terminals
- Terminal voltage in excess of the insulation system CIV level will begin the PD / CORONA process
- Excessive voltage causes partial discharges / corona that attacks insulation materials




Partial Discharge

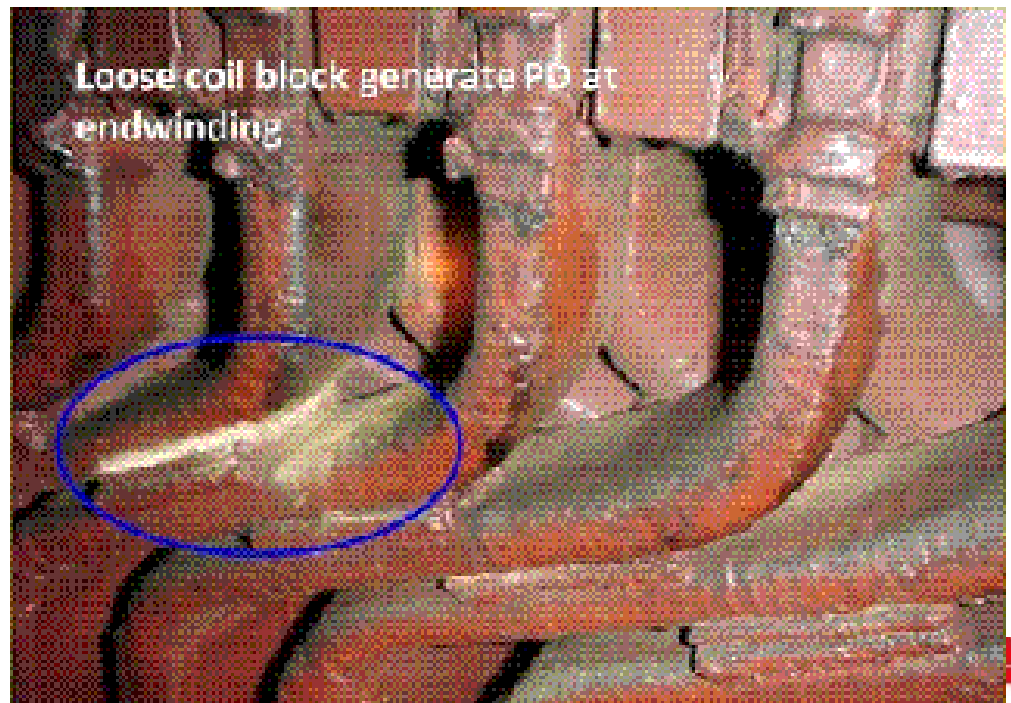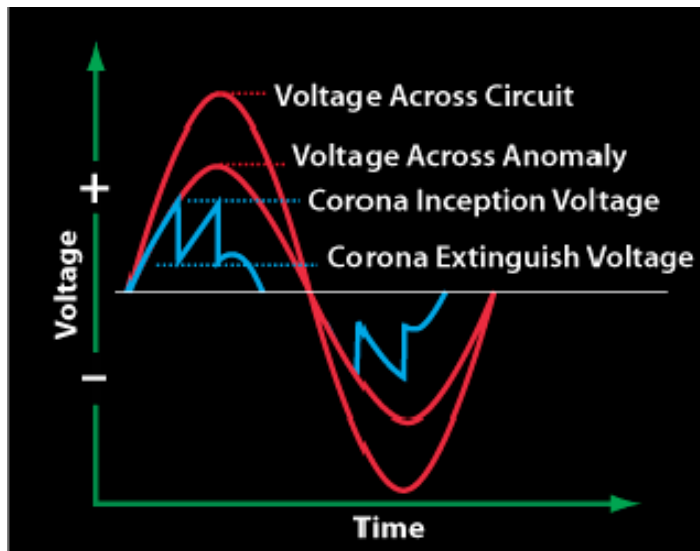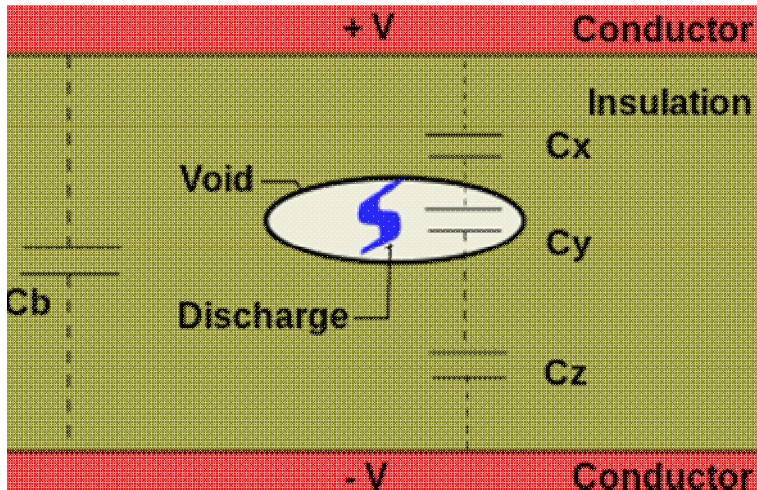


How can we reduce the dV/dt ?

Filtering


* Used in MV drives

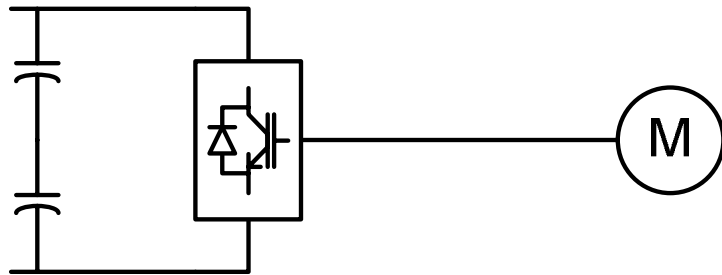


Basic Inverter and Motor

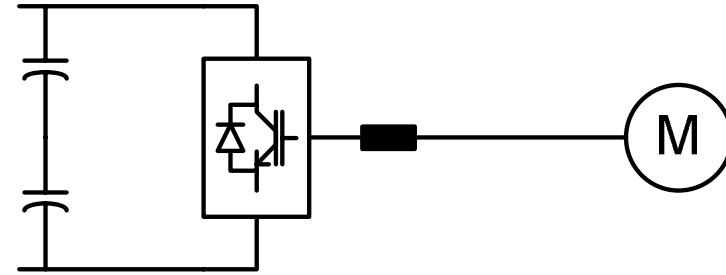


Output Load Reactor

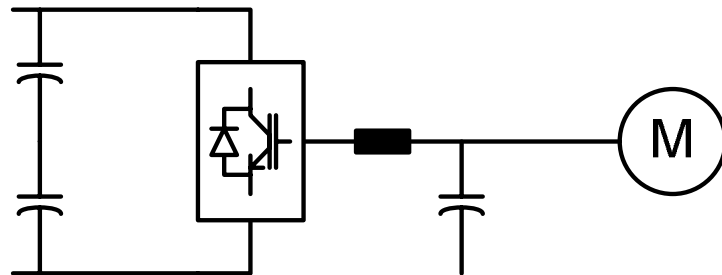


* dV/dt Filter

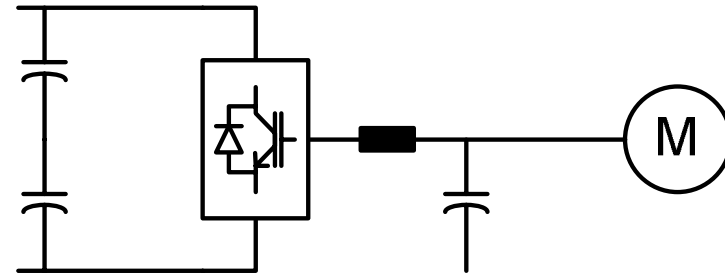

*Broadband Sinewave Filter


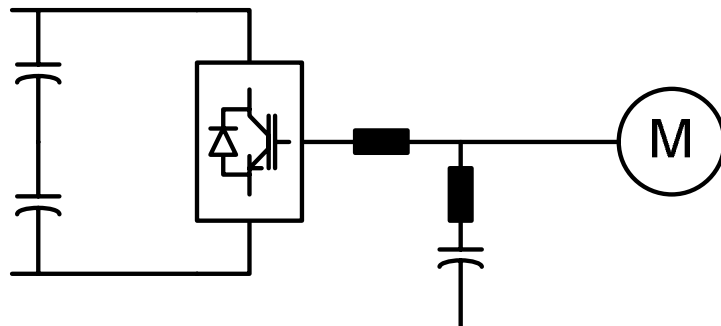


Sinewave Filter

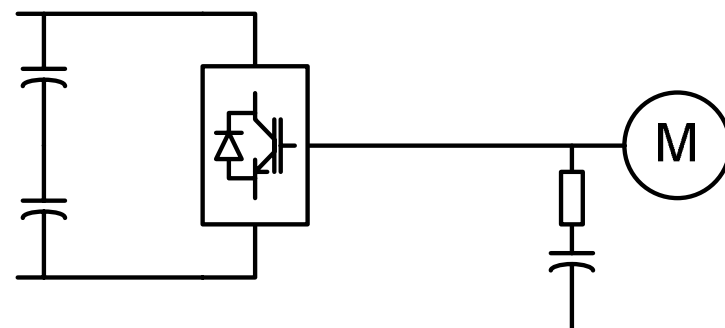



RC Terminator

Step size of 100%

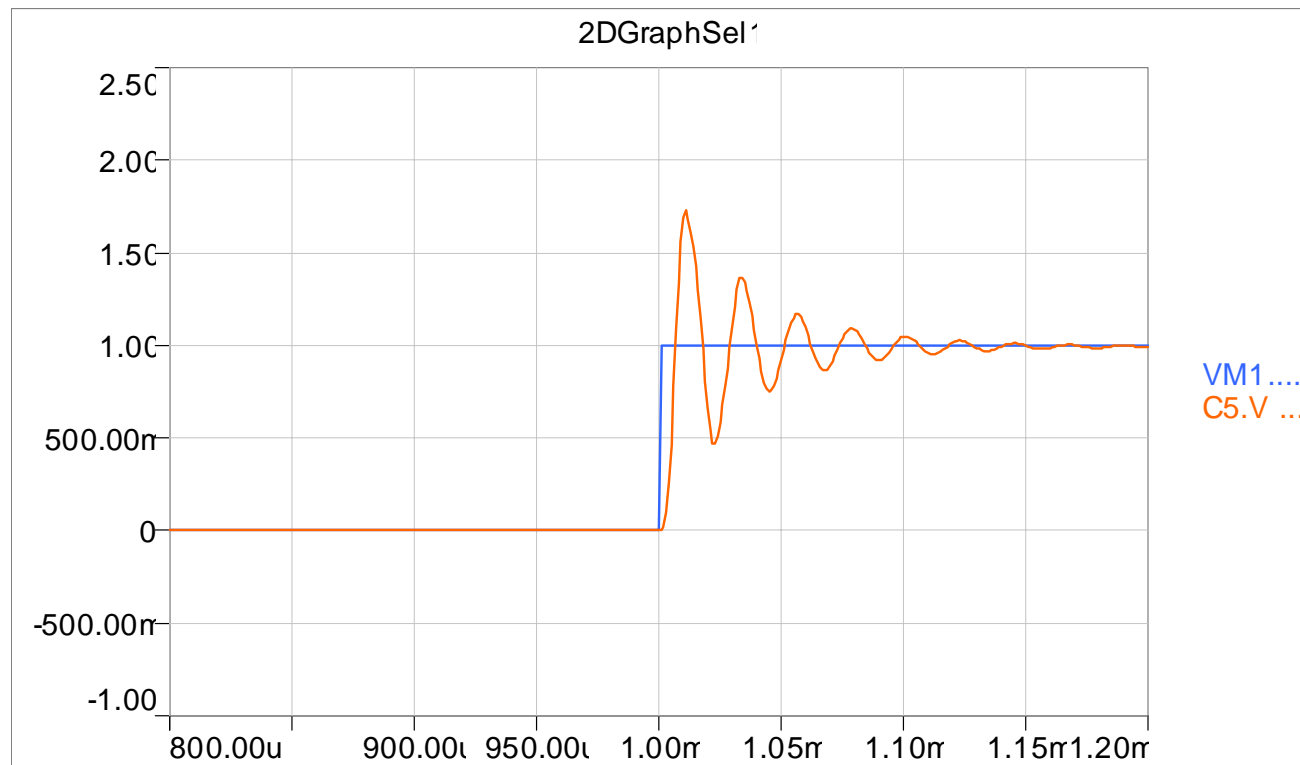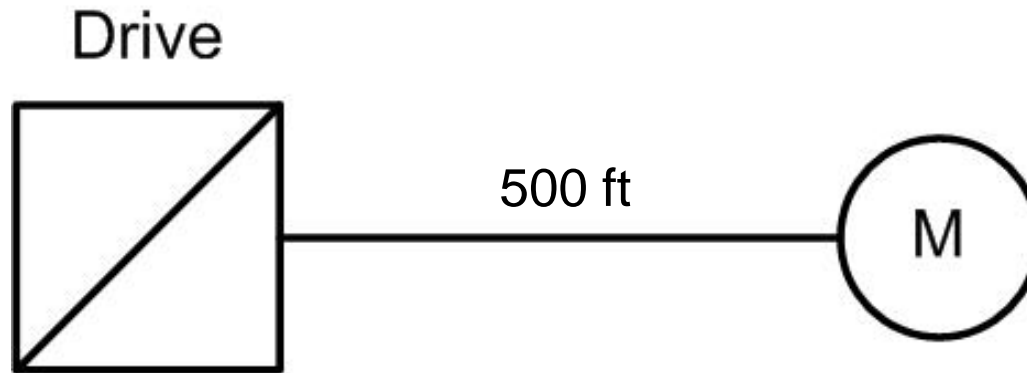

Vpk is about 1.7x the Voltage step size



Step size of 20%

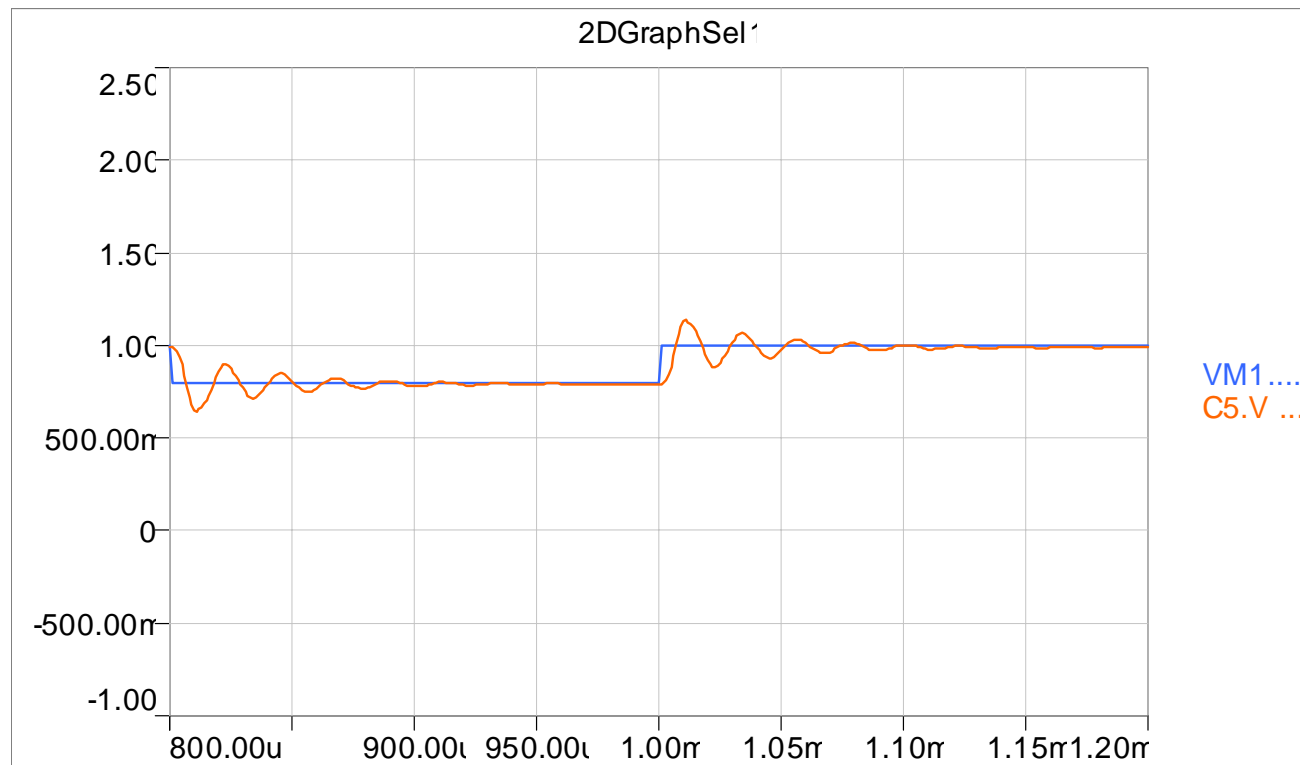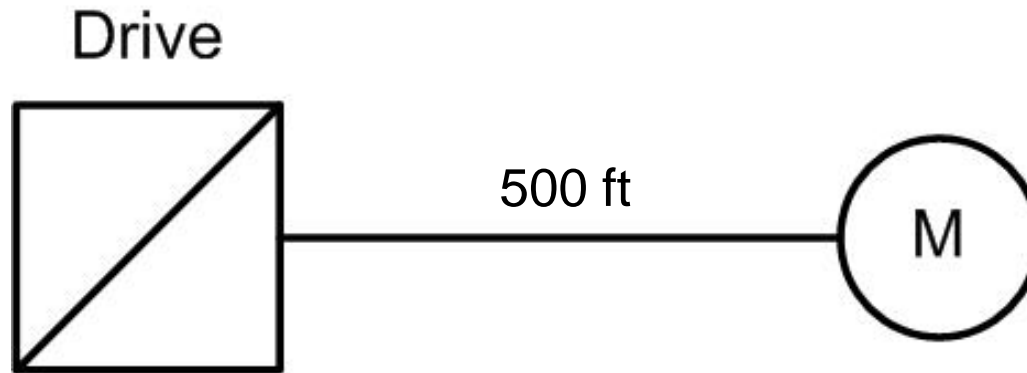


Have small voltage steps

$$dV/dt = 10,000 \text{ V/us}$$


Drive

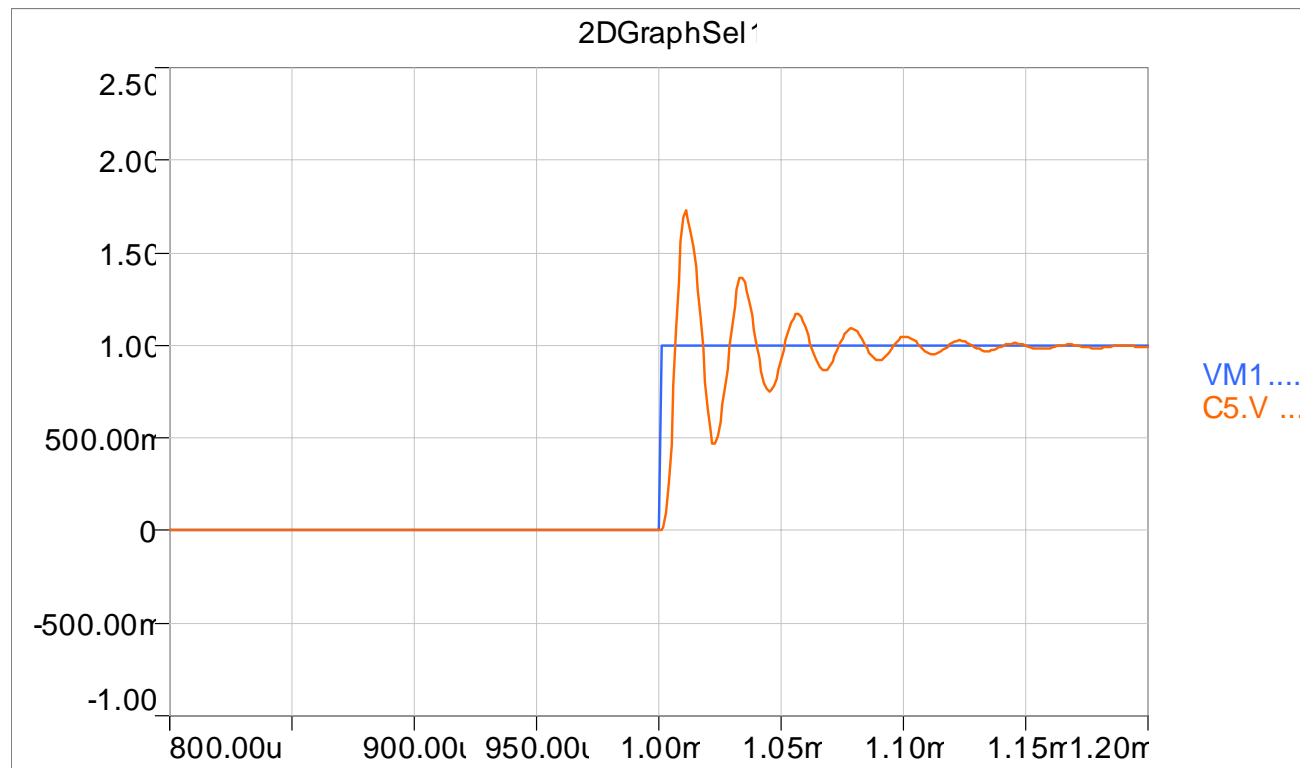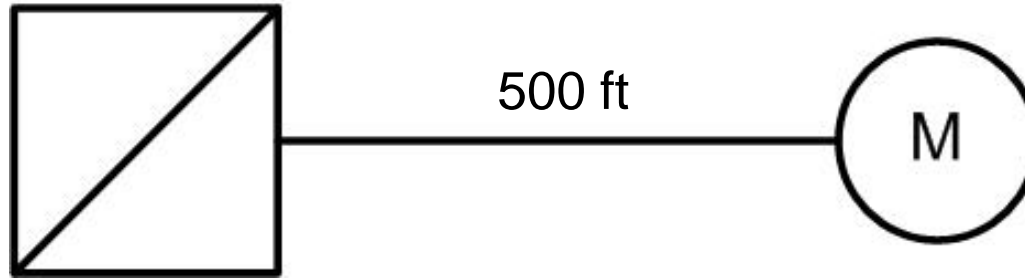


$$dV/dt = 500 \text{ V/us}$$

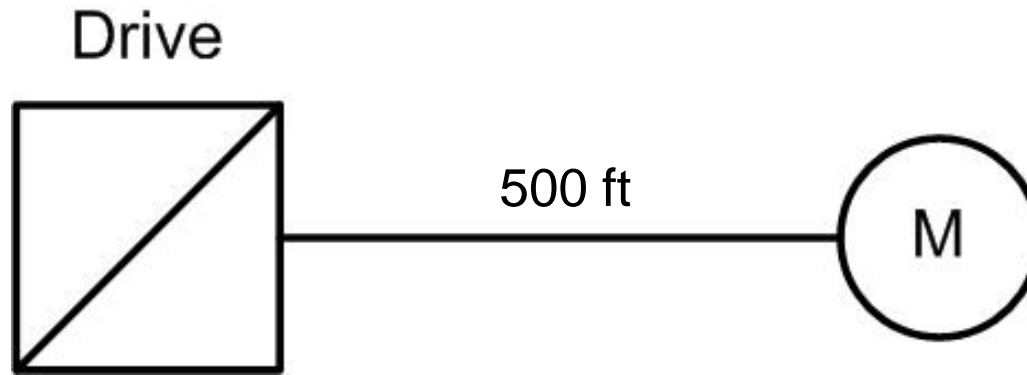

Multi-Step Approach, low dV/dt

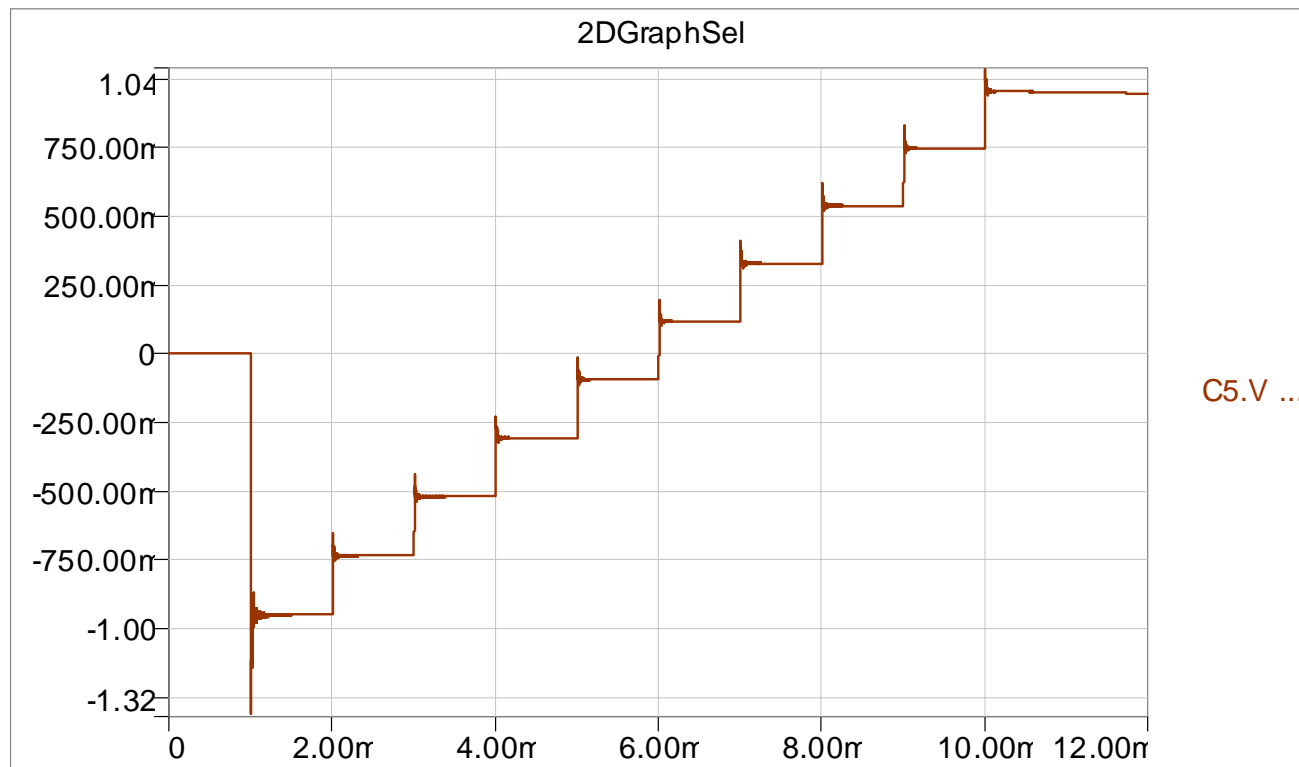


Implementation in a MV Drive

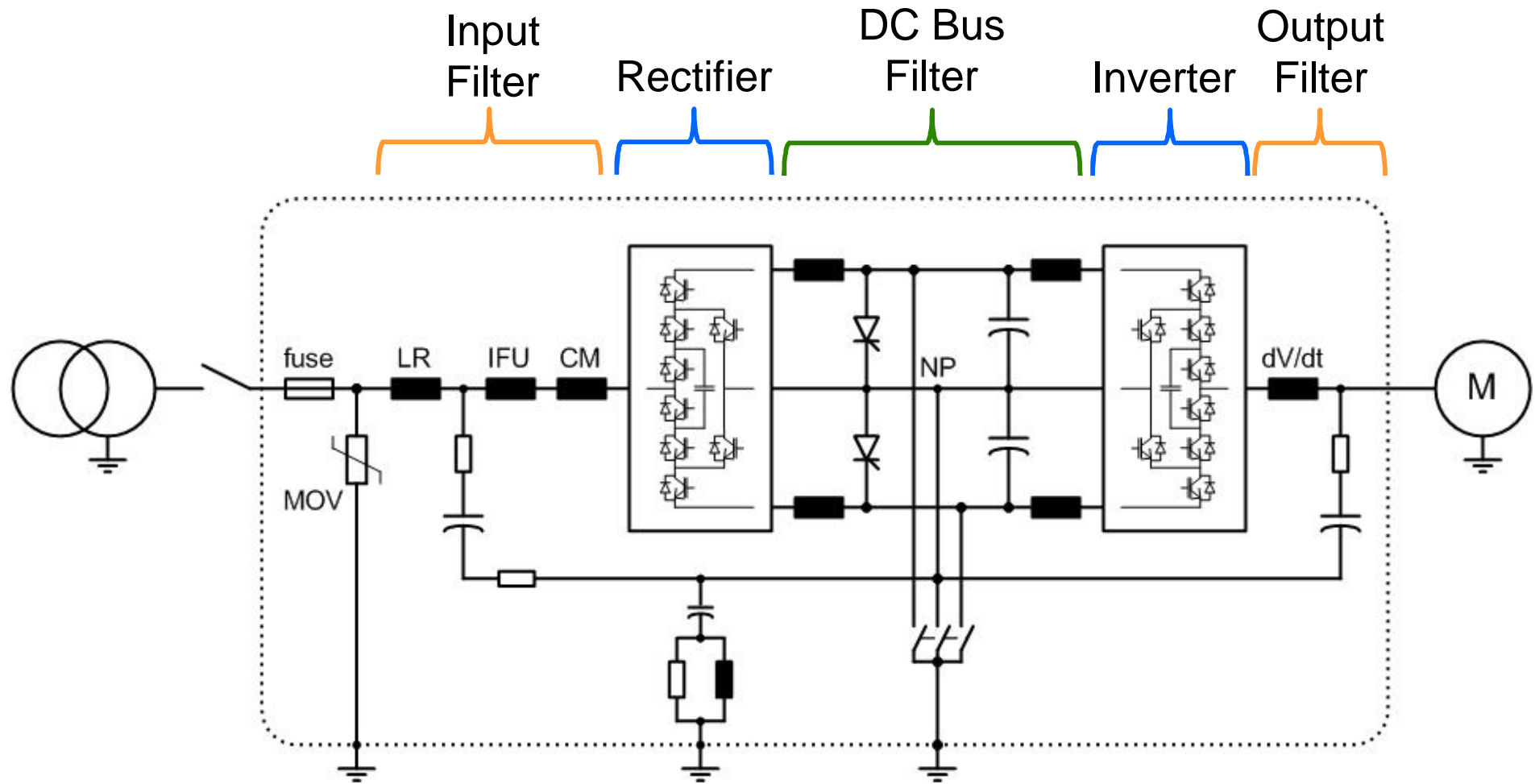

The n-level VSI topology



5-Level phase-to-phase voltage levels

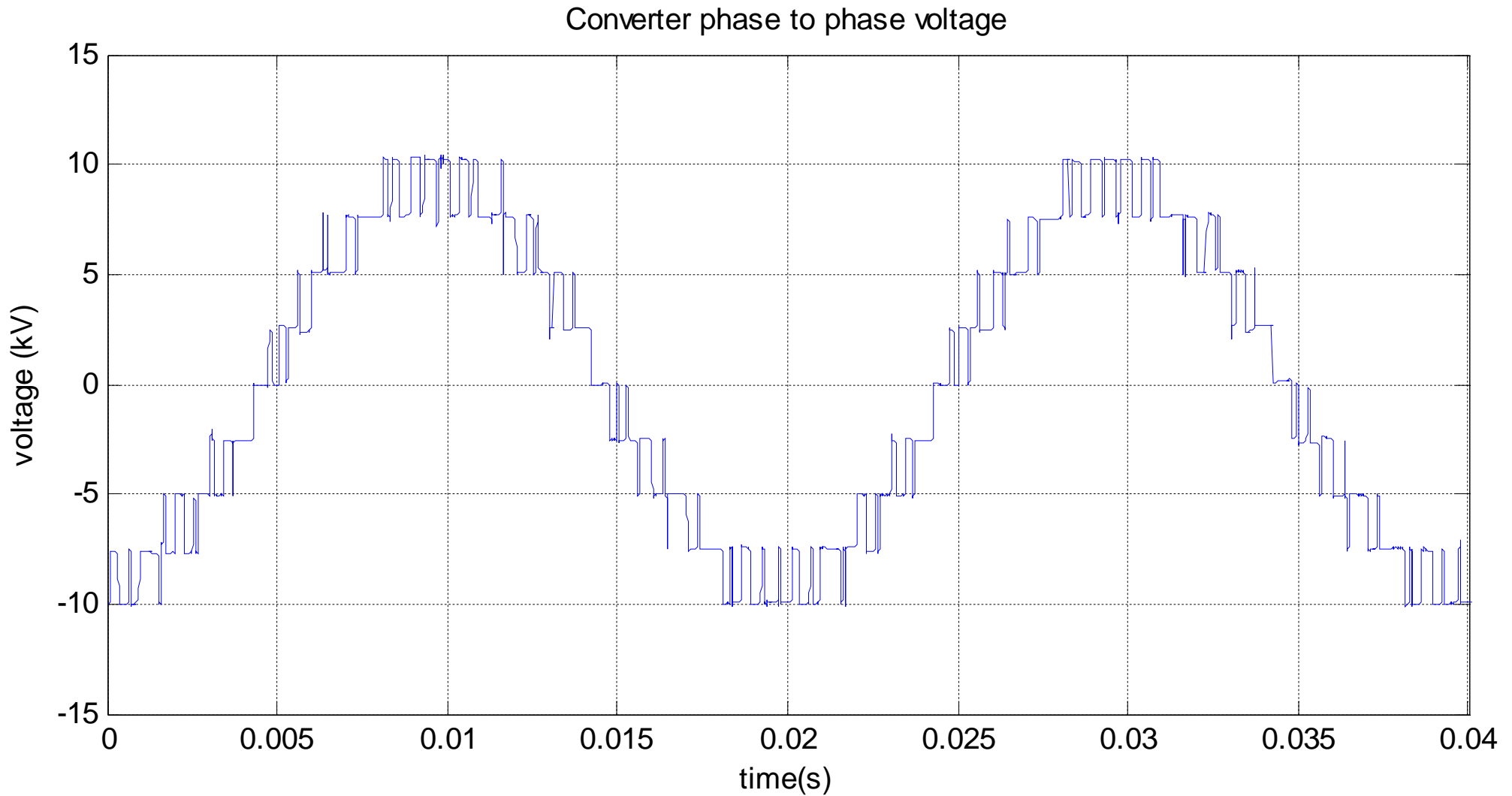


Protection

- PQ Events
- Over-Voltage
- Over-Current

Drive Self Monitoring – LV Drive

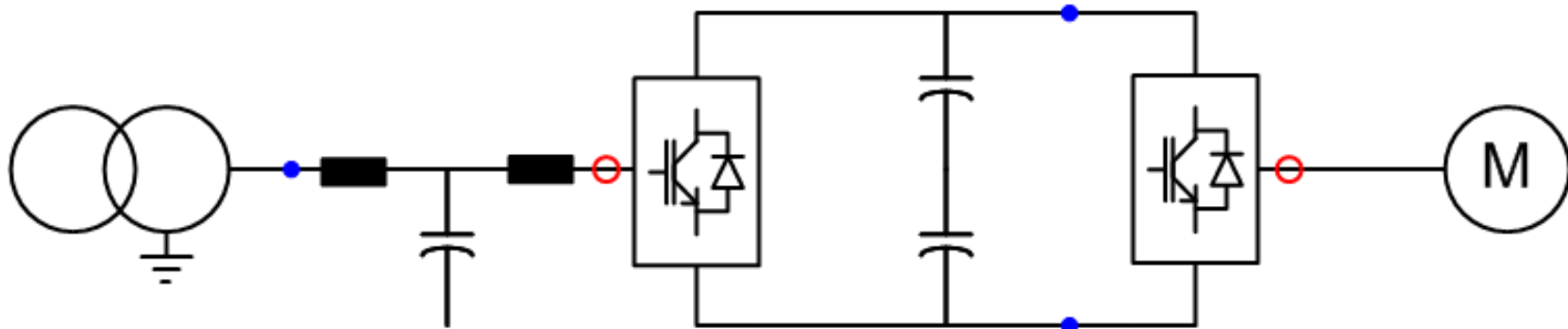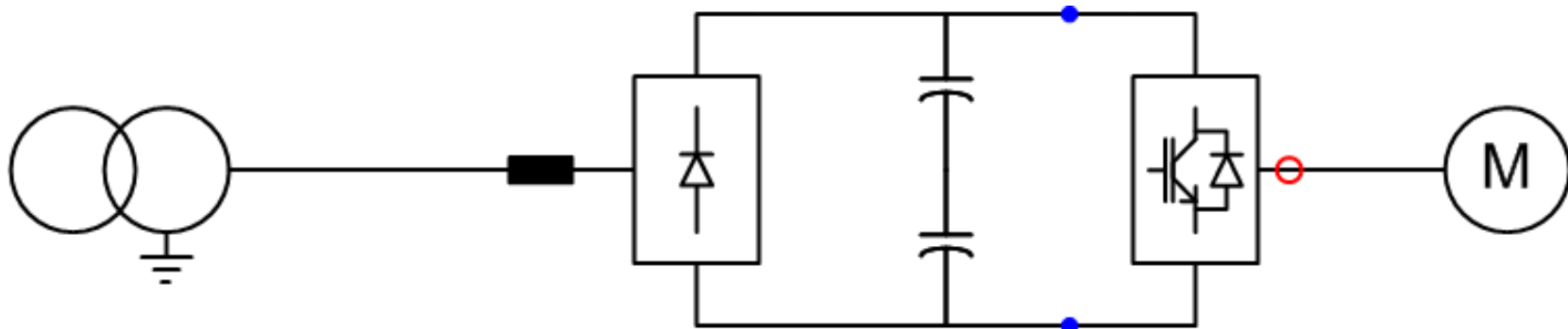

Drive Self Monitoring – MV Drive

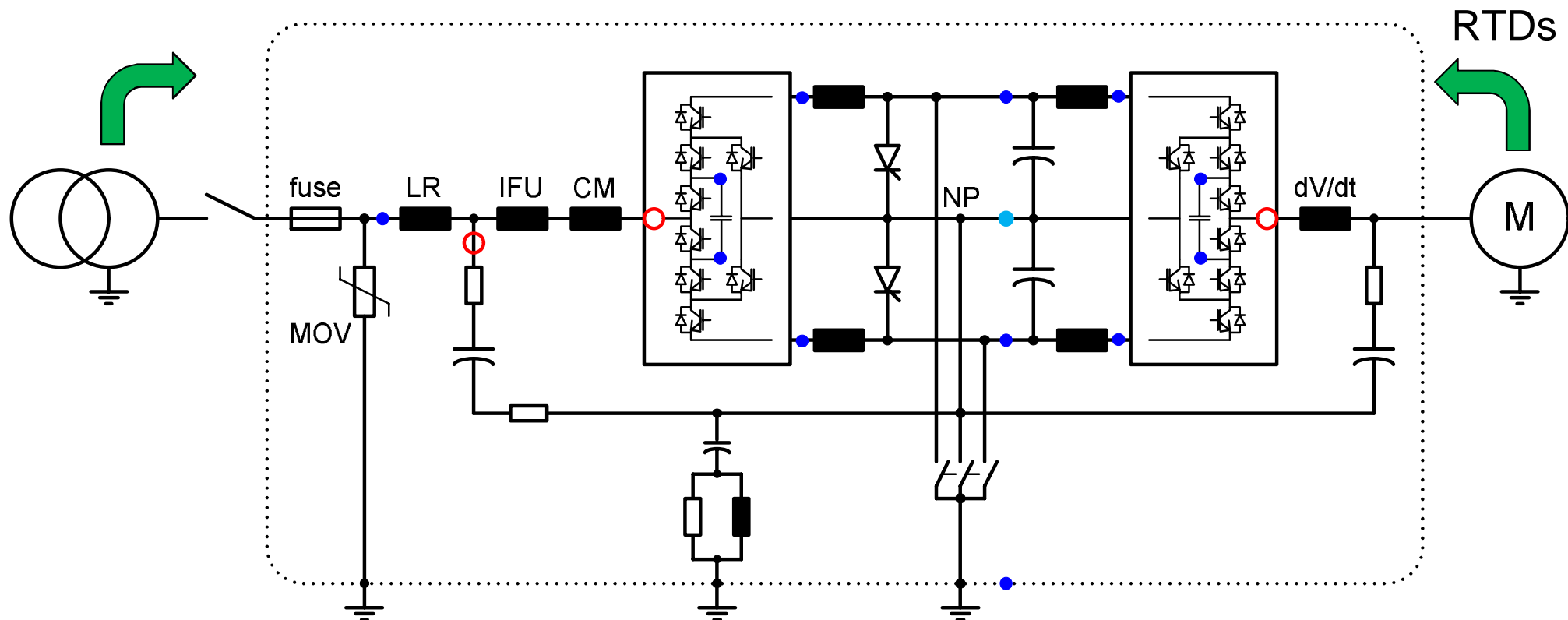

RTDs

M

Operation and Protection Concept

- Try to keep operating
- If unable to due to external issues
 - Alarm, but don't stop
 - Trip
- If catastrophic failure
 - Limit collateral damage
 - Minimal MTTR (mean time to repair)
- Look-out for its motor and transformer, too!
 - Like a big brother or sister

LV Low Harmonic Drives

Active front end drives, what do they look like?

Wall-mounted low harmonic drive ACS800-U11/U31

10 – 125 HP



Cabinet-built low harmonic drive ACS800-17/37

75 - 2800 HP



MV Low Harmonic Drives

Active front end drives, what do they look like?



MV Drives


ACS 2000 4kV - 6.9kV

300 – 3,000 HP

ACS 6000 2.3kV, 3.3kV

4,000 – 31,000 HP

Questions?

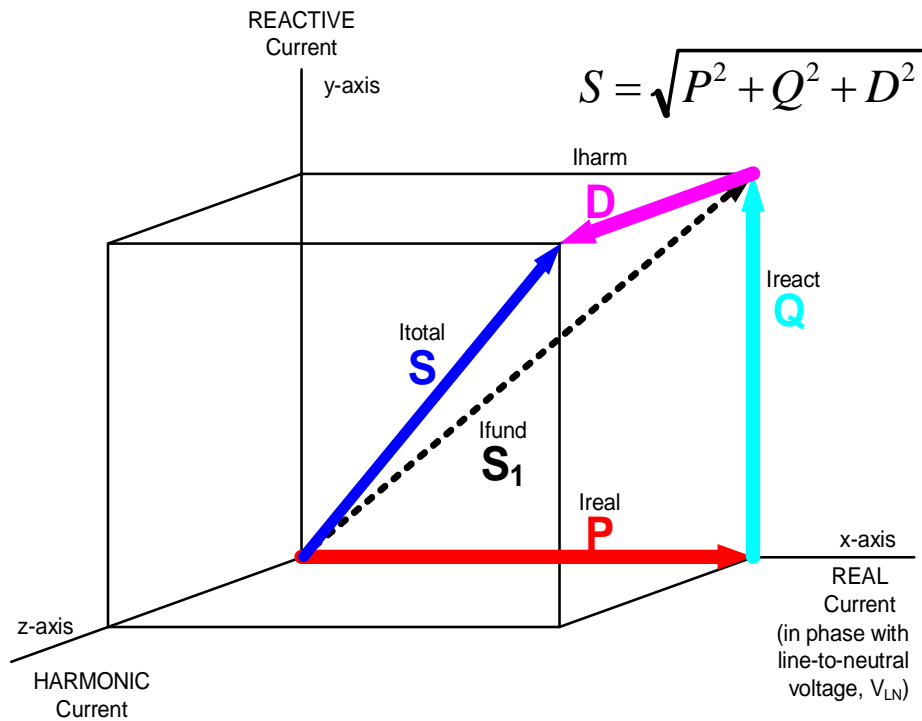

Rick Hoadley
ABB, New Berlin, WI
(262) 408-1589
Rick.L.Hoadley@us.abb.com



Power and productivity
for a better world™

